

USN

--	--	--	--	--	--	--	--	--	--

**NEW SCHEME**


**Fourth Semester B.E. Degree Examination, Dec.06 / Jan.07**  
**Electronics and Communication Engineering**  
**Power Electronics**

Time: 3 hrs.]

[Max. Marks:100

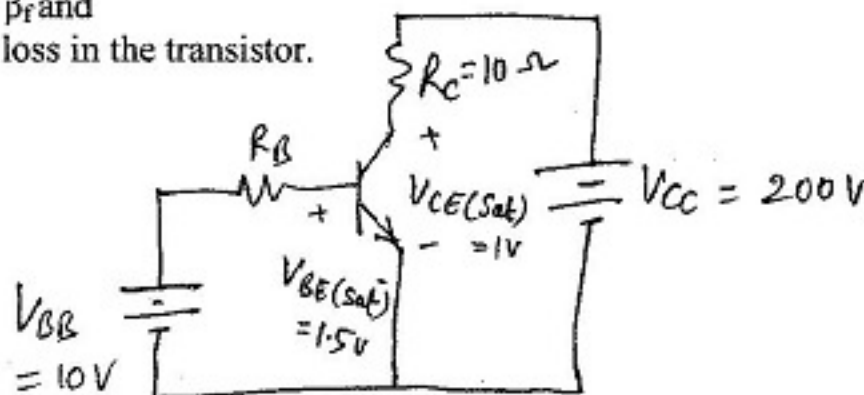**Note: 1. Answer any FIVE full questions.**

- 1
  - a. Give a list of Power Electronic circuits for different input / output requirements. (05 Marks)
  - b. Discuss the peripheral effects of Power Electronics equipments. (05 Marks)
  - c. With model and waveforms, explain how the internal capacitances of the transistor influence the switching characteristics of the transistor. (10 Marks)
  
- 2
  - a. Explain the anti saturation control technique used to improve the switching speed of a power B.J.T. (06 Marks)
  - b. Discuss methods of providing isolation of gate/base circuits from power circuits. (06 Marks)
  - c. A transistor switch of Fig Q2 (c) has  $\beta$  in the range of 8 to 40. Calculate
    - i) The value of  $R_B$  that results in saturation with an overdrive factor of 5.
    - ii) The forced  $\beta_f$  and
    - iii) The power loss in the transistor. (08 Marks)



- 3
  - a. Explain the principle of operation of an SCR using two transistor model. (06 Marks)
  - b. What is the need for protection of thyristors. Explain how thyristors are protected against high  $\frac{di}{dt}$  and high  $\frac{dv}{dt}$ . (07 Marks)
  - c. A string of series connected thyristors is to with stand a dc voltage of 16 kV. The maximum leakage current and recovery charge differences of the thyristors are 10 mA and 100  $\mu$ C respectively. The derating factor for steady-state and transient voltage sharings are 20%. For a maximum steady state voltage sharing of 1 kV. Determine
    - i) The steady state voltage sharing resistance R for each thyristor and
    - ii) The transient voltage capacitance  $C_1$  for each thyristor. (07 Marks)

- a. What is forced commutation? Discuss the following forced commutation techniques.  
 i) Self commutation.  
 ii) Impulse commutation. (14 Marks)
- b. Obtain proper values of the commutating components for the circuit shown in Fig. Q4 (b). The load current to be commutated is 5 A, turn off time is 50  $\mu$ sec. Supply voltage is 100 V, SCR<sub>2</sub> holding current is 2 mA. Derive the equation used. (06 Marks)

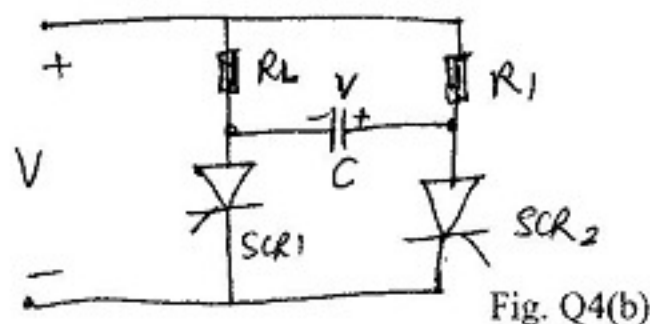


Fig. Q4(b)

- a. With necessary waveforms, explain the operation of a 1 $\phi$  full wave controller with inductive load. Derive expressions for rms output voltage and rms output current. (10 Marks)
- b. Explain why short duration gate pulses are not suitable for bidirectional ac voltage controllers with inductive loads. (03 Marks)
- c. A 1 $\phi$  full wave ac voltage controller supplies a resistive load of  $R = 10 \Omega$  from an input voltage  $V_s = 200$  V, 60 Hz. The delay angles of the thyristors are equal,  $\alpha_1 = \alpha_2 = \frac{\pi}{2}$ . Determine  
 i) The rms output voltage.  
 ii) The input p.f and  
 iii) Average current of thyristors  
 iv) Rms current of thyristors. (07 Marks)
- a. With the help of relevant waveforms, explain the working of a 1 $\phi$  full converter assuming continuous current operation. Derive expressions for average and rms output voltages. (10 Marks)
- b. With necessary waveforms explain the working of a 3 $\phi$  half wave converter. Obtain expressions for average and rms output voltages. (10 Marks)
- a. Explain the principle of operation of a step-up chopper. (06 Marks)
- b. With the help of necessary mode equivalent circuits and waveforms, explain the operation of an impulse commutated chopper. (14 Marks)
- a. What are inverters? Explain the working of an half bridge inverter with necessary waveforms. What is the function of the feed back diodes? (10 Marks)
- b. Explain how the output voltage of a 1 $\phi$  inverter is controlled using sinusoidal P.W.M technique. (10 Marks)