

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

Fourth Semester B.E. Degree Examination, Dec.09/Jan.10
Power Electronics

Time: 3 hrs.

Max. Marks:100.

**Note:1. Answer any FIVE full questions, selecting
at least TWO questions from each part.
2. Missing data may be suitably assumed.**

Part – A

- 1 a. Give the circuit symbol, output characteristics and applications of various semiconductor devices. (10 Marks)
- b. With the help of circuit and waveforms, explain the various types of power electronic converter circuits. (10 Marks)
- 2 a. With the help of necessary waveforms, explain the switching characteristics of a BJT. (06 Marks)
- b. With the help of necessary waveforms, explain the switching characteristics of an IGBT. (06 Marks)
- c. What is the necessity of base drive control? Explain the various methods of base drive control used for BJTs. (08 Marks)
- 3 a. Explain the two transistor analogy of a thyristor. (06 Marks)
- b. Mention and explain the various methods of turn ON used for thyristors. (08 Marks)
- c. The thyristor is gated with a pulse width of 40 μ sec. The latching current of thyristor is 36 mA. For a load of 60 Ω and 2 H, will the thyristor get turned ON? If the answer is negative, how this problem can be overcome for the given load? Find the value of remedial parameter. Given $V_s = 300V$. (06 Marks)
- 4 a. What do you mean by commutation? Explain the method of self commutation with necessary circuit and waveforms. (07 Marks)
- b. With necessary circuit and waveforms, explain the complementary commutation method. (07 Marks)
- c. In the resonant pulse commutation circuit, the capacitance $C = 30 \mu F$ and inductance $L = 4 \mu H$. The initial capacitor voltage is $V_0 = 200 V$. Determine the circuit turn-off time t_{off} if the load I_m is 50 A. (06 Marks)

Part – B

- 5 a. With the help of circuit diagram and waveforms, explain the operation 1Q bidirectional voltage controller with R-L load. (07 Marks)
- b. Explain the principle of ON-OFF control. Obtain an expression for rms voltage, rms current and p.f. for full wave AC voltage controller. (07 Marks)
- c. A single phase half wave ac voltage controller has a resistive load of $R = 10 \Omega$ and the input voltage $V_s = 120 V$, $f = 60 Hz$, $\alpha = \frac{\pi}{2}$. Determine i) rms value of output voltage, ii) Input power factor iii) Average input current. (06 Marks)

Important Note: 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42-8=50, will be treated as malpractice.

- 6 a. For a single phase semi-converter with R-L load operating in continuous mode, i) Draw the circuit diagram, input and output waveforms ii) Derive an expression for average and rms output voltages. (10 Marks)
- b. With the circuit diagram, explain the operation of three phase full converter for constant load current. If the input to this circuit is 3 phase, 50 Hz supply, determine the firing angle α for the SCRS to obtain an output average dc voltage of 50% of the maximum. If this output voltage is 270 V, calculate ac supply line-line rms voltage. (10 Marks)
- 7 a. What is chopper? Explain the operation of various types of chopper. (08 Marks)
- b. With the help of circuit and waveforms, explain the operation of step up chopper. (06 Marks)
- c. In the step down chopper $V_s = 230$ V, load resistance is 10Ω . Take a voltage drop of 2 V across chopper when it is ON. For a duty cycle of 0.4, calculate i) Average and rms values of output voltage. ii) Chopper efficiency. (06 Marks)
- 8 a. Explain the concept of sinusoidal modulation technique of voltage control in an inverter. (06 Marks)
- b. What is the effect of harmonics? Explain harmonic reduction by transformer connection method. (08 Marks)
- c. For the inverter circuit shown in figure,
 i) Sketch to scale the waveforms of V_o , i_o , i_{Q1} , i_{Q2} , i_1 and i_2 .
 ii) Power delivered to load.
 iii) State whether this circuit will require forced commutation. (06 Marks)

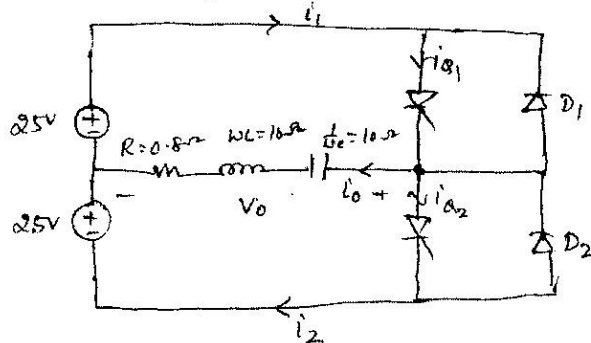


Fig. Q8 (c)
