

USN

--	--	--	--	--	--	--	--	--	--

10EE45

Fourth Semester B.E. Degree Examination, Dec.2017/Jan.2018
Power Electronics

Time: 3 hrs.

Max. Marks:100

Note: 1. Answer FIVE full questions, selecting at least TWO questions from each part.
2. Draw suitable sketches wherever necessary.

PART - A

1.
 - a. What is power electronics? Mention its industrial applications. (05 Marks)
 - b. With neat diagram and waveforms, explain control characteristics of (i) SCR and (ii) IGBT. (08 Marks)
 - c. Describe thyristorised tap changer with a neat schematic. (07 Marks)
2.
 - a. Compare BJT, MOSFET and IGBT (any four points). (04 Marks)
 - b. For the circuit shown in Fig. Q2 (b) the details are given. The bipolar transistor is specified to have β_f in the range of 8 to 40. The load resistance is $R_c = 11 \Omega$. The DC supply voltage is $V_{CC} = 200 \text{ V}$ and the input voltage to the base circuit is $V_B = 10 \text{ V}$. If $V_{CE(sat)} = 1 \text{ V}$ and $V_{BE(sat)} = 1.5 \text{ V}$ find (i) the value of R_B that results in saturation with an ODF of 5, (ii) the β_{forced} and (iii) the power loss P_T in the transistor. (10 Marks)

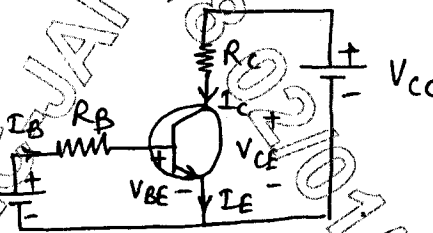


Fig. Q2 (b)

- c. With a neat sketch describe the construction of IGBT. (06 Marks)
3.
 - a. With the help of a two transistor model derive the expression for anode current for an SCR. (10 Marks)
 - b. Calculate the values of R , R_{B1} and R_{B2} for the following UJT trigger circuit. The parameters of UJT are $V_s = 30 \text{ V}$, $\eta = 0.51$, $I_p = 10 \mu\text{A}$, $V_v = 3.5 \text{ V}$ and $I_v = 10 \text{ mA}$ and $C = 0.5 \mu\text{F}$. Assume $V_D = 0.5$ and frequency of oscillations $f = 60 \text{ Hz}$, width of the triggering pulse $t_g = 50 \mu\text{s}$. (10 Marks)

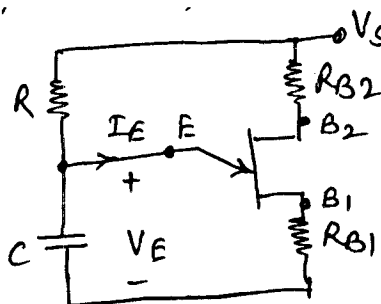


Fig. Q3 (b)

Important Note : 1. On completing your answers compulsorily draw diagonal cross lines on the remaining blank pages. 2. Any scribble or modification after evaluation and for questions written on 2, 3, 4, 5, will be treated as unattempted.

- 4 a. What do you mean by commutation in thyristors? Differentiate between natural and forced commutation. (06 Marks)
- b. With the help of a schematic and waveforms explain complementary commutation. (08 Marks)
- c. For the commutation circuit shown in Fig. Q4 (c) the DC source voltage is 120 V and the current through R_1 and $R_2 = 20$ A. The turn off time of both the SCRs is 60 μ sec. Calculate the value of commutations capacitor C for successful commutation. (06 Marks)

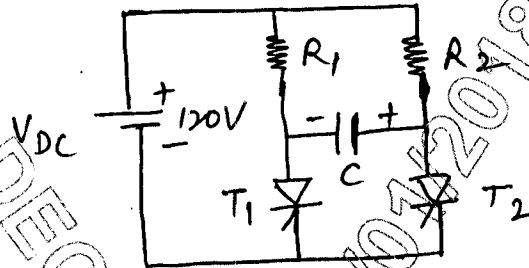


Fig. Q4 (c)

PART - B

- 5 a. With the help of a neat schematic and waveforms derive an expression for average output voltage of single phase semiconverter with RL load. (10 Marks)
- b. A single phase half wave controlled rectifier is used to supply power to 10 Ω load from 230 V, 50 Hz supply at a firing angle of 30°. Calculate (i) Average output voltage (ii) Effective output voltage (iii) Average load current (iv) Effective load current. (10 Marks)
- 6 a. What is chopper? What are the various types of chopper? (06 Marks)
- b. With the help of a schematic and waveform explain step down chopper. (08 Marks)
- c. A stepdown chopper has a resistive load of 10 Ω and the input voltage is 220 V. When the chopper switch remains on its voltage drop is $V_{ch} = 2$ V and the chopping frequency is 1 kHz. If the duty cycle is 50% determine (i) The average output voltage (ii) the rms output voltage and (iii) the chopper efficiency. (06 Marks)
- 7 a. Describe various performance parameters of inverter. (06 Marks)
- b. What are the drawbacks of single phase half bridge inverter? Explain the operation of single phase full bridge inverter for resistive load. (08 Marks)
- c. With relevant waveforms, explain the sinusoidal pulse width modulation in an inverter. (06 Marks)
- 8 a. Explain the principle of ON-OFF and phase control of AC voltage regulators. (06 Marks)
- b. With the help of circuit diagram and waveforms explain the operation of single phase AC voltage bidirectional controller with R-L load. Derive an expression for output voltage. (08 Marks)
- c. A single phase fullwave AC voltage controller has a resistive load of 10 Ω . Input voltage is 120 V (rms), 60 Hz. The delay angle of each thyristor is 90°. Find (i) rms output voltage and (ii) input power factor. (06 Marks)
