

--	--	--	--	--	--	--	--	--	--

Fourth Semester B.E. Degree Examination, Dec.2018/Jan.2019
Power Electronics

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting
atleast TWO questions from each part.**

PART – A

- 1 a. Explain briefly the concept of power electronics. (04 Marks)
- b. With help of neat block diagram, explain the functional elements of power electronics system. (08 Marks)
- c. Explain the different types of power electronics converters with applications. (08 Marks)
- 2 a. Draw and explain the operation of cross-sectional structure and switching characteristics of power MOSFET. (10 Marks)
- b. With the help of neat structural diagram, explain the switching and static characteristics of IGBT. (10 Marks)
- 3 a. With the help of neat diagram, explain the two transistor analogy of an SCR. (10 Marks)
- b. With appropriate diagram and waveform explain R-Firign circuit. What are the limitations of R-firing circuit. (10 Marks)
- 4 Define commutation of SCR. What are the different classes of forced commutation methods? Explain class B and C commutation methods with appropriate diagram and waveforms. (20 Marks)

PART – B

- 5 a. Explain the effect of freewheeling diode in details. Also, justify the statement “Free wheeling diode improves the power factor of the system” (10 Marks)
- b. Explain the operation of 3- ϕ , half wave controlled converter with resistive load, sketch the associated waveforms. (10 Marks)
- 6 a. Explain the Time Ratio Control [TRC] and Current Limit Control [CLC], and control strategies used for chopper. (10 Marks)
- b. A chopper, circuit is operating on TRC principle at a frequency of 2KHz on a 220V DC supply. If the load voltage is 170V, compute the conduction and blocking period of thyristor in each cycle. (10 Marks)
- 7 a. Explain the operation of 1 - ϕ bridge inverter with the help of voltage waveforms. Derive the expression for rms value of output voltage. (10 Marks)
- b. Explain the working of 3 - ϕ inverter with circuit diagram and waveforms. (180° mode of conduction). (10 Marks)
- 8 a. Describe the operation of single phase full-wave AC voltage regulator with the help of voltage and current waveforms. Also derive the expression for average value of output voltage. (10 Marks)
- b. A 1- ϕ half wave AC regulator feeds power to a resistive load of 6 Ω form 230V, 50Hz source. The firing angle of SCR is $\pi/2$. Calculate :
 - i) The RMS value of output voltage
 - ii) The input power factor pf
 - iii) The average input current. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.