

Reg. No.

--	--	--	--	--	--	--	--	--	--


Fourth Semester B.E. Degree Examination, January/February 2006
EC/TE/BM/ML/EE/IT
Power Electronics

Time: 3 hrs.)


(Max.Marks : 100)

- Note:** 1. Answer any FIVE full questions from the following.
2. All questions carry equal marks
3. Justify any assumptions made.

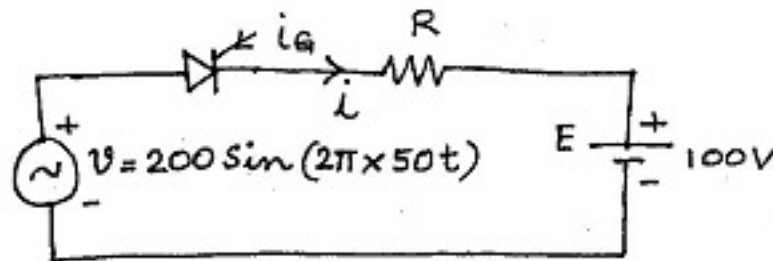
1. (a) What is a power converter? List the different types of power converters and mention their conversion functions. (7 Marks)
- (b) What are the peripheral effects of power electronic circuits? What are the remedies for them? (5 Marks)
- (c) The thyristor shown in the circuit of Fig Q. 1(c) is triggered by a dc signal applied to the gate. Calculate i) the average value of current i , ii) power loss in the resistor. (8 Marks)



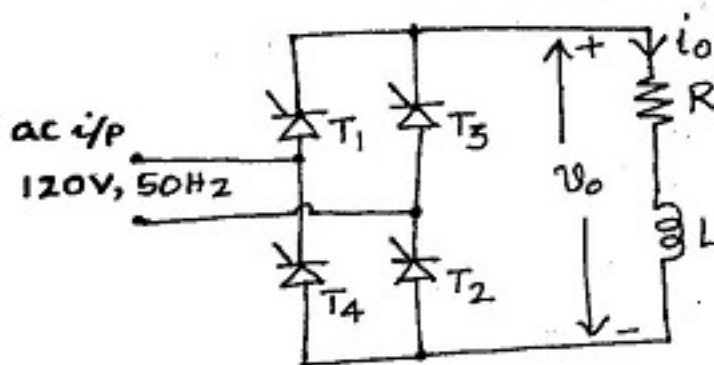2. (a) The single phase full converter shown in fig Q. 2(a) is operating from a 120V, 50Hz supply and provides an average load current of 5A at a delay angle of $\alpha = 30^\circ$. If the ripple content of the load current is negligible, calculate
 - i) dc load voltage and dc output power
 - ii) the quantities mentioned in (i) if a freewheeling diode is connected across the output for the same load resistance and delay angle and
 - iii) the dc load voltage and current if thyristor T_3 is open circuited. Assume same load resistance and firing angle and a freewheeling diode across the load. (10 Marks)




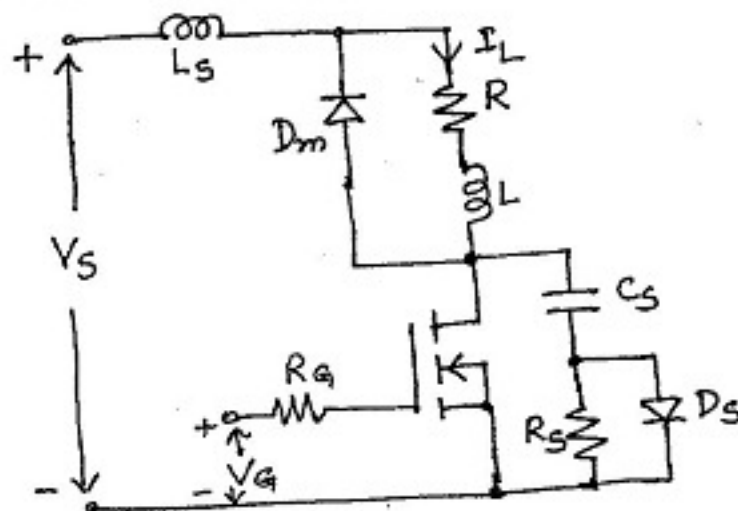- (b) Draw the circuit diagram of a single phase dual converter with RL load. Sketch the waveforms of input voltage, output voltage of converter 1, output voltage of converter 2 and voltage across the circulating inductor. Assume $\alpha = 60^\circ$. Mention any two advantages of circulating current mode of operation of dual converters. (10 Marks)
3. (a) Explain how antisaturation base control improves the switching performance of a BJT. (6 Marks)
- (b) With the help of switching waveforms explain the switching times of a power MOSFET. (7 Marks)
- (c) A MOSFET is operated as a chopper switch at a frequency of $f_s = 50 \text{ kHz}$. The circuit arrangement is shown in fig Q 3(c). The dc input voltage of the chopper is $V_s = 30 \text{ V}$ and the load current is $I_L = 40 \text{ A}$. The switching times are $t_r = 60 \text{ ns}$ and $t_f = 25 \text{ ns}$. Determine the values of i) L_s , ii) C_s , iii) R_s for critically damped condition and iv) R_s if peak discharge current is limited to 5% of load current. (7 Marks)



4. (a) Distinguish between :
- Latching current and holding current of a thyristor
 - Converter grade and inverter grade thyristors. (4 Marks)
- (b) Define turn-off time of thyristor and mention any two factors that affect it. (3 Marks)
- (c) Ten thyristors are used in a string to withstand a dc voltage of $V_s = 15 \text{ kV}$. The maximum leakage current and recovery charge differences of thyristors are 10 mA and $150 \mu\text{C}$ respectively. Each thyristor has a voltage sharing resistance of $R = 56 \text{ k}\Omega$ and capacitance of $C_1 = 0.5 \mu\text{F}$. Determine
- the maximum steady state voltage sharing $V_{DS}(\text{max})$,
 - the steady state voltage derating factor,
 - the maximum transient voltage sharing $V_{DT}(\text{max})$ and
 - The transient voltage derating factor. (8 Marks)
- (d) Briefly explain RC triggering circuit for full wave control. (5 Marks)
5. (a) What do you mean by commutation? What are the conditions to be satisfied for commutation of a thyristor? (4 Marks)

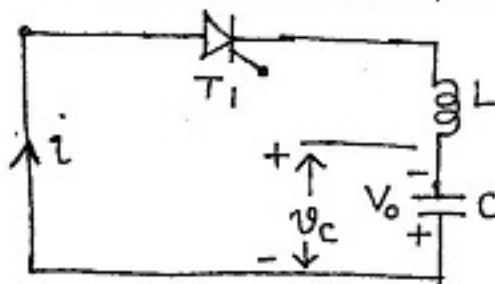- (b) In fig Q 5(b) the initial capacitor voltage $V_0 = 500V$, capacitance $C = 25\mu F$ and inductance $L = 10\mu H$. Determine the peak value of resonant current and the conduction time of thyristor T_1 . Derive the expressions used. (8 Marks)



- (c) With the help of a neat circuit diagram and relevant waveforms explain the operation of a complementary commutation circuit. (8 Marks)
6. (a) Mention the advantages and disadvantages of on-off control method of ac voltage control. (3 Marks)
- (b) A single phase full wave ac voltage controller using two thyristors in antiparallel has a resistive load of $R = 1.5\Omega$ and the input voltage is $120V(rms), 50Hz$. If the desired output power is $P_0 = 4.53kW$ determine
 i) the delay angles of the thyristors T_1 and T_2 ,
 ii) the rms output voltage and output current,
 iii) the input power factor, PF and
 iv) the rms current of each thyristor. (11 Marks)
- (c) Explain why short duration single gate pulses are not suitable for triggering thyristors in a full wave ac voltage controller with inductive loads. (6 Marks)
7. (a) With the help of a neat circuit diagram explain the principle of working of a step-down chopper. (6 Marks)
- (b) In a step-down chopper, the source voltage is $220V$ dc. The load circuit parameters are $R = 10\Omega$ and $L = 5mH$. If the chopper is operating at a frequency of $200Hz$ and the ON/OFF ratio of the chopper is $2 : 1$ calculate
 i) the average load current,
 ii) the maximum and minimum values of instantaneous load current under steady state conditions. (7 Marks)
- (c) Explain how the principle of step-up chopper can be used to transfer energy from a low voltage dc source to a high voltage dc source. (7 Marks)
8. (a) A single phase full bridge inverter has a resistive load of $R = 10\Omega$ and the dc input voltage is $V_s = 220V$. Calculate i) the rms output voltage at the fundamental frequency, V_1 , ii) the average rms and peak currents of each transistor switch, iii) the output power, P_0 and iv) the peak off-state voltage of each transistor, V_{BR} . (6 Marks)
- (b) Draw the circuit diagram of a three phase bridge inverter with wye connected resistive load. Sketch the gating signals and line to line output voltages for 180° conduction operation. (7 Marks)
- (c) With the help of neat waveforms explain the principle of multiple pulse width modulation method of output voltage control in a single phase inverter. Write the expression for the rms output voltage. (7 Marks)