

USN

--	--	--	--	--	--	--	--	--	--

NEW SCHEME

Fourth Semester B.E. Degree Examination, July 2007
EC / TE / EE / IT / ML / BM
Power Electronics

Time: 3 hrs.]

[Max. Marks:100

Note : Answer any FIVE full questions.

1.
 - a. Mention and explain the different types of power electronic converter systems. Draw their output / input characteristics. (08 Marks)
 - b. What are the peripheral effects of power converter system? (04 Marks)
 - c. What is the need of a base drive control in a power transistor? Explain proportional and anti saturation control. (08 Marks)

2.
 - a. With the necessary waveforms explain the switching characteristics of a power transistor. (07 Marks)
 - b. Give the comparison between SCR, MOSFET and IGBT. (06 Marks)
 - c. With the necessary sketches, explain the switching characteristics of an IGBT. (07 Marks)

3.
 - a. Sketch the static V-I characteristics of an SCR and then explain
 - i) Latching current.
 - ii) Holding current.
 - iii) Break over voltage. (08 Marks)
 - b. Explain the various methods of turn-on of an SCR and mention the advantages of gate triggering. (08 Marks)
 - c. The thyristor is gated with a pulse width of 40 μ sec. The latching current of thyristor is 36 mA. For a load of 60 Ω and 2H, will the thyristor get turned ON? If not, how it can be overcome for the given load? Find its value. (04 Marks)

4.
 - a. What do you mean by commutation? Explain briefly the different types of commutation. (08 Marks)
 - b. With necessary circuit and waveforms, explain complementary commutation scheme. (08 Marks)
 - c. The resonant pulse commutation circuit has a capacitance $C = 30 \mu\text{F}$ and $L = 4 \mu\text{H}$. The initial capacitor voltage is $V_0 = 200 \text{ V}$. Determine the circuit turn OFF time for the load current $I_m = 250 \text{ A}$. (04 Marks)

5.
 - a. What are the advantages of freewheeling diode? Explain the principle of operation of a single phase HWR feeding an RL load. Draw the necessary sketches. (08 Marks)
 - b. With the necessary circuit and waveforms, explain the operation of three-phase full converter. (08 Marks)
 - c. A single phase rectifier for 10 kW rating is required. Thyristor of current rating 50 A are to be used. Find the rated voltage of thyristor using a safety factor of 2, if the rectifier is
 - i) Full wave using centre tapped transformer.
 - ii) Full wave bridge rectifier.
 Assume RL load. (04 Marks)

- 6 a. Classify the choppers and explain the different types and chopper circuits. (08 Marks)
b. Obtain an expression for the output voltage for a step-up chopper. Explain how duty cycle is controlled. (08 Marks)
c. A dc chopper has an input voltage of 200 V and a load of 8Ω resistance. The voltage drop across thyristor is 2 V and the chopper frequency is 800 Hz. The duty cycle $\alpha = 0.4$. Find
i) Average output voltage.
ii) Rms output voltage.
iii) Chopper efficiency. (04 Marks)
- 7 a. With necessary circuit and waveforms, explain the operation and fullwave a.c. voltage controller feeding an RL load. (08 Marks)
b. Explain the various methods of gating an SCR. State why short duration pulses are insufficient for an ac voltage controller feeding an RL load. (06 Marks)
c. A single phase half wave ac voltage controller has an input voltage of 150 V and a load resistance of 8Ω . The firing angle of thyristor is 60° in each positive half cycle. Find
i) Average output voltage.
ii) RMS output voltage.
iii) Power output.
iv) Power input
v) Average input current over one cycle (06 Marks)
- 8 a. What do you mean by Inverters? Explain the operation of single phase full bridge inverter. Draw the load current waveforms for R, RL and RLC loads. (08 Marks)
b. With necessary circuit and waveforms, explain the operation of three phase bridge inverter with 180° mode of operation. (08 Marks)
c. Explain how harmonics can be reduced by transformer connections. (04 Marks)
