

NEW SCHEME

USN

--	--	--	--	--	--	--	--	--	--


Fourth Semester B.E. Degree Examination, July/August 2005
EC/TE/BM/ML/EE/IT
Power Electronics

Time: 3 hrs.]

[Max.Marks : 100


Note: 1) Answer any FIVE full questions.
 2) All questions carry equal marks

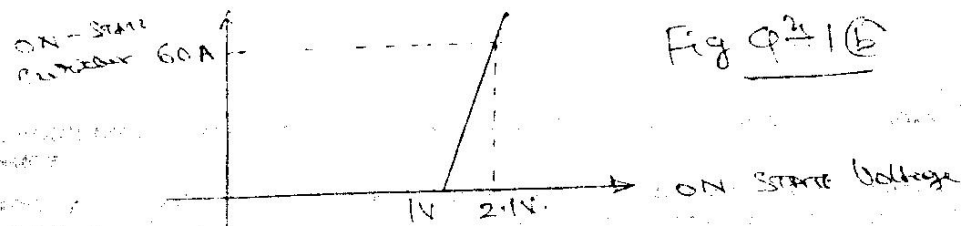1. (a) Explain the turn-on and turn off characteristics of the SCR. (8 Marks)
- (b) A thyristor has a forward characteristic which may be approximated by a straight line shown in the following figure. Calculate the mean power loss for
- i) a continuous on state current of 23 A.
 - ii) a half sine wave of mean value 18A
 - iii) A level current of 39.6A for one half cycle. (6 Marks)



- (c) The input voltage to circuit shown below is $V_s = 200\text{volts}$ with a load resistance of $R = 10\Omega$ and a load inductance of $L = 50\mu\text{H}$. If the damping ratio is 0.7 and discharging current of capacitor is 5A, determine :

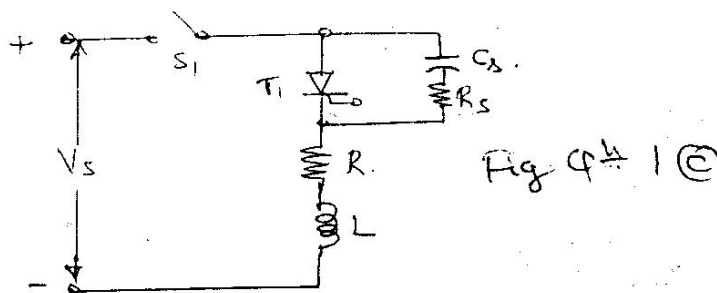
- i) the values of R_s & C_s
- ii) Maximum $\frac{dv}{dt}$ (6 Marks)



2. (a) List the different types of power electric circuits. (4 Marks)
- (b) Describe briefly the various base drive control methods used in Juverson transistors. (10 Marks)

- (c) In the circuit shown the BJT is acting as a chopper switch at a frequency of 15 KHz. $E_{DC} = 240V$ and load current is 100 Amps. The switching times are $t_d = 0$, $t_r = 1.5\mu sec$ and $t_f = 0.7\mu sec$. Calculate the values of
- L_s and C_s
 - R_s for critically damped conditions
 - R_s if the discharge current is limited to 5% of load current
 - Power loss due to snubber neglecting effect of inductor L_s on voltage of C_s . Assume that $V_{ce(sat)} = 0$. (6 Marks)

Fig Q2 ©

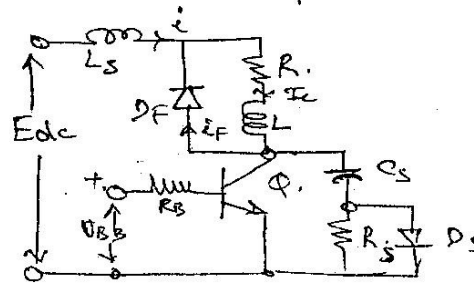

3. (a) Distinguish clearly between natural commutation and forced commutation. (8 Marks)
- (b) With the help of a neat diagram and associated waveforms, explain the operation of a complementary commutation circuit. Derive an expression for the turn-off time assuming a resistive load. (8 Marks)
- (c) For the commutation circuit shown in the following figure, $C = 20\mu F$ and $L_1 = 25\mu H$. The initial capacitor voltage is equal to input voltage i.e., $V_o = V_s = 200$ volts. If the load current I_m varies between 50A and 200 A, determine the variations in circuit turn-off. Derive any formulae you use. (10 Marks)


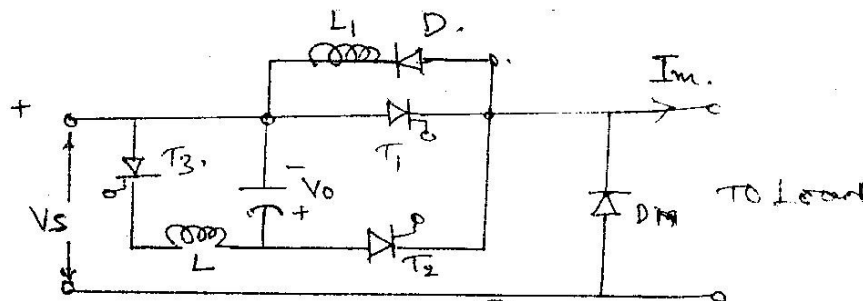


Fig Q3 ©

4. (a) Compare and contrast on-off control with phase control as applied to AC voltage controllers. (6 Marks)
- (b) A single phase half wave AC voltage controller shown in the following figure feeds power to a resistive load of 6Ω from 230V, 50Hz source. The firing angle of SCR is $\alpha = \frac{\pi}{2}$. Calculate :
- Rms value of output voltage
 - Input power factor
 - Average input current. Derive any formulae you use for atleast two subdivisions.

(10 Marks)

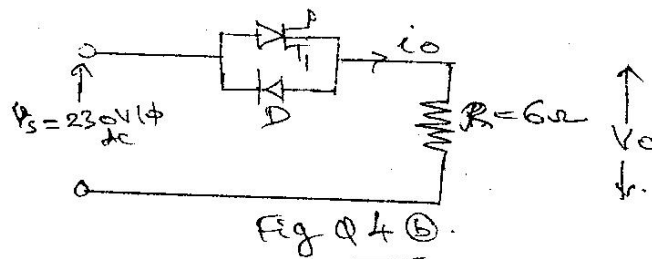

- (c) Explain why short duration pulses are not suitable for AC voltage controller with inductive loads. (4 Marks)
5. (a) A three phase fully controlled converter is operating with a highly inductive load. The load current is continuous and ripple free equal to I_o . Determine :
- Rms supply current
 - Displacement factor
 - Distortion factor
 - Power factor
 - Harmonic factor.
- (10 Marks)
- (b) A single phase half wave rectifier has a transformer secondary voltage of 230 volts, 50 Hz and supplies a purely resistive load of $R = 1\Omega$. If the average output voltage is 25% of the maximum possible value of DC output voltage. Calculate :
- Delay angle of thyristor
 - Rms and average value of output current
 - Rms and average value of thyristor current
 - Input power factor.
- (10 Marks)
6. (a) Explain in detail how choppers are classified. (10 Marks)
- (b) For an ideal type class A chopper circuit $V_s = 220\text{volts}$, $R = 5\Omega$, $L = 7.5\text{mH}$, $f = 1\text{KHz}$ and $E = 0$. Duty cycle $K = 0.5$. Calculate :
- I_{min} & I_{max}
 - ΔI i.e., peak to peak ripple current.
 - Average and Rms value of load current.
 - Effective input resistance of chopper.
 - Rms chopper current.
- (10 Marks)

7. (a) Define the performance parameter and inverters. (4 Marks)
- (b) With necessary waveforms explain the operation of a single phase half-bridge inverter. (10 Marks)
- (c) For a type A chopper circuit, $E_{dc} = 220V$, $f = 500Hz$. Duty cycle $k = 0.3$ and load $R = 1\Omega$, $L = 3mH$ and $E = 23$ Volts. Compare the following quantities.
- i) Check whether the conversion is continuous or not.
 - ii) Average o/p current
 - iii) I_{max} & I_{min} (6 Marks)
8. (a) With the help of a neat diagram and associated w/F's, explain the operation of a three phase inverter employing 120° conduction strategy. (10 Marks)
- (b) Explain :
- i) Phase displacement technique.
 - ii) Multiple pulse width modulation technique.
- used for controlling the output voltage of a single phase inverter. (10 Marks)

** * **