

--	--	--	--	--	--	--	--	--	--

Fourth Semester B.E. Degree Examination, June/July 08
Power Electronics

Time: 3 hrs.

Max. Marks:100

Note : Answer any FIVE questions choosing at least TWO questions from each part.

Part A

1.
 - a. List the different types of power electronic circuits and converter circuits and their applications. (06 Marks)
 - b. Plot the input and output characteristics of any four power semiconductor devices. (08 Marks)
 - c. What are the advantages of static power converters? Mention the peripheral effects of such static power converters. (06 Marks)

2.
 - a. Explain how antisaturation base control improves the switching performance of a BJT. (06 Marks)
 - b. With the help of switching waveforms explain the switching times of a power MOSFET. (07 Marks)
 - c. A transistor switch of figure Q2 (c) has β in the range of 8 to 40. Calculate i) The value of R_B that results in saturation with an overdrive factor of 5. ii) The forced β_f and iii) The power loss in the BJT. (07 Marks)

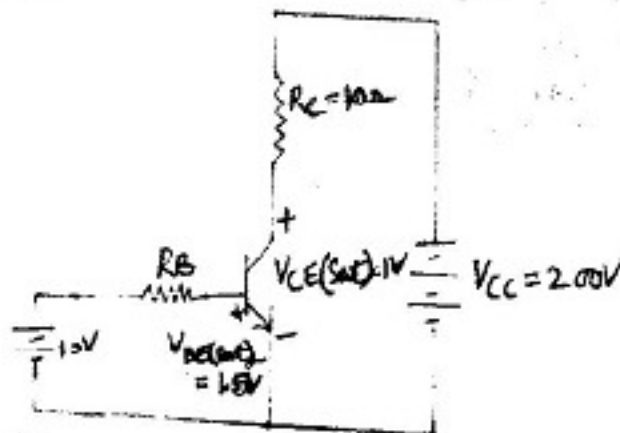


Fig. Q2 (c)

3.
 - a. Explain the principle of operation of an SCR using two transistor model. (06 Marks)
 - b. What is the need for protection of thyristors? Explain how thyristors are protected against high $\frac{di}{dt}$ and high $\frac{dv}{dt}$. (07 Marks)
 - c. Sketch the static V-I characteristics of an SCR and explain i) Latching current ii) Holding current and iii) Break over voltage. (07 Marks)

4.
 - a. Discuss the process of thyristor commutation and differentiate between i) Natural and forced commutation. ii) Self and impulse commutation. (12 Marks)
 - b. The resonant pulse commutation circuit has a capacitance $C = 30 \mu F$ and $L = 4 \mu H$. The initial capacitor voltage is $V_c = 200V$. Determine the circuit turn off time for the load current $I_m = 250A$. (08 Marks)

Part B

- 5 a. With a circuit diagram and waveforms of gating pulses and output voltage, explain the operation of 1- ϕ ON-OFF type ac voltage controller. Derive an expression for $V_{o(rms)}$.
(10 Marks)
- b. With necessary waveforms explain the operation of 1- ϕ full wave controller with inductive load. Derive expressions for rms output voltage and rms output current. (10 Marks)
- 6 a. Explain the working of 1- ϕ semi converter with the help of waveforms for resistive load and inductive loads. (10 Marks)
- b. With circuit diagram, explain the operation of a 3 ϕ full converter for constant load current. If the input to this circuit is 3 ϕ , 50 Hz, ac supply, determine the firing angle, α , for the SCRS to obtain an output average dc voltage of 50% of the maximum. If this output voltage is 270 volts, calculate ac supply line to line rms voltage. (10 Marks)
- 7 a. Explain in detail how choppers are classified. (10 Marks)
- b. A chopper is feeding an R-L load as shown in the figure Q7 (b), $V_s = 220V$, $R=5\Omega$, $L = 7.5\text{ mH}$, $f = 1\text{ kHz}$, $\delta = 0.5$ and $E = 0$ volts. Calculate
- Minimum instantaneous load current, I_{min}
 - Peak instantaneous load current I_{max} .
 - Maximum peak to peak load ripple current.
 - Average value of load current.
 - rms load current $I_{o(rms)}$.
 - Effective input resistance R_i .
 - rms chopper current, $I_T(rms)$.
- (10 Marks)

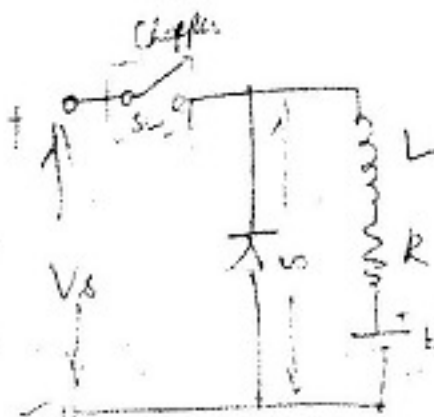


Fig. Q7 (b)

- 8 a. With necessary waveforms explain the operation of a single phase half bridge inverter. (10 Marks)
- b. Draw the circuit diagram of a three phase bridge inverter with Y connected resistive load. Sketch the gating signals and line to line output voltages for 180° conduction operation. (10 Marks)