

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

Fourth Semester B.E. Degree Examination, June/July 2014
Power Electronics

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting
atleast TWO questions from each part.**

PART – A

- 1 a. Mention and explain the different types of power electronic converter systems and also specify the form of input and output with wave forms. **(12 Marks)**
- b. With neat sketch explain the operation of H.V.D.C power transmission systems. **(08 Marks)**
- 2 a. With necessary waveforms explain the switching characteristics of an I.G.B.T. **(10 Marks)**
- b. In the bipolar transistor circuit shown in Fig.Q.2(b), β varies between 10 to 60. The load resistance $R_C = 5\Omega$, $V_{CC} = 100V$, $U_{BB} = 8V$, if $V_{CE(sat)} = 2.5V$ and $V_{BE(sat)} = 1.75V$, calculate:
 - i) The value of R_B that results in saturation with an overdrive factor of 20; ii) The forced β value; iii) Power loss in the transistor. **(10 Marks)**

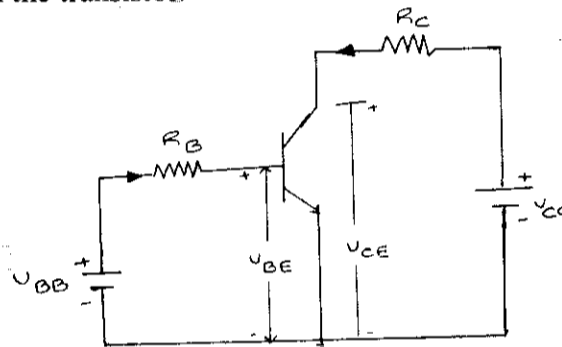


Fig.Q.2(b)

- 3 a. With the help of two transistor model derive an expression for the anode current of a thyristor. **(08 Marks)**
- b. For the circuit shown in Fig.Q.3(b) if the latching current is 4mA, calculate the minimum width of gate pulse required to properly turn on the SCR. **(04 Marks)**

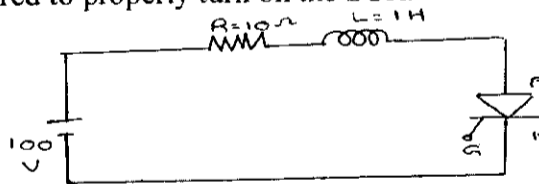


Fig.Q.3(b)

- c. With circuit diagram and wave forms explain the working of U.J.T. triggering technique of SCR. **(08 Marks)**
- 4 a. With circuit diagram and wave forms explain the resonant pulse commutation. **(12 Marks)**

- b. Circuit of Fig.Q.4(b) employing class C commutation has $V_S = 200V$, $R_1 = 10\Omega$ and $R_2 = 100\Omega$. Calculate: i) Peak value of current through thyristor T_1 ; ii) The value of capacitor C if each thyristor has turn off time of $40 \mu\text{ sec}$. Consider factor of safety as 2; iii) Sketch the thyristors voltage wave forms for one complete cycle. (08 Marks)

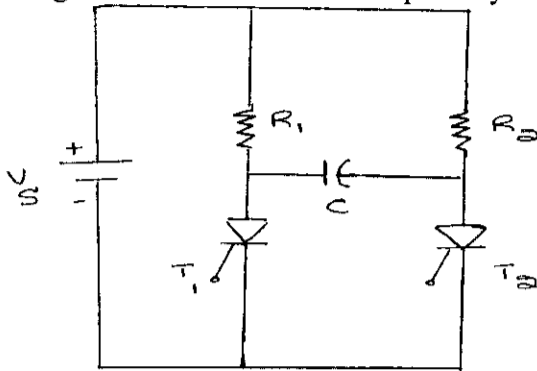


Fig.Q.4(b)

PART - B

- 5 a. With circuit diagram and wave forms explain the operation of a three phase full wave controlled rectifier with resistive load. And also derive the equation for average value of output voltage. (12 Marks)
- b. A single phase half wave controlled rectifier supplies a purely resistive load of 10Ω , from a $230V$, 50Hz supply. If the average output voltage is 75% of the maximum possible value of the d.c. output voltage. Calculate: i) Delay angle of thyristors; ii) R.M.S. value of output voltage; iii) RMS value of output current; iv) The input power factor. (08 Marks)
- 6 a. With circuit diagram and quadrant operation, explain four quadrant choppers. (10 Marks)
- b. In the circuit shown in Fig.Q.6(b) the supply voltage is $240V$. The voltage drop across the switch when it is on is $V_s = 1.5V$. If the load resistance is $R = 15\Omega$, $f = 1.2 \text{ KHZ}$ and duty cycle is 60%. Calculate: i) The average d.c. output voltage; ii) the r.m.s. output voltage; iii) The chopper efficiency; iii) The input resistance of the chopper. (10 Marks)

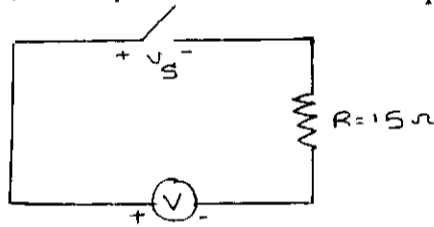


Fig.Q.6(b)

- 7 a. With circuit diagram and wave forms explain the operation of a single phase full bridge inverter supplying a resistive load. (10 Marks)
- b. Explain any two modulation techniques available for voltage control a single phase inverter. (10 Marks)
- 8 a. With circuit diagram and wave forms explain the operation of a bidirectional controller with RL load. (10 Marks)
- b. A single phase full wave a.c. voltage controller has an input voltage of $230V$ and a load resistance of 10Ω . The firing angle is 90° . Calculate: i) RMS output voltage; ii) RMS output current; iii) Output power; iv) The input power factor; v) Average thyristor current. (10 Marks)
