

**Fourth Semester B.E. Degree Examination, June/July 2015**  
**Power Electronics**

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions, selecting  
atleast TWO questions from each part.**

**PART – A**

- 1 a. With a neat circuit and waveforms of control signal and output voltage, explain the control characteristics of IGBT and SCR. (08 Marks)
- b. Explain briefly the different types of thyristor power converter and mention two applications of each and also specify the form of input and output waveforms. (12 Marks)
- 2 a. Sketch the structure of n-channel enhancement type MOSFET and explain its working principle. Also draw its transfer characteristics. (07 Marks)
- b. Sketch and explain the switching characteristics of power BJT. The sketch should have the waveform i)  $V_{BE}$  ii)  $I_B$  and iii)  $I_C$ . (06 Marks)
- c. The IGBT shown in the circuit of Fig.Q.2(c) has the following data:  
 $t_{on} = 3\mu\text{sec}$ ,  $t_{off} = 1.2\mu\text{sec}$ . Duty cycle  $D = 0.7$ ,  $V_{ce(sat)} = 2V$ ,  $f_s = 1\text{kHz}$ . Determine:
  - i) Average load current.
  - ii) Conduction power loss.
  - iii) Switching power loss during turn-on and turn off. (07 Marks)

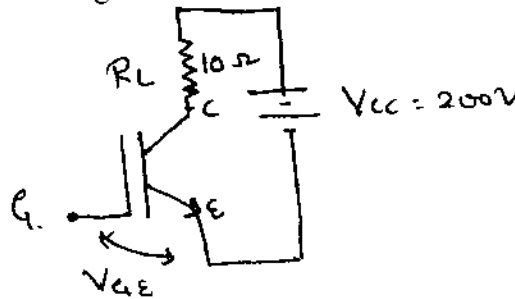


Fig.Q.2(c)

- 3 a. Using two transistor analogy, derive an expression for anode current of SCR. (06 Marks)
- b. The SCR in Fig.Q.3(b) is used to control power in resistance R. The supply is 400V, and the maximum allowable  $di/dt$  and  $dv/dt$  the SCR are  $50\text{ A}/\mu\text{sec}$  and  $200\text{ V}/\mu\text{sec}$  respectively. Compute the values of the  $di/dt$  inductor and the snubber circuit components  $R_s$  and  $C_s$ . (06 Marks)

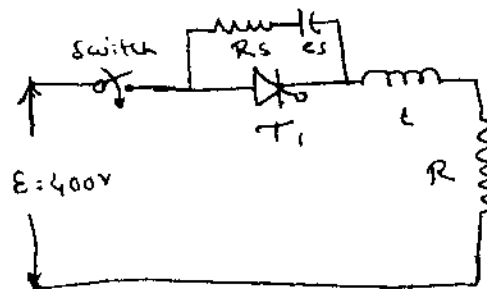


Fig.Q.3(b)

- c. Mention and explain the various methods of turn-on used in thyristors. (08 Marks)

- 4 a. State the conditions to be satisfied for proper turn-off of SCR. (02 Marks)  
 b. With the help of circuit diagram and waveforms explain the operation of self commutation. (08 Marks)  
 c. In the Fig.Q.4(c) the source voltage  $V_s = 100V$  and the current through  $R_1$  and  $R_2$  is 25A. The turn-off time of both the SCRS is 40  $\mu$ sec. Find the value of capacitor for successful commutation and hence show that circuit turn off time is 0.693 RC. (10 Marks)

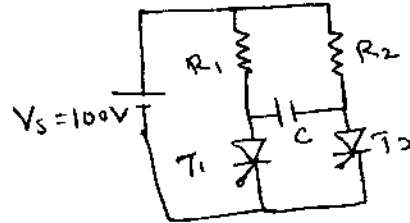


Fig.Q.4(c)

## PART – B

- 5 a. With neat circuit and waveform derive an expression for the RMS value of output voltage of single phase semi converter with R.L. load (Assume discontinuous load current). (06 Marks)  
 b. A single phase half wave controlled rectifier is used to supply power to  $10\Omega$  load from 230V, 50Hz supply at a firing angle of  $30^\circ$ . Calculate: i) Average output voltage; ii) Effective output voltage; iii) Average load current. (06 Marks)  
 c. With neat circuit and waveforms explain the working principle of 3- $\phi$  half wave controlled rectifier with R load. (08 Marks)
- 6 a. What is a chopper? How are choppers classified? Give the quadrant of operation and one application of each type. (08 Marks)  
 b. With the help of a circuit schematic describe principle of step-up chopper. Obtain the expression for average output voltage in terms of duty ratio. (06 Marks)  
 c. A DC chopper has a resistive load of  $20\Omega$  and input voltage.  $V_s = 220V$ . When the chopper is on, its voltage drop is 1.5V and chopping frequency is 10kHz, if duty cycle is 80%. Determine the average output voltage, rms output voltage  $\alpha$  chopper on time. (06 Marks)
- 7 a. With the help of neat diagram and waveform explain the operation of  $180^\circ$  mode of 3- $\phi$  inverter with star connected R-load. (10 Marks)  
 b. Explain the principle of operation of a single phase full bridge inverter with suitable circuit diagram and waveform. (10 Marks)
- 8 a. Distinguish between on-off control and phase control of AC voltage controller. (04 Marks)  
 b. Explain the operation of single phase bidirectional AC voltage controller for resistive load with the help of circuit diagram and waveforms. (06 Marks)  
 c. An AC voltage controller has a resistive load of  $R = 10\Omega$  and rms input voltage is  $V_s = 120V$ , 60Hz. The thyristor switch is on for  $n = 25$  cycles and off for  $m = 75$  cycles. Determine:  
 i) The rms output voltage.  
 ii) Input power factor.  
 iii) Average and rms current of thyristors. (10 Marks)

\*\*\*\*\*