

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Fourth Semester B.E. Degree Examination, Dec.2013/Jan.2014
Transformers and Induction Machines

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting
at least TWO questions from each part.**

PART – A

- 1 a. With the vector diagram, explain operation of practical transformer under no-load and load. (08 Marks)
- b. Write a note on 1- ϕ core type transformer. (05 Marks)
- c. A 50 KVA, 1- ϕ transformer has 500 – turns on the primary and 100-turns on the secondary. The primary is connected to 250volts, 50Hz supply. Calculate the following neglecting losses:
- The secondary voltage on open circuit.
 - Currents flowing through the windings.
 - Maximum value of flux.
 - If the transformer 50A to a load, what is its impedance. (07 Marks)

- 2 a. Derive the condition for maximum efficiency of a transformer. (05 Marks)
- b. Explain the sumpner's test for testing two 1- ϕ transformer. Also explain why this is beneficial for finding efficiency of transformer. (08 Marks)
- c. Find the all day efficiency of 500KVA distribution transformer whose copper loss and iron loss at full load are 4.5 kW and 3.5 kW respectively. During a day, it is loaded as under.

Number of hours	6	10	4	4
Loading in kW	400	300	100	0
Power factor	0.8	0.75	0.8	-

- 3 a. Deduce expression for the load shared by two transformers in parallel when no-load voltages of these transformers are equal. (06 Marks)
- b. Explain the working principles and construction of constant current transformer. (07 Marks)
- c. Derive an expression for the saving of copper in autotransformer as compared to an equivalent two winding transformer. (07 Marks)

- 4 a. With the help of connection diagram and phasor diagram, explain how a two phase supply can be obtained from a three-phase supply. (08 Marks)
- b. Discuss the conditions that must be satisfied to operate two 3-phase transformer in parallel. (06 Marks)
- c. A balanced 3- ϕ load of 30 KVA, at a p.f. of 0.866 lagging is connected to two transformers connected in open-delta to a five 230V, three-phase system. Find the power delivered by each transformer. (06 Marks)

PART – B

- 5 a. What are the advantages of skewed slots in the rotor of squirrel cage induction motor? (04 Marks)
- b. Show that a rotating magnetic field can be produced by the use of 3- ϕ currents of equal magnitude. (08 Marks)
- c. Draw the complete torque-slip characteristics of a 3- ϕ I.M. indicating all the regions and explain. (08 Marks)

- 6 a. Explain the phenomenon of cogging and crowling in a 3- ϕ induction motor. (08 Marks)
 b. A 415 volts, 40HP, 50Hz, Δ -connected motor gave the following test data:

No-load test	415V, 21A, 1250 Watt
Locked rotor test	100V, 45A, 2730 Watt

Construct the circle diagram and determine:

- i) The line current and power factor for rated output.
 ii) The maximum torque. (12 Marks)
 Assume stator and rotor copper losses are equal at stand still.
- 7 a. With a neat sketch, explain the working of a double-cage induction motor. Draw its equivalent circuit. (10 Marks)
 b. Explain the working operation of induction generator, with a neat sketch. (10 Marks)
- 8 a. What is the necessity of starter for a 3- ϕ I.M? Explain the star-delta (Y- Δ) starter. (07 Marks)
 b. Why 1- ϕ I.M is not self starting? Explain the working operation of 1- ϕ capacitor start and run induction motor. (07 Marks)
 c. Explain any two methods of speed control of three-phase cage type motors. (06 Marks)

* * * * *