

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

15NT44

## Fourth Semester B.E. Degree Examination, June/July 2019 Electronic Instruments and Measurements

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. With the help neat diagram, explain the transistor voltmeter. (06 Marks)
- b. Write a note on multirange voltmeter and explain how the range of a voltmeter can be extended to measure high voltages. (06 Marks)
- c. What is meant by error? Explain the types of errors. (04 Marks)

OR

- 2 a. Explain in detail about RF ammeter, its types and limitations. (08 Marks)
- b. Explain multirange ammeters with the help of circuit diagrams. (04 Marks)
- c. Write a note on probability of errors. (04 Marks)

### Module-2

- 3 a. Explain RAMP technique mention the advantages and disadvantages. (08 Marks)
- b. Write a note on continuous balance DVM. (04 Marks)
- c. Explain digital P<sup>H</sup> meter. (04 Marks)

OR

- 4 a. Describe the working of universal counter. (06 Marks)
- b. With diagram, explain the working of Digital multimeter. (06 Marks)
- c. Write a note on ADC. (04 Marks)

### Module-3

- 5 a. Discuss about standard signal generator with the help of Diagram. (08 Marks)
- b. With block diagram, explain the working of Oscilloscope. (08 Marks)

OR

- 6 a. With diagram, explain the principle and working of function generator. (08 Marks)
- b. Discuss about different types of probes for CRO. (06 Marks)
- c. Write the circuit diagram of vertical amplifier in CRO. (02 Marks)

### Module-4

- 7 a. Explain the principle and working of stroboscope. (08 Marks)
- b. Discuss about Q-meter and state its advantages. (08 Marks)

OR

- 8 a. With circuit diagram, explain the principle and working of vector impedance meter. (08 Marks)
- b. Write a note on Megger. (06 Marks)
- c. Write the circuit diagram of Wheatstone's bridge. (02 Marks)

### Module-5

- 9 a. With neat diagram, explain the working of LVDT and mention the advantages and limitations. (08 Marks)
- b. Explain the working of photo transistor with the help of diagrams. (06 Marks)
- c. Mention two types of electrical transducers. (02 Marks)

OR

- 10 a. Write a detailed note on inductive transducers. (08 Marks)
- b. Write a note on Photovoltaic cell. (04 Marks)
- c. Explain optical transducer. (04 Marks)

\*\*\*\*\*

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.