

CRASH COURSE

USN

--	--	--	--	--	--	--	--	--	--

10EC56

Fifth Semester B.E. Degree Examination, May 2017 Fundamentals of CMOS VLSI

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, selecting atleast TWO questions from each part.

PART – A

- 1 a. Explain with neat sketches of NMOS fabrication. (10 Marks)
b. Derive the expression for V_{out} at region C of CMOS inverter characteristic plot (05 Marks)
c. What is latch up phenomenon? (05 Marks)
- 2 a. Draw the schematic, stick and layout of CMOS NAND gate. (08 Marks)
b. Explain the design rules with neat diagrams for diffusion, metal and transistor. (07 Marks)
c. What are the different types of contacts? Explain. (05 Marks)
- 3 a. Explain pseudo NMOS logic, dynamic CMOS and clocked CMOS logic. (15 Marks)
b. Explain 2 input XNOR gate in pass transistor logic. (05 Marks)
- 4 a. Derive the expression for delay (τ) in terms of sheet resistance and area capacitance for NMOS inverter and CMOS inverter circuit. (10 Marks)
b. Find the scaling factors for following MOS circuits : (i) Gate capacitance (ii) Gate delay (iii) Saturation current (iv) Current density (v) Power dissipation. (10 Marks)

PART – B

- 5 a. Explain the structured design of a parity generator with necessary blocks and stick diagrams. (10 Marks)
b. Explain 4 bit shift register (non inverting) using NMOS logic. (10 Marks)
- 6 a. Design a 4 bit adder to implement addition, subtraction, XOR, XNOR, OR and AND operations. (08 Marks)
b. Draw the basic form of a 2 phase clock generator and explain. (06 Marks)
c. What are the system timing considerations in system design? (06 Marks)
- 7 a. Explain 3 transistor dynamic RAM cell. (06 Marks)
b. Explain Braun array multiplier with a neat diagram. (06 Marks)
c. What are the ground rules required for successful design? (08 Marks)
- 8 Write short notes on:
a. Transmission gate.
b. BiCMOS logic.
c. Input output pads.
d. BIST. (20 Marks)

* * * * *

Important Note: 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank space.
2. Any remaining or unutilized space, appear to evaluator and/or equations written e.g. 4+3=8-20, will be treated as inappropriate.