

Fifth Semester B.E. Degree Examination, December 2011
Fundamental of CMOS VLSI

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting at least TWO questions from each part.

PART – A

- 1 a. Explain the nMOS enhancement mode transistor for different conditions of v_{ds} . (08 Marks)
 b. Describe in detail BiCMOS fabrication in an n-well process. (08 Marks)
 c. What are the advantages of BiCMOS process over CMOS technology? (04 Marks)
- 2 a. What is body effect? Which parameters are responsible for it? (08 Marks)
 b. An nMOS transistor is operating in active region with following parameters $V_{GS} = 3.9V$, $V_{th} = 1V$, $\frac{W}{L} = 100$, $\mu_n c_{ox} = 90 \mu A/r^2$. Find I_D and drain to source resistance. (05 Marks)
 c. Explain in detail regions of operation and mid-point voltage equation for CMOS inverter. (07 Marks)
- 3 a. List the λ -based design rules for CMOS. (05 Marks)
 b. Draw the stick diagram for nMOS EX-OR gate. (07 Marks)
 c. What is transmission gate? And design stick diagram for transmission gate. (08 Marks)
- 4 a. What is clocked CMOS gate? Where it is preferred? (06 Marks)
 b. Two nMOS inverters are cascaded to drive capacitive load $C_L = 16 C_g$ as shown in Fig.Q.4(b). Calculate pair delay v_{in} to v_{out} interms of τ . (06 Marks)

 


Fig.Q.4(b)

- c. Find the scaling factors for MOS circuits :
 i) For gate capacitance ; ii) Channel resistance (R_{on})
 ii) Saturation current (I_{dss}) ; iv) Speed power product (PT). (08 Marks)

PART – B

- 5 a. Design bus arbitration logic for n-line bus. (10 Marks)
 b. Explain two-phase clocking generator using D flip – flops. (10 Marks)
- 6 a. Explain the design steps for 4 bit adder. (08 Marks)
 b. Draw the basic arrangements of 4 bit serial parallel multiplier. (08 Marks)
 c. Discuss the timing constraints for system timing considerations. (04 Marks)
- 7 a. For single phase clock define following parameters :
 i) Set up time (T_s) ; ii) Hold time (T_n) ; iii) Clock to Q delay (T_q). (03 Marks)
 b. How to read or write and hold the bit in SRAM cell? (09 Marks)
 c. Explain the working of 1-transistor DRAM cell. Give the difference between SRAM and DRAM. (08 Marks)
- 8 a. Discuss the meaning of “REAL ESTATE” in VLSI design. (04 Marks)
 b. What are the different types of I/O pads? (06 Marks)
 c. List the ground rules for a system design. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

