

Fifth Semester B.E. Degree Examination, December 2012
Fundamentals of CMOS VLSI

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART – A

- 1 a. Explain the nMOS fabrication process with neat diagram. (10 Marks)
- b. Obtain the dc transfer characteristics of a CMOS inverter and mark all the region showing the status of PMOS and NMOS. (10 Marks)
- 2 a. Compare CMOS and bipolar technologies. (04 Marks)
- b. Draw the circuit schematic and stick diagram of CMOS 2 input NAND gate. (06 Marks)
- c. Draw the layout for the schematic shown in the Fig.Q.2(c). (10 Marks)

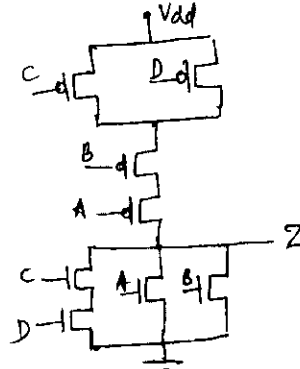


Fig.Q.2(c)

- 3 a. Explain the operation of CMOS dynamic logic. Also discuss the cascading problem of dynamic CMOS logic. (10 Marks)
- b. Realize $Z = A(B + C) + DE$ for clocked CMOS logic. (05 Marks)
- c. Find the equation for the node voltages V_1, V_2, V_3 during logic "1" transfer, when each pass transistor is driving another pass transistor, as shown in Fig.Q.3(c). Assume threshold voltage of each transistor is V_{th} . (05 Marks)

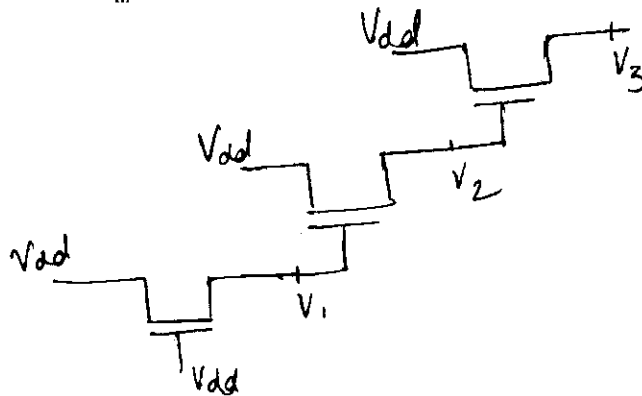


Fig.Q.3(c)

- 4 a. Find the scaling factors for:
i) Channel Resistance R_{on} (06 Marks)
ii) Current density J . (08 Marks)
b. Derive the equation for rise time and fall time for CMOS inverter. (06 Marks)
c. Write a note on limitations of scaling. (08 Marks)

PART – B

- 5 a. Explain structured design of bus arbitration logic for n-line bus. (10 Marks)
b. Explain dynamic 4-bit shift register using CMOS logic. (10 Marks)
- 6 a. Design 4-bit ALU to implement addition, subtraction, EXOR, EXNOR, OR and AND operations. (10 Marks)
b. With the neat diagram, explain Braun array multiplier. (10 Marks)
- 7 a. Explain the working of three-transistor dynamic RAM cell. (06 Marks)
b. Explain one transistor dynamic memory cell with schematic and stick diagram. (06 Marks)
c. Discuss CMOS pseudo-static memory cell with stick diagram. (08 Marks)
- 8 a. Explain sensitized path-based testing for combinational logic. (10 Marks)
b. Write a note on ground rules for successful design. (10 Marks)

* * * * *