

--	--	--	--	--	--	--	--	--	--

Fifth Semester B.E. Degree Examination, Dec. 2013 / Jan 2014.
Fundamentals of CMOS VLSI


Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting atleast TWO questions from each part.

PART - A


- 1 a. Explain the fabrication steps of CMOS P – well process with neat diagram and write the mask sequence. (12 Marks)
 b. List the threshold voltage equations and emphasize each term. (08 Marks)
- 2 a. Write the CMOS inverter circuit and briefly explain. Write the CMOS VTC showing regions A, B, C, D, E. Derive the expressions for output voltage in region 'B'. (10 Marks)
 b. Write the circuit and layout for $Y = \overline{AB + CD + E}$ in CMOS style. (10 Marks)
- 3 a. Write the circuit and stick diagram for CMOS tristate inverter. (04 Marks)
 b. Write the circuit of Bi CMOS NAND and NOR gate and briefly explain. (08 Marks)
 c. Explain the circuit of dynamic CMOS logic by taking an example of the function $Y = \overline{A(B + C) + DE}$. (08 Marks)
- 4 a. Define Sheet Resistance (R_s) and standard unit of capacitance ($\square C_g$). Calculate the on resistance of 4:1 nmos inverter with $R_s = 10k\Omega$, $Z_{pu} = \frac{8\lambda}{2\lambda}$, $Z_{pd} = \frac{2\lambda}{2\lambda}$. Also estimate the total power dissipated if $V_{DD} = 5V$. (08 Marks)
 b. Calculate the capacitance in $\square C_g$ for the given metal layer shown in fig.Q4(b), if feature size = $5\mu m$ and relative value of metal to substrate = 0.075. (05 Marks)

 

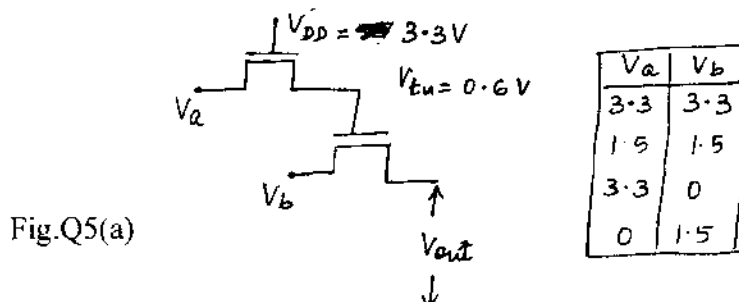- c. Explain briefly the circuit of inverting and non – inverting super buffer. (07 Marks)

PART - B

- 5 a. Calculate the O/P voltage V_{out} in the circuit given below for different values of V_a, V_b . (04 Marks)



Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42.8.50, will be treated as malpractice.

- b. Design Bus Arbitration logic for n – line bus. (10 Marks)
- c. Consider λ – based design rules and $5\mu\text{m}$ technology. How many nmos 8:1 inverter $\left(Z_{pu} = \frac{16\lambda}{2\lambda} \text{ and } Z_{pd} = \frac{2\lambda}{2\lambda} \right)$ can be driven by a minimum size conductor which is 3λ wide and $1\mu\text{m}$ thick? Assume $J_{th} = 1\text{mA}/(\mu\text{m})^2$, $R_s = 10\text{K}\Omega / \square$, $V_{DD} = 5\text{V}$. (06 Marks)
- 6 a. Discuss the 4 phase clocking scheme to avoid the problem of cascading in dynamic CMOS logic. (06 Marks)
- b. What are the adder enhancement techniques? Briefly explain. (04 Marks)
- c. Write and explain 6 – bit carry select adder. (10 Marks)
- 7 a. Write and explain 4 Transistor dynamic and 6 Transistor static CMOS memory cell with sense amplifier. (12 Marks)
- b. Explain the one transistor dynamic memory cell emphasizing three plate capacitor. (08 Marks)
- 8 Write short notes on :
- a. Latch up. (07 Marks)
- b. Nature of failures in CMOS. (06 Marks)
- c. I/O pads. (07 Marks)
