

**Fifth Semester B.E. Degree Examination, Dec.2016/Jan.2017**

**Fundamentals of CMOS VLSI**

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting at least TWO questions from each part.**

**PART – A**

- 1 a. Explain the action of enhancement mode transistor for different values of  $V_{gs}$  and  $V_{ds}$ . (08 Marks)
- b. Explain the second order effects viz.
  - (i) Fowler Nordheim Tunneling.
  - (ii) Drain punch through.
  - (iii) Impact ionization. (06 Marks)
- c. Describe in detail CMOS fabrication in an P-well process. (06 Marks)
- 2 a. Draw schematic, stick diagram, layout for nMOS 2-input NOR gate, where 4 : 1 ratio for pull up and 1 : 1 ratio for each pull-down. Specify  $\lambda$ -based rules for layout. (12 Marks)
- b. Provide the  $\lambda$ -based design rules for transistors, contact cuts and vias. (08 Marks)
- 3 a. Realize 2-input NAND gate as example in,
  - (i) BiCMOS logic.
  - (ii) Pseudo-nMOS logic.
 Discuss merits and demerits. (10 Marks)
- b. Explain the dynamic CMOS logic with example. List the problems and solution for issues. (10 Marks)
- 4 a. What are the scaling factor for:
  - (i) Gate capacitance
  - (ii) Maximum operating frequency
  - (iii) Current density
  - (iv) Power speed product. (10 Marks)
- b. Define sheet resistance and standard unit of capacitance  $\square Cg$ . Calculate the ON resistance for NMOS inverter with  $R_{SN} = 10 \text{ K}\Omega$ ,  $Z_{PU} = 4$  and  $Z_{pd} = 1$ ,  $V = 5 \text{ V}$ . And calculate power dissipation. (10 Marks)

**PART – B**

- 5 a. Design a parity generator, where output is 1 for even number of one's and draw the stick diagram for one basic cell. (10 Marks)
- b. In the circuit shown in Fig. Q5 (b). Find  $V_1, V_2, V_3, V_4$ . Assume threshold voltage of each transistor is  $V_{tn}$ . (04 Marks)

 


Fig. Q5 (b)

- c. Draw the basic form of a 2- $\phi$  clock generator and explain. (06 Marks)

- 6** a. Discuss the architectural issues to be followed in the design of a VLSI sub-system. **(06 Marks)**  
b. Realize a  $4 \times 4$  barrel shifter using MOS switches and explain in brief. **(06 Marks)**  
c. Explain carry skip adder. **(08 Marks)**
- 7** a. Discuss the various system timing consideration. **(04 Marks)**  
b. Explain the 3T DRAM cell with stick diagram. **(10 Marks)**  
c. Describe the CMOS pseudo-static RAM circuit. **(06 Marks)**
- 8** a. Explain different types of Input/Output pads. **(05 Marks)**  
b. List the ground rules for a system design. **(05 Marks)**  
c. Write a note on Built-in self test. **(05 Marks)**  
d. Write a note on BiCMOS logic with neat circuit. **(05 Marks)**

\* \* \* \* \*