

--	--	--	--	--	--	--	--	--	--

Fifth Semester B.E. Degree Examination, June/July 2013
Fundamental of CMOS VLSI

Time: 3 hrs.

Max. Marks:100

Note: 1. Answer FIVE full questions, selecting at least TWO questions from each part.
2. Missing data may be assumed suitably.

PART - A

- 1 a. Explain briefly the nMOS enhancement mode transistor action with neat sketches. (06 Marks)
 b. With the help of cross-sectional schematic, explain the various steps involved in n-well CMOS fabrication process. (08 Marks)
 c. Define noise margin. Calculate the noise margins for the transfer characteristic of typical inverter, shown in Fig.Q.1(c). (06 Marks)

 


Fig.Q.1(c)

- 2 a. Explain briefly the circuit operation of a basic differential inverter and a Tristate inverter. (06 Marks)
 b. Draw the circuit diagram, mono chrome stick diagram and mask layout of p-well CMOS inverter. (08 Marks)
 c. Distinguish buried and butting contacts with suitable diagrams. (06 Marks)
- 3 a. Draw the circuit diagram and monochrome stick diagram for two input CMOS NOR gate. (06 Marks)
 b. What do you mean by pre-charge and evaluate modes in CMOS dynamic logic? Explain. (06 Marks)
 c. What are single rail and dual rail networks? Explain how cascade voltage switch logic (CVSL) may be used to obtain dual-rail logic gates. (08 Marks)
- 4 a. Calculate the area capacitance values associated with the following structure, having different layers as shown in Fig.Q.4(a) (relative 'C' value for polysilicon-to-substrate = $0.1 \text{ pf} \times 10^{-4}/\mu\text{m}^2$ and metal 1-to-substrate = $0.075 \text{ pf} \times 10^{-4}/\mu\text{m}^2$). (06 Marks)

 


Fig.Q.4(a)

- b. Prove how the delay associated with CMOS inverter pair is independent of input transitions. (06 Marks)
- c. Write the scale factors for the following parameters:
- Gate capacitance (C_g)
 - Maximum operating frequency (f_0)
 - Current density (J)
 - Power speed product (P_T). (08 Marks)

PART – B

- 5 a. Discuss the architectural issues in the design of VLSI sub system. (06 Marks)
- b. Implement a 4-way multiplexer using nMOS switches. (06 Marks)
- c. Explain structured design approach for a parity generator. (08 Marks)
- 6 a. Realize a 4×4 barrel shifter using MOS switches and explain in brief its salient features. (06 Marks)
- b. Explain the various steps involved in designing a 4-bit adder. (08 Marks)
- c. Discuss on a serial-parallel multiplier approach used in adder. (06 Marks)
- 7 a. What are the system timing considerations? Explain. (06 Marks)
- b. Explain the circuit operation of a three-transistor dynamic RAM cell. (07 Marks)
- c. Show the functioning of a pseudo-static memory cell. (07 Marks)
- 8 Write short notes on the following:
- Input output pads.
 - Controllability and observability.
 - Boundary scan test (BST).
 - Built-in-self-test (BIST). (20 Marks)

* * * * *