

USN

--	--	--	--	--	--	--	--	--	--

10EC56

Fifth Semester B.E. Degree Examination, June/July 2018
Fundamentals of CMOS VLSI

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART – A

- 1 a. Briefly explain the speed / power performance of different technologies. (04 Marks)
 b. Explain the different steps required for nMOS fabrication process. (10 Marks)
 c. What is noise margin? Explain CMOS inverter noise margins. (06 Marks)
- 2 a. Explain λ based design rules applicable to wires and contacts. (10 Marks)
 b. Write the stick diagram and layout for the Fig. Q2 (b). (05 Marks)

 


Fig. Q2 (b)

- c. Write the layout for two input CMOS NAND gate. (05 Marks)
- 3 Explain the following logic structures with their salient features:

(i) Pseudo nMOS logic	(ii) Dynamic CMOS logic
(iii) Clocked CMOS logic	(iv) CMOS domino logic

 (20 Marks)
- 4 a. Define sheet resistance and standard unit of capacitance. (02 Marks)
 b. Explain propagation delays with respect to pass transistor chain and long polysilicon wires. (08 Marks)
 c. Explain scaling factors as applicable to MOS device parameters. (10 Marks)

PART – B

- 5 a. Explain the concept of basic inverting dynamic storage cells and non inverting dynamic storage cells. (05 Marks)
 b. Briefly explain the basic form of two phase clock generator circuit. (05 Marks)
 c. Explain bus arbitration logic for n-line bus. (10 Marks)
- 6 a. Explain the concept of carry look ahead adder and represent the 4 bit block CLA unit. (10 Marks)
 b. Discuss Baugh Wooley method used for two's complement multiplication. (10 Marks)
- 7 a. What are the timing considerations in system design? (06 Marks)
 b. Explain the read and write operation of a three transistor dynamic RAM memory cell. (06 Marks)
 c. Explain decoder based selection and control of the 4×4 bit register array. (08 Marks)
- 8 a. Explain input / output pads and represent the 4 bit processor pad utilization. (10 Marks)
 b. With the help of example, explain sensitized path based testing a combinational logic. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.