

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

15EC53

Fifth Semester B.E. Degree Examination, Dec.2019/Jan.2020

Verilog HDL

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Explain the advantages of HDL's over schematic-based design. (06 Marks)
b. Explain top-down design methodology and bottom-up design methodology. (10 Marks)

OR

- 2 a. Discuss the trends in HDLs. (06 Marks)
b. Explain the design hierarchy using 4-bit ripple carry counter. (10 Marks)

Module-2

- 3 a. Explain the following data types with an example in verilog:
i) Vectors ii) Registers iii) Time iv) Real. (08 Marks)
b. What are system tasks and compiler directives? Explain. (08 Marks)

OR

- 4 a. What are the components of SR-latch? Write verilog HDL module of SR-latch. (08 Marks)
b. With an example, explain Hierarchical names. (08 Marks)

Module-3

- 5 a. With the help of logic diagram, write a verilog code for 4 to 1 multiplexer using gate – level modeling. (08 Marks)
b. What are rise, fall and turn-off delays? Explain, how they are specified in verilog. (08 Marks)

OR

- 6 a. Explain conditional and concatenation operator with an example. (06 Marks)
b. Write a verilog dataflow description for 4-bit full adder with carry lookahead. (10 Marks)

Module-4

- 7 a. Explain briefly event based timing control in verilog. (08 Marks)
b. Explain sequential and parallel blocks of verilog HDL. (08 Marks)

OR

- 8 a. Write a verilog HDL code for JK flip-flop using case statement. (08 Marks)
b. With syntax, explain conditional and branching loop statements in verilog HDL. (08 Marks)

Module-5

- 9 a. Explain the advantages and benefits of VHDL. (06 Marks)
b. Write a VHDL code for full-adder using two half adder in mixed style description. (10 Marks)

OR

- 10 a. Explain the synthesis process with a block diagram. (10 Marks)
b. Differentiate between signal assignment and variable assignment. (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.