

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18EC56

Fifth Semester B.E. Degree Examination, June/July 2023

Verilog HDL

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Explain typical design flow for designing VLSI IC circuits with a neat flow chart. (10 Marks)
- b. Explain top-down design methodology and bottom-up design methodology. (06 Marks)
- c. Explain trends in HDL's. (04 Marks)

OR

- 2 a. Explain design hierarchy by taking 4-bit ripple carry counter. (08 Marks)
- b. Define the following terms with examples "
i) Module
ii) Instances
iii) Instance name. (06 Marks)
- c. Explain the different levels of abstraction used for programming in verilog. (06 Marks)

Module-2

- 3 a. With a neat block diagram, explain the components of verilog module. (08 Marks)
- b. Explain \$display, \$monitor, \$finish and \$stop system tasks with examples. (08 Marks)
- c. How to write comments in verilog HDL, explain with examples. (04 Marks)

OR

- 4 a. Explain the following data types of with an examples :
i) Nets
ii) Registers
iii) Integers
iv) Parameters. (08 Marks)
- b. Write verilog description of SR latch. Also write stimulus code. (08 Marks)
- c. With an example, explain hierarchical names. (04 Marks)

Module-3

- 5 a. What are Rise, Fall and Turn-off delays? How they are specified in verilog. (06 Marks)
- b. Write a verilog dataflow level of abstraction for 4 to 1 multiplexer using conditional operator. Also write stimulus code. (08 Marks)
- c. Design a gate level module according to the logic diagram given Fig.Q5(c). Write stimulus code delay. (06 Marks)

 


Fig.Q5(c)

1 of 2

(06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

OR

- 6 a. Develop a gate-level verilog code for 4-bit ripple carry adder from 1-bit full adder. What is the output if $A = 1010$, $B = 1100$ and $c_{in} = 0$ at $t = 0$. (10 Marks)
- b. What would be the output of the following :
 $a = 4'b0111$, $b = 4'b1001$
- $\&b$
 - $a \ll 2$
 - $\{a, b\}$
 - $\{2\{b\}\}$
 - $a \wedge b$
 - $a|b$
 - $a \& b$
 - $\sim a$. (08 Marks)
- c. Declare following variables in Verilog,
- A 8-bit vector called a – in (02 Marks)
 - An integer called count.

Module-4

- 7 a. Discuss sequential and parallel blocks with examples. (08 Marks)
- b. Write a verilog behavioral description of 8 : 1 multiplexer using case statement. (06 Marks)
- c. Illustrate the use while loop and repeat loop with examples. (06 Marks)

OR

- 8 a. Explain blocking and non-blocking assignment statements with relevant examples. (08 Marks)
- b. Write verilog behavioral description of 4-bit binary counter. (06 Marks)
- c. Write the verilog behavioral description of Dflip – flap. (06 Marks)

Module-5

- 9 a. Define the term logic synthesis. With a neat flow-chart explain computer – Aided logic synthesis process. (10 Marks)
- b. What will the following statement translate to when run on a logic synthesis tool,
- $assign\ y = (a\&b) | (c\&b)$ where y, a, b, c and d are 3 – bit vectors
 - if(s)
 $out = i1 ;$
else
 $out = i0 ;$ (10 Marks)

OR

- 10 a. With neat flow diagram explain synthesis design flow. (10 Marks)
- b. Write a notes on :
- Assign and deassign
 - Overriding parameters. (10 Marks)
