

USN

--	--	--	--	--	--	--	--	--	--

NEW SCHEME

Fifth Semester B.E. Degree Examination, Dec. 06 / Jan. 07
Electrical and Electronics Engineering
Operational Amplifier and Linear IC's

Time: 3 hrs.]

[Max. Marks:100

- Note: 1. Answer any FIVE full questions.**
2. Missing data may be suitably assumed.
3. Use of Op-amp data sheets is permitted.

1. a. Define the following electrical parameters for an op-amp:
 i) Input off-set voltage ii) Input resistance iii) Output voltage swing iv) CMRR. (08 Marks)
 b. What information does transfer curve reveal about op-amp? (04 Marks)
 c. Sketch the circuit of a capacitor-coupled voltage follower. Explain the design procedure. (08 Marks)
2. a. Define: i) Loop phase shift ii) Loop gain iii) Open-loop-gain iv) Closed loop gain for a feed back system. (08 Marks)
 b. What is frequency compensation? Explain phase lag or phase lead compensation method. (08 Marks)
 c. List the precautions that should be observed for op-amp circuit stability. (04 Marks)
3. a. The maximum output voltages of each of the voltage comparators shown in fig.3(a) are ± 15 V. Sketch the output waveforms for each when V_{in} is a 10 V peak sine wave. In each case show V_{in} and V_o and label voltage levels where switching occurs. (06 Marks)

 


Fig.3(a)

- b. Sketch and explain the working of sample and hold circuit. (06 Marks)
- c. Name the op-amp circuit shown in fig.3(c) and explain its working and sketch its transfer curve. (08 Marks)

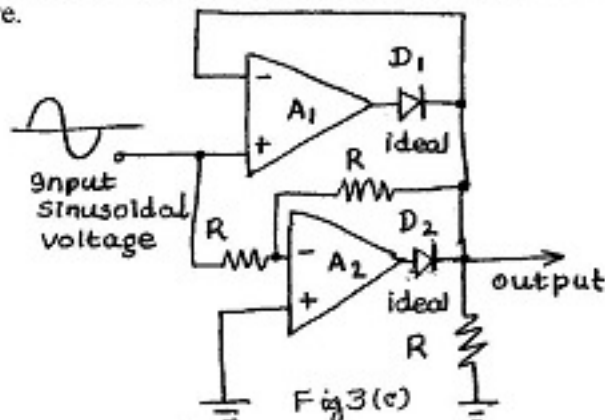


Fig.3(c)

Contd.... 2

- 4 a. Referring to fig.4(a) sketch the output and transfer curve for the given op-amp clipper circuits. Take $V_{in} = 8 \sin \omega t$ volts. (12 Marks)

 


Fig.4(a)

- b. Sketch positive clamper circuit using op-amp and explain its operation. (08 Marks)
- 5 a. Sketch the circuitry of an astable multivibrator using op-amp and sketch the relevant waveforms. (10 Marks)
- b. The output of the Schmitt trigger shown in fig.5(b) switches between +10 V and -10 V.
- i) Find the lower and upper trigger levels ii) Find hysteresis iii) Sketch the hysteresis loop iv) Sketch the output when V_{in} is a 10 V peak sine wave. (10 Marks)

 


Fig 5(b)

- 6 a. Define an oscillator and what are the two requirements for oscillation. (03 Marks)
- b. Sketch Wein Bridge oscillator circuit and derive expression for the:
i) frequency of the waveform generated and ii) gain required for sustaining oscillations. (12 Marks)
- c. Sketch the output of an integrator shown in fig.6(c) on the graph sheet. Take $R_1 = 1 \text{ K}$, $C = 0.1 \mu\text{F}$. (05 Marks)

 


Fig.6(c)

- 7 a. Derive expression for gain and phase angle of first order low pass Butterworth filter. (08 Marks)
- b. What is a phase - locked loop? Explain the working of building blocks of PLL. (08 Marks)
- c. What is a dc voltage regulator? Define: i) line regulation ii) load regulation. (04 Marks)
- 8 a. Sketch the circuit of a voltage follower regulator. Explain its operation. (06 Marks)
- b. Sketch the basic circuit of 723 voltage regulator and explain the regulator action. (10 Marks)
- c. Differentiate small signal amplifiers and power amplifiers. (04 Marks)