

|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|

**Fifth Semester B.E. Degree Examination, Dec. 07 / Jan. 08**

**Operational Amplifiers and Linear IC's**

Time: 3 hrs.

Max. Marks:100

**Note :** 1. *Answer any FIVE full questions.*

2. *Missing data may be suitably assumed.*

3. *Use of resistor, Capacitor standard values list and Op-amp data sheets is permitted.*

1.
  - a. Sketch the circuit of a capacitor – coupled non – inverting amplifier using single polarity supply and explain it briefly. Also draw the waveforms at input, before and after the output coupling capacitor. (08 Marks)
  - b. A high input impedance capacitor-coupled non-inverting amplifier is to be designed to have  $A_v = 120$  and  $f_1 = 100$  Hz. The input signal is 50 mV and the total resistance ranges from 2.7 k $\Omega$  to 27 k $\Omega$ . Design a suitable circuit using a 741 op-amp. (08 Marks)
  - c. Explain briefly the working of notch filter with relevant diagrams. (04 Marks)
  
2.
  - a. Discuss the effects of stray capacitance on op-amp circuit stability. Write the equations to determine the value of input stray capacitance that might produce circuit instability. (08 Marks)
  - b. What are the causes of circuit instability? List the precautions to be taken for circuit stability. (08 Marks)
  - c. Calculate the minimum rise time and maximum undistorted output pulse amplitude at that rise time for an amplifier with closed loop gain 50, using a 741 op-amp. (04 Marks)
  
3.
  - a. Draw an op-amp sample-and-hold circuit. Sketch the signal, control, and output voltage waveform. Explain the circuit operation. (07 Marks)
  - b. A 3.3 kHz,  $\pm 2$  V square wave with a 600  $\Omega$  source resistance is to have its negative peak clamped at ground level. Using a bipolar op-amp, design a suitable precision clamping circuit. The tilt on the output is not to exceed 2 percent. (06 Marks)
  - c. Sketch a precision rectifier peak detector circuit, draw the input and output waveforms and explain the circuit operation. Write the expression for calculating the capacitor value and op-amp minimum slew rate. (07 Marks)
  
4.
  - a. Draw the circuit of an op-amp monostable multivibrator. Show the relevant voltage waveforms and explain its operation. (06 Marks)
  - b. Using a 741 op-amp with a supply of  $\pm 12$ V, design an inverting Schmitt trigger circuit to have trigger points of  $\pm 2$ V. (06 Marks)
  - c. Sketch the circuit of capacitor-coupled zero-crossing detector. Show the waveforms at various points in the circuit and explain its operation. (08 Marks)
  
5.
  - a. Sketch the circuit of a triangular / rectangular waveform generator. Draw the output waveforms at different stages and explain the circuit operation. (09 Marks)
  - b. Using a 741 op-amp with a supply of  $\pm 12$ V, design a phase shift oscillator to have an output frequency of 500 Hz. (05 Marks)
  - c. Draw the circuit of a Wein bridge oscillator. Sketch the output and feedback voltage waveforms and explain the circuit operation. (06 Marks)

- 6 a. Draw the circuit of a first order high-pass filter and derive an expression for gain magnitude and phase angle. (06 Marks)
- b. Design a wideband-reject filter using first order highpass and lowpass filters having  $f_L = 2$  kHz and  $f_H = 400$  Hz respectively with pass band gain as 2. (08 Marks)
- c. Discuss the differences between wideband and narrowband band pass filters. Sketch typical frequency responses for each. Explain the terms – figure of merit, centre frequency and band width with respect to band pass filters. (06 Marks)
- 7 a. Explain with a block diagram the operation of a phase locked loop. Enlist the applications of phase locked loop. (08 Marks)
- b. Distinguish clearly between small signal amplifiers and power amplifiers. (04 Marks)
- c. Briefly explain the theory of operation of switched capacitor filter. What are the advantages of switched capacitor filters? (08 Marks)
- 8 a. Explain the terms line regulation, load regulation and ripple rejection for a dc voltage regulator. (06 Marks)
- b. Explain with a circuit diagram, the operation of a voltage follower regulator. (06 Marks)
- c. Explain with a schematic diagram LM217 integrated circuit positive voltage regulator. Calculate the resistance of R1 and R2 for the LM217 voltage regulator to produce an output voltage of 9 volts. (08 Marks)

\*\*\*\*\*