

USN

--	--	--	--	--	--	--	--	--	--

NEW SCHEME

Fifth Semester B.E. Degree Examination, July 2007
Electrical and Electronics
Operational Amplifiers and Linear IC's

Time: 3 hrs.]

[Max. Marks:100

*Note : 1. Answer any FIVE full questions.**2. Use of register and capacitor standard values list and Op-Amp data sheets are permitted.*

- 1
 - a. With a neat circuit diagram, explain the operation of a high Z_{in} capacitor coupled non-inverting amplifier circuit. Justify the practical values. (08 Marks)
 - b. Discuss the effects of input and output capacitors used in capacitor coupled amplifiers. (06 Marks)
 - c. Design a capacitor coupled voltage follower using a 741 Op-Amp. The lower cut-off frequency of the circuit is to be 115 Hz. The load resistance R_L is 6.8 k Ω . (06 Marks)

- 2
 - a. List the precautions that should be observed for Op-Amp circuit stability. (08 Marks)
 - b. Show how feedback in a non-inverting amplifier circuit can produce instability. Define i) Frequency compensation ii) Loop gain iii) Loop phase shift. (06 Marks)
 - c. Calculate the slew rate limited cut-off frequency for a voltage follower circuit using 741 Op-Amp. The peak of the sine wave output is to be 5V. The slew rate of Op-Amp is 0.5V/ μ sec. Determine the maximum peak value of the sinusoidal output voltage that will allow the voltage follower circuit to operate at 500 kHz unity gain cut-off frequency. (06 Marks)

- 3
 - a. With a neat circuit diagram and block diagram show how a half wave precision rectifier can be combined with a summing circuit to produce a fullwave precision rectifier. Draw the voltage waveforms at relevant stages of the circuit and write equations to show that full wave rectification is performed. (08 Marks)
 - b. Explain the operations of an adjustable peak clipper circuit with back-to-back connected zener diodes. Write the equations with $V_o(\max) = \pm 4V$. (06 Marks)
 - c. A 5 kHz, $\pm 5V$ square wave with 100 Ω source resistance is to have its negative peak clamped at ground level. Using a bipolar Op-Amp design a suitable precision clamping circuit. The tilt on the output is not to exceed 2.5%. (06 Marks)

- 4
 - a. Draw circuits to show how diodes may be used to select the trigger points upper and lower for an inverting Schmitt trigger circuit. Explain the operation and draw the output / input characteristic. (06 Marks)
 - b. Draw the circuit of an Op-Amp mono stable multi vibrator. Show the relevant voltage waveforms and explain its operation. (08 Marks)
 - c. A capacitor coupled zero crossing detector is to provide an output voltage of approximately $\pm 15V$, when a 5kHz, $\pm 3V$ square wave input is applied. Design a suitable circuit to use a bipolar Op-Amp. Tilt at the non inverting terminal ΔV is to be 0.75V. (06 Marks)

Contd...2

- 5 a. State Barkhausen criteria and explain how it is fulfilled in the phase shift oscillator. (06 Marks)
- b. Design a triangle / rectangular waveform generator to have an output frequency of 5kHz. The triangle output amplitude of $\pm 6V$ and square wave output amplitude of approximately $\pm 10V$. Use bipolar Op-Amp and estimate a minimum suitable Op-Amp slew rate. (08 Marks)
- c. Draw the circuit of an output stage for controlling the output amplitude and dc voltage level of a signal generator. Explain the operation. (06 Marks)
- 6 a. Draw the circuits of a second-order low pass and second-order high pass active filters. Sketch the frequency response for each circuit and briefly explain the operation of each filter. (12 Marks)
- b. Design a second-order low pass active filter to have a cut-off frequency of 3.3 kHz. Use 741 Op-Amp. (08 Marks)
- 7 a. With a neat circuit diagram explain the operation of a precision voltage regulator. (08 Marks)
- b. Explain the following performance parameters of a voltage regulator i) Line regulation ii) Load regulation iii) Ripple rejection. (06 Marks)
- c. Explain the operation and applications of a phase locked loop circuit. (06 Marks)
- 8 Write explanatory notes with relevant circuit diagrams and waveforms, wherever applicable:
- a. Explain the significance of upper cut-off frequency of an Op-Amp and show how the cut-off frequency can be set for inverting amplifier.
- b. Operation of a sample and hold circuit.
- c. Universal active filter.
- d. Peak detector. (20 Marks)
