

--	--	--	--	--	--	--	--	--	--

Fifth Semester B.E. Degree Examination, June / July 08
Operational Amplifier and Linear IC's

Time: 3 hrs.

Max. Marks:100

Note : 1. Answer any FIVE full questions.

2. Use of resistor and capacitor standard values list and OPamp data sheets are permitted.

3. Missing data may be suitably assumed.

1.
 - a. With a circuit diagram, explain the operation of a high Input – Impedance capacitor – coupled non – inverting amplifier. (08 Marks)
 - b. A capacitor – coupled inverting amplifier has the following components ; $R_1 = 2.7 \text{ k}\Omega$, $R_2 = 100\text{k}\Omega$, $R_L = 1.5 \text{ k}\Omega$, $C_1 = 3.9\mu\text{F}$, $C_2 = 0.68\mu\text{F}$. Determine the circuit voltage gain, lower cut – off frequency and impedance of C_1 at f_1 . Draw the circuit and insert the given values. (06 Marks)
 - c. With a neat circuit diagram, show how a capacitor – coupled voltage follower should be used with a single polarity supply. Briefly explain the circuit operation. (06 Marks)
2.
 - a. What are the effects of Load capacitance on Op-Amp circuit stability? Give the methods of compensating for the load capacitance effect. (08 Marks)
 - b. What are the effects of slew – rate on Band – width, out – put pulse rise time and output amplitude? (06 Marks)
 - c. List the precautions that should be observed for operational Amplifier circuit stability. Briefly explain. (06 Marks)
3.
 - a. With a neat diagram, show how a half – wave precision rectifier can be combined with summing circuit to produce a full wave precision rectifier. Draw the voltage waveforms and justify with equations how full wave rectification is performed. (10 Marks)
 - b. Design a non – saturating precision half wave rectifier using a bi-polar OP-Amp with supply voltage of $\pm 20\text{V}$, to produce a 3V peak output. The input signal has a 1V peak amplitude and a frequency of 50 kHz. (05 Marks)
 - c. With a neat diagram, explain a clamping circuit using an Op-Amp. (05 Marks)
4.
 - a. Draw an OP-Amp non – inverting Schmitt trigger circuit and explain its operation. Also explain how trigger points can be adjusted. (10 Marks)
 - b. Using a bi-polar OP-Amp, design an inverting Schmitt trigger circuit to trigger at $\pm 0.5\text{V}$ and produce an output of approximately $\pm 11\text{V}$. (05 Marks)
 - c. With a neat circuit diagram and wave forms explain the operation and design procedures for an astable multivibrator. (05 Marks)
5.
 - a. With a neat circuit diagram, explain the operation of Triangular/Rectangular waveform generator. Explain how frequency and duty – cycle can be controlled in the circuit. (12 Marks)
 - b. Using 741 OP-Amp, with a supply of $\pm 9\text{V}$, design an RC – phase shift oscillator to have output frequency of 10 kHz. Draw the circuit and insert the values. (08 Marks)

- 6 a. What is the difference between wide band and narrow – band pass filters? Draw the circuit diagrams and typical frequency responses for each. Briefly explain. (10 Marks)
- b. Design a low –pass filter at a cut-off frequency of 1kHz with a pass band gain of 2. Using frequency scaling convert 1kHz cut-off frequency of low – pass filter to a cut – off frequency of 1.6 kHz. (10 Marks)
- 7 a. Explain with a block diagram, Universal active filter. How can it be realized as a second order Low pass, High pass and Band pass filter? (10 Marks)
- b. With a neat sketch, explain the basic circuit of 723 integrated circuit DC – voltage regulator. Show how it can be used as positive voltage regulator. (10 Marks)
- 8 Write short notes on:
- a. Voltage follower regulator.
- b. Phase Locked Loop
- c. Wein bridge oscillator with oscillator amplitude stabilization
- d. Peak detectors. (20 Marks)
