

CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

15EE53

Fifth Semester B.E. Degree Examination, Dec.2017/Jan.2018 Power Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. With the help of circuit diagram, input and output waveforms explain working of different types of power electronic converters. (08 Marks)
- b. The reverse recovery time of a diode is $5\mu\text{s}$ and rate of fall of diode current is $80\text{A}/\mu\text{s}$. Calculate : i) the storage charge Q_{RR} ii) Peak reverse current I_{RR} . (04 Marks)
- c. List the parameters on which the performance of rectifier is evaluated. (04 Marks)

OR

- 2 a. Briefly explain different types of power diodes. (06 Marks)
- b. Explain the peripheral effects of power electronic equipments. (06 Marks)
- c. The bridge rectifier has an AC source with $V_m = 100\text{V}$ at 60Hz and a series load (RL) with $R = 10\Omega$ and $L = 10\text{mH}$. Calculate :
i) Average current in the load
ii) Average currents in the diodes. (04 Marks)

Module-2

- 3 a. Explain the switching characteristics of MOSFET. (05 Marks)
- b. Explain the anti-saturation control of BJT. (05 Marks)
- c. The β of bipolar transistor varies from 12 to 75. The load resistance is 1.5Ω . The supply voltage $V_{CC} = 40\text{V}$ and base input voltage is 6V . If $V_{CE(\text{sat})} = 1.2\text{V}$, $V_{BE(\text{sat})} = 1.6\text{V}$ and $R_B = 0.7\Omega$, calculate : i) ODF ii) Forced β iii) total power loss in transistor. (06 Marks)

OR

- 4 a. List and explain the switching limits of power BJT. (08 Marks)
- b. The base drive circuit of anti-saturation control has supply voltage 400V , collector resistance 4Ω , $V_{d1} = 3.6\text{V}$, $V_{d2} = 0.9\text{V}$, $V_{BE(\text{sat})} = 0.7\text{V}$. The voltage to the base circuit is 15V . $R_B = 1.1\Omega$ and $\beta = 12$. Find : i) Collector current without clamping ii) collector clamping voltage V_{CE} and ii) Collector current with clamping. (08 Marks)

Module-3

- 5 a. Explain the V-I characteristics of SCR. Also define : i) holding current and ii) Latching current. (06 Marks)
- b. Explain different methods of turning on of thyristor. (06 Marks)
- c. For the SCR shown in Fig.Q5(c), has a latching current of 20mA and is fired by a pulse width of 50 μ s. Determine whether the SCR turns on or not and comment on the result obtained. (04 Marks)

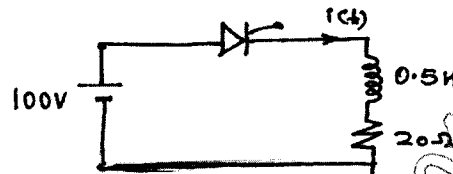


Fig.Q5(c)

OR

- 6 a. With the help of two transistor model, derive an expression for anode current of a thyristor and explain why gate loses its control over the device once thyristor is turned on. (08 Marks)
- b. A string of SCRs are connected in series to withstand a DC voltage of 15KV. The maximum leakage current and recovery charge difference of thyristor are 10mA and 150 μ C respectively. A derating factor of 20% is applied for steady state and transient state voltage sharing's of thyristors. If the maximum steady state voltage sharing is 1000V. Calculate : i) steady state voltage sharing resistance R for each thyristor ii) transient voltage capacitance C_1 and iii) string efficiency. (08 Marks)

Module-4

- 7 a. With the help of circuit diagram and waveforms, explain the working of single – phase full converter with R-L load. (08 Marks)
- b. A single –phase full wave AC voltage controller has an input voltage of 150V (rms) and a load of 8 Ω . The firing angle of thyristor is 60°. Find : i) average output voltage ii) rms output voltage iii) output power and iv) input P.F. (08 Marks)

OR

- 8 a. Explain the working of single – phase full wave AC voltage controller with resistive load. Draw relevant circuit, waveforms. Derive an expression for rms output voltage. (08 Marks)
- b. A single – phase circulating current dual converter is fed by 230V, 50Hz supply. The load is resistive. The peak current of converter 1 is 39.7A. The firing angles are 45° and 135° respectively. If peak – circulating current is 11.5A, Find : i) inductance of current limiting reactor ii) load resistance. (08 Marks)

Module-5

- 9 a. Explain the working of step-up chopper. Draw the relevant waveforms. Derive an expression for average output voltage. (06 Marks)
- b. A step-down chopper has an input voltage of 200V and a load of 8 Ω resistance. The voltage drop across thyristor is 2V and the chopping frequency is 800Hz. The duty cycle is 0.4. Find : i) average output voltage ii) rms output voltage iii) chopper efficiency. (06 Marks)
- c. Briefly explain the factors that influence the performance of inverter. (04 Marks)

OR

- 10 a. Explain the voltage control of single –phase inverter using : i) multiple pulse width modulation ii) sinusoidal pulse width modulation. (08 Marks)
- b. With the help of circuit diagram, explain the operation of different types of choppers. (08 Marks)