

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

21EE54

Fifth Semester B.E. Degree Examination, Dec.2023/Jan.2024

Power Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. With neat diagram, explain the different types of power electronic circuits. (10 Marks)
b. List the applications of power electronics. (06 Marks)
c. Write short notes on peripheral effects of power electronic circuits. (04 Marks)

OR

- 2 a. Explain the reverse recovery characteristics of diode. (07 Marks)
b. The reverse recovery time of a diode is $t_{rr} = 3 \mu s$ and the rate of fall of the diode current is $\frac{di}{dt} = 30 \frac{A}{\mu s}$. Determine the (i) Storage charge QRR (ii) Peak reverse current I_{RR} . (03 Marks)
c. With neat circuit diagram and waveform, explain the single phase full wave bridge type diode rectifier with R load, derive average and RMS output voltage. (10 Marks)

Module-2

- 3 a. Explain the switching characteristics of MOSFET. (10 Marks)
b. Write short notes on switching limits of BJT. (06 Marks)
c. List the applications of BJT, MOSFET, IGBT. (04 Marks)

OR

- 4 a. Explain the isolation of Gate and Base drives with the help of,
(i) Pulse transformer.
(ii) Opto coupler. (12 Marks)
b. Explain with neat diagram, Anti saturation control of BJT using collector clamping circuit. (08 Marks)

Module-3

- 5 a. Explain the two transistor model of Thyristor with neat diagram and derive the expression for anode current. (10 Marks)
b. Explain different turn ON methods of thyristor. (05 Marks)
c. Draw the VI characteristics of thyristor, define latching current and holding current. (05 Marks)

OR

- 6 a. Explain the $\frac{di}{dt}$ protection of thyristors. (06 Marks)
b. Explain UJT firing circuit for the SCR. (08 Marks)
c. A thyristor operating at 200 V, latching current of the thyristor is 100 mA, for a load of 20 Ω and 0.2 H. Find the minimum width of gate pulse required to turn on the thyristor. (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

Module-4

- 7 a. With neat circuit and waveforms, explain the single phase half wave controlled rectifier with RL load, derive the average and RMS output voltage. (10 Marks)
- b. Explain with neat circuit and waveform, the single phase dual converter. (10 Marks)

OR

- 8 a. Explain the single phase full wave AC voltage controller with R load with neat diagram and waveforms, and derive the RMS output voltage. (12 Marks)
- b. An AC voltage controller with ON-OFF control has an input of 230 V, 50 Hz is connected to a resistive load of 20Ω . The circuit is operating with the switch ON for 30 cycles and OFF for 30 cycles. Determine (i) RMS output voltage, current (ii) Input power factor. (05 Marks)
- c. List the applications of AC voltage controller. (03 Marks)

Module-5

- 9 a. With neat diagram and waveform, explain the step-up chopper and derive the expression for the output voltage. (10 Marks)
- b. Classify the different types of chopper. With the help of circuit and quadrant diagram, explain four quadrant (Class E) chopper. (10 Marks)

OR

- 10 a. With neat circuit and waveform, explain the operation of single phase full bridge inverter and derive the RMS output voltage. (10 Marks)
- b. List the different types of voltage control techniques for single phase inverters, briefly explain about,
(i) Single pulse width modulation.
(ii) Sinusoidal pulse width modulation. (10 Marks)
