

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

15NT54

## Fifth Semester B.E. Degree Examination, Dec.2018/Jan.2019 Digital Systems Design

Time: 3 hrs.

Max. Marks: 80

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

### Module-1

- 1 a. Explain and design a binary full adder with a truth table and Boolean expressions for the outputs. (08 Marks)
- b. What are comparators? Design 1 bit binary comparator and implement with suitable logic gates. (08 Marks)

OR

- 2 a. Explain briefly about combinational circuits and sequential circuits. (06 Marks)
- b. State and explain the applications of a multiplexer. (04 Marks)
- c. Describe the implementation of logic for basic gates using NAND and NOR gates. (06 Marks)

### Module-2

- 3 a. Write a short note on parity generators. (08 Marks)
- b. Write a verilog code for 4-bit ripple carry adder. (08 Marks)

OR

- 4 a. Write a verilog code for 2:1 MUX using IF and CASE statement. (08 Marks)
- b. Design a 4-bit comparator using 2 bit comparator. (08 Marks)

### Module-3

- 5 a. Explain the working of D-latch using NOR gate with truth table, symbol. (08 Marks)
- b. Write a short note on shift registers. Name the types of shift registers. (04 Marks)
- c. Draw logic diagram and truth table for up/down counter. (04 Marks)

OR

- 6 a. Explain the working of Asynchronous counter with truth table. (10 Marks)
- b. Explain about T-latch with truth table and logic diagram. (06 Marks)

### Module-4

- 7 a. Write notes on: i) Noise margin ii) Rise time iii) Fall time in CMOS. (04 Marks)
- b. Draw and explain realization of CMOS OR gate and AND gate. (08 Marks)
- c. Explain about NMOS and PMOS with suitable diagram. (04 Marks)

OR

- 8 a. Discuss about CMOS transmission gates and multiplexer. (08 Marks)
- b. Draw and explain realization of CMOS NOR gate and NAND Gate. (08 Marks)

### Module-5

- 9 a. Write a verilog HDL code for SR and D-flipflop. (10 Marks)
- b. Write a verilog code for up/down counter. (06 Marks)

OR

- 10 a. Write a note on programmable logic array (PLA) and Field Programmable Gate Array (FPGA). (10 Marks)
- b. Write a verilog HDL code for 4 bit ALU design by behavior model method. (06 Marks)

\* \* \* \* \*

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.