

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

15NT54

Fifth Semester B.E. Degree Examination, Dec.2019/Jan.2020

Digital Systems Design

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Draw and explain NAND and NOR gates with truth table. (04 Marks)
- b. Define half adder. Design half adder with truth table and block diagram. (06 Marks)
- c. With the aid of block diagrams, distinguish between a decoder and encoder. (06 Marks)

OR

- 2 a. State and explain the applications of a multiplexers. (04 Marks)
- b. Write a verilog code for all the basic gates using data flow, structural flow and behavioural flow description method. (12 Marks)

Module-2

- 3 a. Explain briefly the operation of ripple carry adder with block diagram and logic diagram. (08 Marks)
- b. Write a short note on parity generators. (08 Marks)

OR

- 4 a. Explain the operation of 3 bit rotators using multiplexer. (08 Marks)
- b. Write a verilog code for 4-bit ripple carry adder. (08 Marks)

Module-3

- 5 a. Explain the operation of SR latch using NAND gate with truth table. (08 Marks)
- b. Define shift register. Discuss PIPO with a neat diagram. (08 Marks)

OR

- 6 a. Discuss binary 4-bit synchronous up counter. (07 Marks)
- b. Discuss the operation of SISO with a neat diagram. (05 Marks)
- c. Draw the circuit diagram and truth table for up down counter. (04 Marks)

Module-4

- 7 a. Draw and explain realization of CMOS NOR gate and NAND gate. (08 Marks)
- b. Explain NMOS and PMOS with suitable diagram. (08 Marks)

OR

- 8 a. Discuss CMOS transmission gates and multiplexers. (10 Marks)
- b. Explain the power dissipation equation for CMOS. (06 Marks)

Module-5

- 9 a. Write a Verilog HDL code for SR and D flip-flop. (10 Marks)
- b. Write a verilog HDL code for 4-bit ALU design by behavior model method. (06 Marks)

OR

- 10 a. Write a note on programmable logic array and field programmable gate array. (12 Marks)
- b. How to write a verilog code for latch? (04 Marks)

* * * * *

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.