

**Sixth Semester B.E. Degree Examination, June 2012**  
**Analog and Mixed Mode VLSI Design**

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting  
at least TWO questions from each part.**

**PART – A**

- 1 a. Determine the number of quantization levels needed if one wanted to make a digital thermometer that is capable of measuring temperature within  $0.1^{\circ}\text{C}$  accuracy over the range  $-50^{\circ}\text{C}$  to  $150^{\circ}\text{C}$ . What is the resolution of ADC? (04 Marks)
- b. Calculate DNL for a 3 bit ADC for the transfer curve shown in Fig.Q1(b). Assume  $V_{\text{ref}} = 5\text{V}$ . Draw the quantization error  $Q_e$  in units of LSB. (06 Marks)

 


Fig.Q1(b)

- c. With a neat diagram, explain the mixed signal layout issues in detail. (10 Marks)
- 2 a. Plot the transfer curve of a 3-bit R-2R DAC, if all  $R_s = 1.1\text{ k}\Omega$  and  $2R_s = 2\text{ k}\Omega$ . What is the max INL for the converter? Assume all of the switch to be ideal and  $V_{\text{ref}} = 5\text{ V}$ . (12 Marks)
- b. Design a 3 bit pipeline DAC and explain its operation. Also find the output voltage for a 3-bit pipeline DAC for 3 cases  $D_A = 101$ ,  $D_B = 010$ ,  $D_C = 011$ . Show that the conversion time to perform all three conversions is 5 clock cycles using pipeline approach. Assume  $V_{\text{ref}} = 5\text{ V}$ . (08 Marks)
- 3 a. With a neat diagram, explain the operation of a parallel feed through ADC along with its advantages and disadvantages. (08 Marks)
- b. Design a 3 bit pipeline ADC. Analyse the conversion process by making a table for  $D_2$ ,  $D_1$ ,  $D_0$ ,  $V_2$ ,  $V_1$  for  $V_{\text{in}} = 2\text{V}$ ,  $3\text{V}$ ,  $4.5\text{V}$ . Assume  $V_{\text{ref}} = 5\text{V}$ . Let  $V_3$  be residue of 1<sup>st</sup> stage and  $V_2$  be residue of 2<sup>nd</sup> stage. (06 Marks)
- c. Explain the operation of a single slope ADC, with a neat diagram. (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- 4 a. Draw the block diagram of a high performance comparator and hence explain the operation of a decision circuit and obtain an expression for switching point. (10 Marks)
- b. Explain the operation of a CMOS quad multiplier and hence obtain an expression for the multiplier output voltage. (10 Marks)

**PART – B**

- 5 a. Develop an expression for the effective number of bits in terms of measured SNR if the input sinewave has a peak amplitude of 40% of  $(V_{ref+} - V_{ref-})$ . (06 Marks)
- b. Explain dump and interpolate circuit used for interpolation and reverse averaging. (08 Marks)
- c. What is the magnitude response of  $(1 - z^{-1})^3$ . Sketch a block diagram implementation of the filter. (06 Marks)
- 6 a. Explain the sub-mirror CMOS process flow with a neat diagram. (12 Marks)
- b. Estimate the size of Metall only to obtain the capacitance of 1 pF for the capacitor layout shown in Fig.Q6(b). Also estimate the bottom parasitic capacitance. (04 Marks)

 


Fig.Q6(b)

- c. Explain the fabrication of resistor using n-well. (04 Marks)
- 7 a. Explain the operation of D-Flip flop using TSPC logic and clocked CMOS logic with a neat diagram. (08 Marks)
- b. Write the design equation for full adder. Using the equation, design full adder using dynamic logic. (08 Marks)
- c. For the circuit shown in Fig.Q7(c), estimate the delay time. (04 Marks)

 


Fig.Q7(c)

- 8 a. Show that the floating current source will not load or decrease the resistance seen by cascade structure. (08 Marks)
- b. Implement high speed, low power differential output op-amp and explain the operation. (12 Marks)

\*\*\*\*\*