



Sixth Semester B.E. Degree Examination, June-July 2009
Analog and Mixed Mode VLSI Design

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting
at least TWO questions from each part.**

PART – A

- 1 a. State the reasons for the pedestal error, droop aperture error and sampling error. (08 Marks)
b. State and explain specifications of ADC. (12 Marks)
- 2 a. An 8 bit resistor string DAC was fabricated with a nominal resistor value of 1 k Ω . If the process was able to provide matching of resistors to within 1%, find maximum INL and DNL of the converter. Assume $V_{REF} = 5V$. (06 Marks)
b. Explain generic (unweighted) current steering DAC and discuss the related mismatch errors. (08 Marks)
c. Design a 4 bit charge scaling DAC using a split array. Assume that $V_{REF} = 5V$ and that $C = 0.5$ pF. Draw the equivalent circuit for $D = 0001$ and 0010 and determine the value of the output voltage. (06 Marks)
- 3 a. Explain the principle of single slope ADC and the problems associated with it. (10 Marks)
b. Draw the block diagram for 4 bit successive approximation ADC with $V_{REF} = 5V$. Explain the same. Trace the output at various stages for $V_{in} = 3.7V$. (10 Marks)
- 4 a. Explain the purpose of each stage of a voltage comparator. Also explain the working of 1st stage. (10 Marks)
b. Show that multiplying quad acts as multiplier when all the MOSFETs in the multiplying quad have the same threshold voltage. (10 Marks)

PART – B

- 5 a. Determine the ideal SNR of a 8 bit data converter with averaging of 20 outputs. (04 Marks)
b. Draw the circuit arrangement used for decimation and averaging and explain the same. Determine the transfer function of the same. (10 Marks)
c. Bring out the principle of interpolation. (06 Marks)
- 6 a. Describe CMOS process flow with neat sketches. (10 Marks)
b. Explain how MOSFET behaves as a capacitor. Also explain floating MOS capacitor. (10 Marks)
- 7 a. Estimate the high-to-low and low-to-high delays in the circuits shown in figure Q7 (a). (08 Marks)

 


Fig. Q7 (a)

- b. Draw the arrangement for 4 bit pipelined adder and full adder bit implemented using dynamic logic. (06 Marks)
- c. Explain the working of simple delay element using pass transistor and CMOS inverter. (06 Marks)

- 8 a. Explain the limitations of inverter at the output of OPAMP, with the help of its transfer curve. How is it overcome? (07 Marks)
- b. Consider the AC small signal simplification of floating current source as in figure Q8 (b). Assuming NMOS cascade output resistance is labeled R_{NCOS} , what is the small signal resistance as seen by the test voltage V_{test} ? (07 Marks)

 


Fig. Q8 (b)

- c. Determine time constant of OPAMP with unity gain frequency of 100 MHz. Assume that all the outputs is fed back to the input. Also determine the settling time for 0.1% settling accuracy. (06 Marks)

USN

--	--	--	--	--	--	--	--	--	--

Sixth Semester BE Degree Examination, Dec.09-Jan.10
Analog and Mixed Mode VLSI Design

Time: 3 hrs.

Max. Marks:100

- Note: 1. Answer any FIVE full questions, selecting at least TWO questions from each part.
2. Standard notations are used.
3. Missing data be suitably assumed.

PART – A

- 1 a. Define Resolution, INL, DNL and V_{FS} for a DAC. (06 Marks)
b. Find the maximum DNL and INL in LSBs of a 3 bit DAC which has the following characteristics. Check if it is monotonic. (10 Marks)

Digital input	000	001	010	011	100	101	110	111
Analog output	0 V	0.625 V	1.5625 V	2.0 V	2.5 V	3.125 V	3.4375 V	4.375 V

- c. Find the maximum resolution of an ADC which can use the S/H circuit with maximum sampling error of 0.628 mV while maintaining a sampling error less than 1/2 LSB $V_{ref} = 5V$. (04 Marks)
- 2 a. Discuss the issues involved in mixed signal circuit layout. (10 Marks)
b. Describe the simple resistor string DAC, problem associated with it and how is it overcome by use of a binary switch array. (10 Marks)
- 3 a. Describe the pipelined ADC with a neat diagram. (08 Marks)
b. For an 8 bit pipelined ADC, all the amplifiers had a gain of 2.1 v/v instead of 2v/v. If $V_{in} = 3V$ and $V_{ref} = 5V$, what would be the resulting digital output, assuming other components are ideal. (06 Marks)
c. For a 4 bit successive approximation ADC with $V_{ref} = 5V$, $V_{in} = 1V$, find the output digital code. Assume a dual slope successive approximation ADC. For each clock cycle, give the output of the SAR, V_{out} and the final output. (06 Marks)
- 4 a. Discuss the advantages and disadvantages of using a dual slope over a single slope ADC. (06 Marks)
b. Draw the CMOS analog multiplier and explain its working. (07 Marks)
c. Discuss transient response, propagation delay and minimum slewrate of a comparator. (07 Marks)

PART – B

- 5 a. Develop an expression for effective number of bits in terms of the measured SNR if the input wave has a peak amplitude of 30% of V_{ref} . (07 Marks)
b. With a neat block diagram, describe the accumulate and dump circuit for decimation and averaging. (07 Marks)
c. Sketch the block level circuit diagram for an $f_s/4$ digital resonator. (06 Marks)
- 6 a. With relevant diagrams, describe the CMOS process flow, for devices with $L_{min} < 0.35 \mu m$. (10 Marks)
b. Describe with a neat diagram, the conceptual layout and actual layout of an R-2R resistor string with minimum area and also discuss the problem of laying out metal over the resistive material. (10 Marks)
- 7 a. Sketch the implementation of a synchronous up/down counter and discuss its operation. (07 Marks)
b. Draw the 4 bit pipelined adder and describe how it operates. (08 Marks)
c. Draw the positive edge triggered delay using clocked CMOS logic. (05 Marks)
- 8 a. Illustrate how a pushpull output stage is biased with a floating current source. (07 Marks)
b. Infer that, to minimize the input referred noise, the gain of the first stage of the amplifier should be large in a cascade of amplifiers. (06 Marks)
c. Discuss circuit noise in an opamp. (07 Marks)

Important Note: 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8=50, will be treated as malpractice.

USN

--	--	--	--	--	--	--	--	--	--

06EC63

Sixth Semester B.E. Degree Examination, May/June 2010
Analog and Mixed Mode VLSI Design

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting
at least TWO questions from each part.**

PART – A

- 1 a. Explain the characteristics and typical errors associated with sample and hold circuit. (10 Marks)
- b. Briefly explain the ADC specifications. (05 Marks)
- c. Find the resolution of DAC, if the output voltage is desired to change in 1 mV increments while using a reference voltage of 4V. (05 Marks)
- 2 a. Explain qualitatively the architecture and working of charge scaling DACs. (10 Marks)
- b. Design a 3-bit charge scaling DAC and find the value of output voltage for $D_2D_1D_0 = 100$ and 011. Assume $V_{ref} = 5V$, $C = 0.5 PF$. (05 Marks)
- c. Briefly explain the architecture & working of a pipeline digital to analog converter. (05 Marks)
- 3 a. Explain the architecture and working of a flash ADC. (08 Marks)
- b. If a 10-bit flash ADC is designed, determine maximum offset voltage of comparators which will make INL less than $\frac{1}{2}$ LSB. Assume that resistor string is perfectly matched and $V_{REF} = 4V$. (04 Marks)
- c. Briefly explain the block diagram of a 2-step flash ADC and its working. (08 Marks)
- 4 a. Explain qualitatively preamplification and decision circuits of a CMOS comparator unit. Draw their CMOS circuits. (10 Marks)
- b. Explain the principle of an analog multiplier. (05 Marks)
- c. Briefly explain CMOS analog multiplier with the help of a circuit diagram. (05 Marks)

PART – B

- 5 a. Define SNR, effective number of bits and clock jitter in mixed signal circuits qualitatively. (08 Marks)
- b. Explain the principle of averaging to improve SNR, in mixed signal circuits. (06 Marks)
- c. Briefly explain the role of decimating filters in ADCs. (06 Marks)
- 6 a. With a neat process flow diagram, explain submicron CMOS technology and bring out the differences as compared to CMOS technology. (10 Marks)
- b. Explain how capacitor and resistor elements are fabricated in submicron technology. (07 Marks)
- c. Explain MOSFET as a switch. (03 Marks)

Important Note: 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

- 7 a. What are delay elements? Explain how they are realized using pass transistors, inverters and C²MOS and TSPC circuits. (10 Marks)
- b. Realize a 4-bit pipelined adder using latches and explain its operation. (05 Marks)
- c. Implement full adder using dynamic logic and explain. (05 Marks)
- 8 a. Consider a small signal amplification of a floating current source shown in Fig.Q8(A). Assuming NMOS cascade o/p resistance is labeled $R_{n,cas}$, what is the small signal resistance seen by test voltage V_{test} ? (10 Marks)

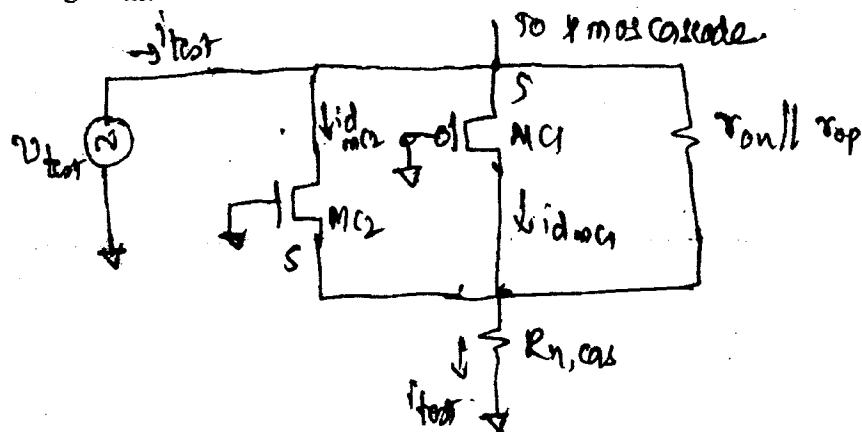


Fig.Q8(A)

- b. Explain with the help of circuit diagrams, the technique of making the flow rate concern in the design of op amp. (10 Marks)
