

7. (a) Explain the following w.r.t. Synthesis (i) RTL (ii) Constraints (12 Marks)
- (b) Write the RTL description that uses component instantiation for D flip flop (8 Marks)
8. Write short notes on
- (a) Drivers
 - (b) File types
 - (c) Packages
 - (d) Procedures
- (20 Marks)

* * *

- 6. (a) Bring out the differences between lower level configuration and ENTITY ARCHITECTURE pair configuration. (8 Marks)
- (b) Explain the importance of Board - Socket - chip analogy. (4 Marks)
- (c) Using the Board - Socket - chip analogy write a VHDL program for D flip flops. (8 Marks)
- 7. (a) Explain the register transfer level description with an example. (10 Marks)
- (b) Write a VHDL program for a 4 bit shifter using sequential statements. (10 Marks)
- 8. Explain
 - a) Statement Concurrency
 - b) Block statement
 - c) Sub program
 - d) Synthesis

(4 x 5 = 20 Marks)

** * **

Page No

Si

Time: 3

1. (

(

(

2. (

(

(

3. (a

(

(

4. (a


(b

5. (a

(b

6. (a

(b

 

EG/TE6D1

Sixth Semester B.E. Degree Examination, July/August 2002
Electronics and Communication/Telecommunications Engineering

VHDL

19

[Max.Marks : 100]

Time: 3 hrs.]

Note: Answer any FIVE full questions.

1. (a) Explain briefly the terms:

- i) Architecture
- ii) Configuration
- iii) Generic
- iv) Process

(4 × 2 = 8 Marks)

(b) Give the structural and behavioural description of SR flip flop.

(6+6=12 Marks)

2. (a) Explain concept of concurrent statements and event scheduling with examples. (6 Marks)

(b) Explain port delay, inertial delay and simulation delta in VHDL. (12 Marks)

3. (a) Explain following sequential statements if, case, loop, assert and wait with examples. (10 Marks)

(b) Write a VHDL program to select the largest of 3 integers. (10 Marks)

4. (a) Explain the various data types of VHDL with examples. (12 Marks)

(b) Write a VHDL program for a 8 to 3 encoder-operation. (8 Marks)

5. (a) Bring out the differences between single dimension and multi dimension arrays with examples. (8 Marks)

(b) Write a VHDL program for a mux when input 'a' is selected the process waits for changes on 'select' and 'a' and ignores changes on 'b'. Similarly if 'b' is selected changes in 'a' is to be ignored. (12 Marks)

6. (a) Explain record types and incomplete types. (6 Marks)

(b) Write a VHDL program to simulate the operation of a stack for read/write purposes. (14 Marks)

7. (a) Explain lower level configuration with examples and entity architecture configuration with examples. (8 Marks)

(b) Using configuration statement realise a full adder circuit using two half adders and a or gate. Write the VHDL program both for full adder and half adder and bind them using configurations. (12 Marks)

8. (a) Describe the file types and packages. (10 Marks)

(b) Explain RTL descriptions and block statements with examples. (10 Marks)



7. (a) Explain briefly RTL description

(5 Marks)

(b) Write a note on state machine in VHDL code.

(5 Marks)

(c) Write a VHDL code for 8 bit universal shift register with serial, parallel data input and left and right shift.

(8 Marks)

8. Write short notes on any FOUR :

(a) Component instantiation

(b) Test bench

(c) Subprograms

(d) Constraints

(e) Attributes

(4 x 5 = 20 Marks)

*** **

- (c) Write the behavioral code to simulate 5 byte ROM. The ROM is provided with active-low chip select line & an address line. (8 Marks)



 


Fig 4(c)

 5. (a) Explain procedure and function with syntax and a common example of finding the average of two numbers. (10 Marks)
- (b) Write the package structure and explain its parts, with an example. (6 Marks)
- (c) What is deferred constant? Give an example. (4 Marks)
6. (a) Explain configuration. Compare default configuration & component configuration. (8 Marks)
- (b) Write VHDL code to simulate 4-bit asynchronous counter (up). The code should have JK flip-flop (behavioral) program and counter (structural) program. Use configurations, to bind them. (12 Marks)
7. (a) Explain RTL description with example. (10 Marks)
- (b) Explain the following with respect to synthesis: (10 Marks)
- i) constraint
 - ii) attribute
 - iii) technology library.
8. Write short notes on: (4 × 5 = 20 Marks)
- i) Library in VHDL
 - ii) Composite data type
 - iii) Event scheduling.
 - iv) ASSERT Statement.



USN

 

Sixth Semester B.E. Degree Examination, January/February 2004
Electronics & Communication / Telecommunication Engineering

VHDL

22

[Max.Marks : 100

Time: 3 hrs.]


Note: Answer any FIVE full questions.

1. (a) Write a VHDL program to simulate 4 : 1 MUX functionality using conditional assignment statement. (8 Marks)
- (b) Explain briefly the statement concurrency with the help of a simple VHDL program. (7 Marks)
- (c) Differentiate inertial delay and transport delay with the help of timing diagrams. (5 Marks)
2. (a) Write a VHDL program to model N-input NAND gate. Use generics and exit statement. (6 Marks)
- (b) Differentiate signal assignment and variable assignment, with an example. (4 Marks)
- (c) Write a VHDL program to model shift register with shift right PIPO and restore status facilities. Use generate statement. (10 Marks)
3. (a) Explain with an example vector the following operations. (6 Marks)
i) sll ii) sra iii) ror.
- (b) Write a simple VHDL program to demonstrate shift left and right operations using concatenation operator. (7 Marks)
- (c) Write a function subprogram to model 4 : 1 MUX circuit. (7 Marks)
4. (a) Write a 3-8 decoder model using VHDL. use file 1 to store and assign signal values for all input ports and use another file to store output of decoder. (10 Marks)
- (b) Write a procedure subprogram to model demux circuit. (10 Marks)
5. (a) Write a package and package body to include few type declarations, constants a procedure and a function. (12 Marks)
- (b) Write ALU model (for add, sub, rot, shift right, NOT, XOR, AND and OR operations) using case statement. Use enumerated data type. (8 Marks)
6. (a) Write state diagram and its implementation in VHDL for "101" sequence detector. (10 Marks)
- (b) Write RTL description for MOD-9 counter and the corresponding VHDL program. (10 Marks)

7. (a) Explain the following in the Leonardo synthesis environment
- i) RTL level description
 - ii) Constraints
 - iii) Attributes
 - iv) Technology libraries.

(3 × 4 Marks)

 - (b) Write VHDL model for the following schematic shown in fig.7(b). Use block configuration



(8 Marks)

8. Write short notes on :

(4 × 5 Marks)

- i) CAD tools for VLSI design
- ii) Justify the use of VHDL for design entry
- iii) Circuit synthesis
- iv) Physical data types

** * **

USN

--	--	--	--	--	--	--	--	--	--

Sixth Semester B.E. Degree Examination, July/August 2004

Electronics & Communication/Telecommunication Engineering


VHDL

Time: 3 hrs.]

[Max.Marks : 100

- Note:** 1. Answer any FIVE full questions.
2. All questions carry equal marks.

 1. (a) Describe the following with suitable example.
 - i) Symbols V/s Entities (4 Marks)
 - ii) Schematic V/s Architecture (4 Marks)
 - iii) Event scheduling. (2 Marks)
- (b) What are the advantages of VHDL over traditional design, explain. (4 Marks)
- (c) Write the VHDL behaviour description for the JK flip-flop shown (fig.1(c)) and explain. (6 Marks)



← fig 1(c)

2. (a) Explain delta delay mechanism and any other delay mechanism with suitable example. Compare the two mechanisms. (10 Marks)
- (b) Explain the syntax of "WITH SELECT" statement with an example. (6 Marks)
- (c) Write VHDL program for D latch using guarded block statement. (4 Marks)
3. (a) Explain with example "Sensitivity list versus WAIT statement". (6 Marks)
- (b) Explain the BNF of "ASSERT Statement" with suitable example. (8 Marks)
- (c) Write VHDL code for structural description of 4-bit adder. (6 Marks)
4. (a) Write behaviour code for four bit shift register with parallel load and serial output and explain. (8 Marks)
- (b) Explain with an example each :
 - i) Enumerated data type
 - ii) Physical data type. (6 Marks)
- (c) Explain VHDL objects with suitable example. (6 Marks)

Contd.... 2

5. (a) Explain 'function' with syntax and write VHDL code for converting array of std-logic type to integer using 'function'. (10 Marks)
- (b) What is resolution function? Explain with VHDL code the resolution function for 4 value system. (10 Marks)
6. (a) Discuss with suitable example architecture that contains instantiated components can be configured. (10 Marks)
- (b) What is default configuration? Explain with example how default configuration can be used to bind architecture to an entity. (10 Marks)
7. (a) Write VHDL model using two process style to describe the 4 bit counter with clear and load. (7 Marks)
- (b) Explain synthesis process. (5 Marks)
- (c) Define Mealy machine and Moore machine. Describe Moore machine with an example. (8 Marks)
8. Write short note on :
- a) Access type data
 - b) Procedure
 - c) Attributes
 - d) Generics.
- (4 × 5 = 20 Marks)

*** **

24
USNSrinivas Institute of Technology
Library, Mangalore EC/TE6D1

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Sixth Semester B.E. Degree Examination, January/February 2005
Electronics & Communication / Telecommunication Engineering
VHDL

Time: 3 hrs.]

[Max.Marks : 100

Note: Answer any FIVE full questions.


1. (a) Explain the following with a suitable example for each :
 - i) Event scheduling
 - ii) Concurrent signal assignment/ statement concurrency
 - iii) Guarded block statement. (4 × 3 = 12 Marks)
- (b) Explain the concept of behavioral description and structural description using half-adder as an example. (8 Marks)
2. (a) Describe the concept of inertial delay and transport delay. Develop a VHDL code for a buffer using inertial delay model and transport delay model. (10 Marks)
- (b) Write VHDL coding for a T flip-flop using PROCESS with a sensitivity list. Include an assertion statement in your model, which expresses the requirement that a flip-flop's two outputs Q and Qb of the type Std-logic are complementary. (10 Marks)
3. (a) Write a VHDL behavioral model of a 4-bit counter with asynchronous reset and preset facilities. (10 Marks)
- (b) Explain the following sequential statements along with BNF and give an example for each:
 - i) CASE ii) WAIT (6 Marks)
- (c) Bring out the differences between signal assignment and variable assignment. (4 Marks)
4. (a) Explain the following data types with suitable example:
 - i) Enumerated type ii) Physical type (6 Marks)
- (b) Indicate the significance of ARRAY type declaration. Write VHDL code for modelling a ROM of capacity 8×4 bits. (10 Marks)
- (c) Write a RECORD type of declaration for a test stimulus record containing a stimulus bit vector of 3-bits, a delay value and an expected response bit vector of 8-bits. (4 Marks)
5. (a) Bring out the differences between functions and procedures. Give the general format for subprogram declaration and the corresponding calling statement. (8 Marks)

Contd.... 2

- (b) Write a complete VHDL code to perform the following operation : use a function to convert the input array to integer, determining the maximum of three numbers in integer and outputting the value in array using functions and packages. (12 Marks)
6. (a) Define the resolution function. Discuss in detail the resolution function for a four value system. (10 Marks)
- (b) Explain the different types of configuration statements with suitable examples. (10 Marks)
7. (a) Explain the following with respect to synthesis i) RTL ii) Constraints (10 Marks)
- (b) Explain the various steps involved in the conversion of RTL description to gate level net list. (10 Marks)
8. (a) Write a VHDL program for a 4-bit shifter using sequential statements. The shifter is to be provided with a facility of loading and shifting to right or left by one bit at a time. (10 Marks)
- (b) Discuss in brief :
- i) Package declaration and package body (6 Marks)
- ii) Generics. (4 Marks)

** * **

NEW SCHEME

 

Reg. No.


Sixth Semester B.E. Degree Examination, January/February 2006
Electronics & Communication/Telecommunication Engineering
Digital System Design Using VHDL

Time: 3 hrs.)

(Max.Marks : 100

Note: Answer any FIVE full questions.

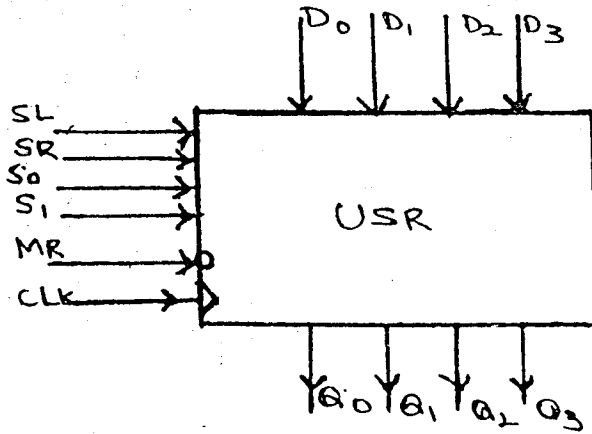1. (a) Explain briefly :
 - i) Entity architecture pair
 - ii) Package in VHDL. (5+5 Marks)
- (b) Write a VHDL code for a full subtracter using logic equation. (6 Marks)
- (c) If $A=1100$, $B=1110$, $C=1001$, compute $Y_1 = \text{not } A \text{ and } B \text{ nor } 2$
 $Y_2 = B \text{ sla } 2 \text{ and } C \text{ sll } 2$. (4 Marks)
2. (a) What is meant by variables, signals and constants in VHDL? Compare signals with variables, give an example for each. (10 Marks)
- (b) Write a VHDL module for a universal shift register with following functions. MR Active low, a synchronous reset I/P that resets all flipflops. Two control inputs ($S_1 S_0$) when 00, no action, when 10, register is shifted right and serial data SR enters Q_0 , when 01, 4 bit data shifted left and SL enters Q_3 . If $S_1 S_0 = 11$, 4 bit data is loaded parallelly. (8 Marks)



(c) Specify the general form of case statement. (2 Marks)

3. (a) Realize the following functions using PLA.

$$F_1 = \sum m(2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$$

$$F_2 = \sum m(2, 3, 5, 6, 7, 10, 11, 14, 15)$$

$$F_3 = \sum m(6, 7, 8, 9, 13, 14, 15)$$


Write VHDL code for implementation of F_1 , F_2 and F_3 .

(6+6 Marks)

Contd.... 2

- (b) Write a VHDL code for D flipflop that reports error for setup and hold time violation. Assume set up time = hold time = 5ns and display text string as violation of setup Or hold time. (8 Marks)
4. (a) Write state diagram that generates control signals for 4x4 bit multiplier. Explain with block diagram. (8 Marks)
- (b) Design signed multiplier and write a VHDL code to multiply two signed numbers. (6+6 Marks)
5. (a) Derive a SM chart to realize DICE game. (10 Marks)
- (b) Using PLA and D flip flops realize the SM chart for the dice game. (10 Marks)
6. (a) Explain briefly with neat sketch Kilink 3000 series I/O block. (8 Marks)
- (b) Write a function Fadd ion VHDL to realize full adder operation. Design 4 bit parallel adder using full adders and write behavioral model for 4 bit parallel adder that uses function Fadd. (6+6 Marks)
7. (a) What is meant by attributes. Explain signal attribution with an example for each. (2+6 Marks)
- (b) Write a VHDL code for T flipflop. Using T flipflop as component write structural model for 8 bit up counter. Assume active low asynchronous clear input and falling edge triggered clock. Use Generate statement (2+4 Marks)
- (c) Write a VHDL module for memory model (RAM6116). Assume 8 bit address lines, 8 bit data lines, active low chip enable and active low write enable. (6 Marks)
8. Write short notes on any FOUR :
- (a) Transport and inertial delay
- (b) Generic
- (c) Signal resolution
- (d) Modeling mealy machine
- (e) VHDL procedures. (5×4=20 Marks)

* * * * *

 

NEW SCHEME

**Sixth Semester B.E. Degree Examination, July 2006
E & C**

Digital System Design using VHDL

Time: 3 hrs.]

[Max. Marks:100

Note: Answer any FIVE full questions.

- 1 a. Explain structural and behavioral description with examples. (08 Marks)
 - b. Differentiate between : i) Signal and variable assignment (06 Marks)
ii) Event and transactions.
 - c. Write a VHDL program for detecting the number of 1's in an eight bit-vector. If even, it should output '0'; if odd, output = '1'. (06 Marks)
- 2 a. If A = 110101 B = 110010, compute (A S112) OR (B S1A3) (04 Marks)
 - b. A Moore sequential machine with two inputs x1 and x2 and output z has the following state table.

State	X1	X2	0 1	1 0	1 1	Z
1	1	0	1	2	2	0
2	1	1	2	2	1	1


Write the VHDL code at behavioral level. State changes occur after 5 ns and output changes occur 5 ns after state changes. (08 Marks)

- c. Realize using ROM and DFF and write the VHDL code using ROM table for

PS	NS	W=0	W=1	Z
0 0	0 0	0 1	0	0
0 1	0 0	1 0	0	0
1 0	1 0	0 1	0	0
1 1	1 0	0 1	1	1

(08 Marks)

 - 3 a. Find a minimum row PLA table to implement the following sets of functions
 $f_1(A,B,C,D) = \sum m(3,4,6,9,11)$
 $f_2(A,B,C,D) = \sum m(2,4,8,10,11,12)$
 $f_3(A,B,C,D) = \sum m(3,6,7,10,11)$
 and realize these functions using a PLA. (06 Marks)
- b. A counter has the count sequence as shown. Realise the counter using 16 R4 PAL. Draw the section of the PAL where this function is implemented.



(10 Marks)

- c. Write a VHDL code for the resolution function for X, 0, 1, z logic. (04 Marks)

Contd...2

- 4 a. Draw and explain the block diagram of a 2 digit BCD to binary converter and draw the state graph for the same. (08 Marks)
- b. Draw the block diagram, state graph and VHDL program for the behavioral model of a 4 x 4 multiplier. (12 Marks)
- 5 a. Design and explain an 8 bit divider wherein dividend is 8 bit and divisor is 4 bit. The shift and subtract action should take place in the same cycle. Draw the block diagram and state diagram. (10 Marks)
- b. Give the contents of the dividend register with respect to clock cycle for the dividend and divisor. Shift and subtract in separate clock cycles.
Dividend = 0 1 1 1 0 0 0 1 0 divisor = 1 0 1 0 1 0 1 0 (10 Marks)
- 6 a. For the following Sm chart give the timing diagram showing the clock, states, inputs and output. Give the PLA table.

 


Fig. 6 (a)


(10 Marks)

- b. Implement a bit binary counter using one Xilinx 3000 series logic cell. Qx is the LSB bit and Qy is the MSB of the counter. The counter has an enable input and a synchronous load. The counter operates as follows :
 En = 0 no change
 En = 1 . Ld = 1 load Qx and Qy with inputs u and v
 En = 1 Ld = 0 2 increment count
 i) Give the next state equations for Qx and Qy
 ii) Label the inputs on the FG mode diagram and show the connection paths. (10 Marks)

- 7 a. Write a VHDL code for a static Ram with truth table (08 Marks)

\overline{CS}	\overline{OE}	\overline{WE}	mode	I/o pins
H	X	X	not selected	high z
L	H	H	output disabled	high z
L	L	H	read	data out
L	X	L	write	Data in

 - b. Write a VHDL function that will find the dot product $\sum a_i * b_i$ of two integer vectors a and b. (06 Marks)
- c. Explain signal attributes with examples. (06 Marks)
- 8 a. Explain the Xilinx 3000 series logic cell (07 Marks)
- b. Explain transport and inertial delays with examples. (06 Marks)
- c. Write a VHDL code and synthesized circuit for case statement. (07 Marks)



USN

NEW SCHEME

Sixth Semester B.E. Degree Examination, Dec. 06 / Jan. 07

EC / TE

Digital System Design Using VHDL

Time: 3 hrs.]

[Max. Marks:100

Note : Answer any FIVE full questions.

1.
 - a. Using a single bit subtractor, write a VHDL code for 4-bit subtractor. (08 Marks)
 - b. Differentiate between the conditional assignment statement and single assignment statement with respect to 4 : 1 Mux. (06 Marks)
 - c. What are the predefined unconstrained arrays? Explain each with an example. (06 Marks)

2.
 - a. Bring out the differences between VHDL function and VHDL procedure with an example. (06 Marks)
 - b. Draw the structure of a 8-bit counter using 74163. Write a VHDL description for a 8-bit counter using 74163 model. (08 Marks)
 - c. Write a VHDL code for synthesis of a sequential CASE statement. (06 Marks)

3.
 - a. Write a VHDL description that converts a 5-bit bit_vector to an integer. (08 Marks)
 - b. Realize the following functions using PLA : (06 Marks)

 $f_1(a,b,c,d) = \sum m(2,3,5,7,8,9,10,11,13,15)$,

 $f_2(a,b,c,d) = \sum m(2,3,5,6,7,10,11,14,15)$ and $f_3(a,b,c,d) = \sum m(6,7,8,9,13,14,15)$
 - c. Model the tristate buffers with active – high output enable. (06 Marks)


 



Fig.3(c)

 4.
 - a. Design a 6-bit binary up-down counter using a 22V10 and a minimum number of external gates. Write the VHDL code for the counter using PLA. (10 Marks)
 - b. Design a keypad scanner for the following keypad layout. (10 Marks)



- 5
 - a. Design a 4-bit serial adder with accumulator and generate the control state graph and table which defines the operation of a serial adder. (08 Marks)
 - b. Write a VHDL module that describes one bit of a full adder with accumulator. The control i/p Ad = 1 add operation and Load = 1 load the i/p to the accumulator. (06 Marks)
 - c. Write a VHDL code for 2 input Nor gate with Rise / Fall time modeling using generic statement. (06 Marks)

 - 6
 - a. Write a test-bench for the Dice game problem to test the game components. (10 Marks)
 - b. The functional equivalent of a static RAM cell is as shown in figure. Write a VHDL code to realize the functionality (10 Marks)



G = 1, Q follows D
G = 0, data is latched

Fig. 6(b)

- 7
 - a. Give sequence of simulator commands that would test the divider for the case 93 divided by 17. (06 Marks)
 - b. Write a VHDL code for the resolution function for X 0 1 Z logic. (06 Marks)
 - c. Realize the SM chart given using a PLA, counter and 4-1 Mux. (08 Marks)

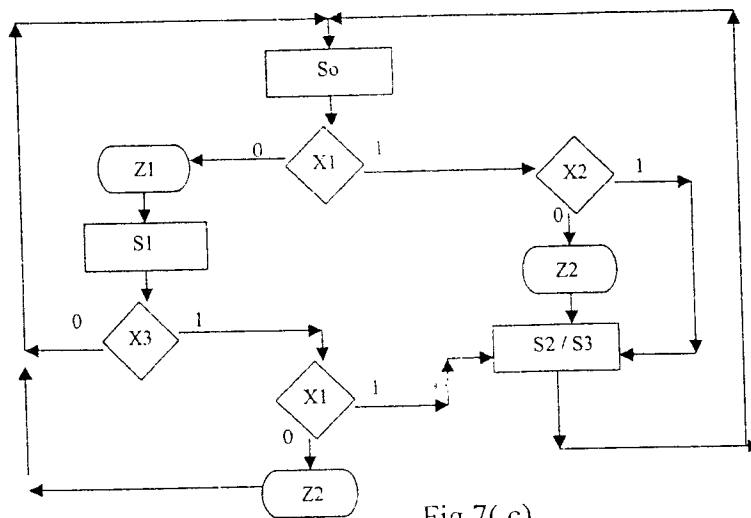



Fig.7(c)

- 8
 - a. Show how to realize the following combinational function using two 3000 series logic cells. (10 Marks)

$$F = X_1^1 X_2 X_3^1 X_6 + X_2^1 X_3^1 X_4 X_6^1 + X_2 X_3^1 X_4^1 + X_2 X_6 X_4^1 X_6 + X_3^1 X_6 X_4 X_5 X_6^1 + X_7$$
 - b. Write a VHDL code using One-hot assignment for the following specifications
 $T_0 : Q_0 Q_1 Q_2 Q_3 = 1000 ; T_1 = 0100 ; T_2 = 0010 ; T_4 = 0001$

$$Q_3^+ = X_1 Q_0 + X_2 Q_1 + X_3 Q_2 + X_4 Q_3 ; \quad Z_1 = X_1 Q_0 + X_3 Q_2 ;$$

$$Z_2 = X_2 Q_1 + X_4 Q_3 ;$$

 

USN

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

①

NEW SCHEME

Sixth Semester B.E. Degree Examination, July 2007
EC / TE

Digital System Design Using VHDL

Time: 3 hrs.]

[Max. Marks:100

Note : Answer any FIVE full questions.

1. a. Write down the VHDL-code to model the following :
 - i) D-flip flop
 - ii) J-K flip flop
 - iii) 4 : 1 multiplexer (09 Marks)
- b. Starting from a single bit full adder as a component, write down the structural VHDL description for a 4 bit adder. (06 Marks)
- c. With the help of a block diagram, explain the stages of compilation, elaboration and simulation. (05 Marks)

2. a. Develop the VHDL code for 8 bit counting using IC 74163 binary synchronous counters. Show the hardware diagram. (06 Marks)
- b. Explain with a set of statements, the sequential execution using process and if else statements. Assume suitable delays wherever necessary. (06 Marks)
- c. Implement a Mealy sequential network with ROM and D-flip flops for BCD to excess 3 code convertor. Draw the ROM truth table and ROM realization code. (08 Marks)

3. a. Using CMOS-PLD 22CE V10, design a VHDL code for a sequential traffic light controller. Supply the necessary state graph and state table. (10 Marks)
- b. For a keypad scanner (4 rows × 3 columns), develop a VHDL code incorporating key bouncing. Supply the stategraph for scanner and truth table for decoder. (10 Marks)

4. a. Draw the state graph for binary multiplier control and hence develop a behavioral VHDL model for binary multiplier. (10 Marks)
- b. Draw the block diagram for a signed divider (32 bits by 16 bits) with the associated control circuits. Supply the steps of procedure to carry out the division. Draw the state graph for control circuit. (10 Marks)

5. a. Describe the design of a serial adder with accumulator supplying the block diagram control state graph and state table. (10 Marks)
- b. Derive an SM chart for the control of unsigned binary multiplier (4 bits × 4 bits). Convert this SM chart into VHDL code. (10 Marks)

- 6 a. For the dice game based on the following rules, draw the SM chart and develop the behavioral VHDL code.
- i) After the first roll of the dice the player wins if the sum is 7 or 11. The player loses if the sum is 2, 3 or 12. Otherwise, the sum the player obtained on the first roll is referred to as a point and he or she must roll the dice again.
 - ii) On the second or subsequent roll of the dice, the player wins if the sum equals the point, and he or she loses if the sum is 7. Otherwise, the player must roll again until he or she finally wins or loses. (10 Marks)
- b. With Xilinx XC 3020, implement a parallel adder-subtractor with an accumulator. Show a typical logic design cell with inputs and outputs, and signal paths shown after programming. (10 Marks)
- 7 a. Assuming that configuration data is available in EPROM, outline the steps of procedure to design any digital system using FPGA. Give one example of design. (10 Marks)
- b. Explain IEEE-1164 standard logic system for use with VHDL taking one VHDL code example. (10 Marks)
- 8 a. Develop a VHDL code for a RAM system with data register, memory control and MAR, giving block diagram and the corresponding SM chart. (10 Marks)
- b. Write the separate SM charts for simplified 486 bus interface with CPU and for UART receiver. (10 Marks)

USN

--	--	--	--	--	--	--	--	--	--	--	--

Srinivas Institute of Technology
Library, Mangalore



EC64

Sixth Semester B.E. Degree Examination, Dec. 07/Jan. 08
Digital System Design Using VHDL

Time: 3 hrs.

Marks: 100

14

Note : Answer any FIVE full questions.

1. a. Explain the following with declaration format and an example each: (06 Marks)
 - i) Variable
 - ii) Signal
 - iii) Constant
- b. Using a process statement write a VHDL source code for 4 to 1 multiplexer. (06 Marks)
- c. Bring out differences between a VHDL function and a VHDL procedure with a suitable example. (08 Marks)

2. a. The data stored in the ROM location are (9, A, 0, 0, 1, 0, 0, 1, F, C, C, D, 7, 4, 6, 7). Write a VHDL code for the ROM realization by using the binary values of the numbers given above. (06 Marks)
- b. Find a minimum row PLA table to implement the following set of functions. (09 Marks)

$$f_1(A, B, C, D) = \sum m(3, 4, 6, 9, 11)$$

$$f_2(A, B, C, D) = \sum m(2, 4, 8, 10, 11, 12)$$

$$f_3(A, B, C, D) = \sum m(3, 6, 7, 10, 11)$$
- c. A keypad has 4 rows and 3 columns as shown in figure Q2 (c)

1	2	3
4	5	6
7	8	9
*	0	#

Fig. Q2 (c)

Assume no more than two keys will be pressed at a time. Write the block diagram of keypad scanner and first 10 rows of the truth table for a keypad decoder. If 2 keys are pressed in the same column, the N output should indicate the key in the first of the 2 rows. (05 Marks)

3. a. With a neat block diagram and the function tables, explain the operation of a serial adder with accumulator. (06 Marks)
- b. The state graph for faster multiplex (4 × 4) is as shown in figure Q3 (b). Write a behavioral model (VHDL source code) for 2's complement 4 × 4 binary multiplier. (07 Marks)

 


Fig. Q3 (b)

- 3 c. Design a binary divider and draw the block diagram of the same. Show the procedure to divide 135 by 13 [convert it into binary and perform the operations]. (07 Marks)
- 4 a. Derive the state machine (SM) chart for dice game and obtain the state graph for dice game controller. (10 Marks)
- b. Write a VHDL description of the state machine based on SM chart. (10 Marks)

Present state	Next state				Output $z_1 z_2$			
	$x_1 x_2 = 00$	01	10	11	$x_1 x_2 = 00$	01	10	11
S_0	S_3	S_2	S_1	S_0	00	10	11	01
S_1	S_0	S_1	S_2	S_3	10	10	11	11
S_2	S_3	S_0	S_1	S_1	00	10	11	01
S_3	S_2	S_2	S_1	S_0	00	00	01	01

- 5 a. Explain in brief with necessary SM charts, the linked state machines. (06 Marks)
- b. Discuss the programmable interconnects between the CLB (Configurable Logic Block) and I/O blocks with respect to
- General purpose interconnects. (08 Marks)
 - Direct interconnects.
- c. With a neat diagram explain the CLB as a Read / Write memory cell of Xilinx 4000 series FPGA. (06 Marks)
- 6 a. Design a floating point multiplier, explicitly showing the exponent adder, fraction multiplier and control network. (10 Marks)
- b. Explain operator over loading and write a source code for VHDL package with overloaded operation for bit-vectors. (06 Marks)
- c. Write a VHDL code for the following tristate buffers with active – high output enable (figure Q6 (c)). (04 Marks)

 


Fig. Q6 (c)

- 7 a. Write a VHDL source code to 4 bit adder using generate statement. (04 Marks)
- b. With a neat block diagram and truth table explain the 6116 static RAM. (07 Marks)
- c. Explain the simplified 486 bus model with a microprocessor bus interface and timing diagram of intel 486 basic 2 – 2 bus cycle. (09 Marks)
- 8 Write short notes on:
- Compilation / Simulation.
 - VHDL operators.
 - Synthesis.
 - Programmable Array Logic (PALs).
