

**Sixth Semester B.E. Degree Examination, Dec.2013/Jan.2014**  
**Microelectronics Circuits**

Time: 3 hrs.

Max. Marks:100

**Note: 1. Answer FIVE full questions, selecting at least TWO questions from each part.**  
**2. State all assumptions, including missing data.**

**PART – A**

- 1 a. Derive an expression for drain-to-source current  $i_{DS}$  from  $i_D$  v/s  $V_{DS}$  relationship for triode and saturation regions of n-MOSFET. (10 Marks)
- b. For an  $0.8\mu\text{m}$  technology for which  $t_{OX} = 15\text{nm}$ ,  $\mu_n = 550\text{ cm}^2/\text{V}$ . Find  $k'_n$  and  $c_{OX}$  and the overdrive voltage  $V_{ov} = V_{as} - V_t$  required to operate a transistor having  $W/L = 20$  in saturation with  $I_D = 0.2\text{ mA}$ . What is the minimum  $V_{DS}$  needed? (06 Marks)
- c. Design the circuit shown in Fig.Q.1(c) to obtain a drain voltage of  $0.1\text{V}$ . What is the effective resistance between drain and source? At this operating point, let  $V_t = 0.8\text{V}$  and  $K'_n\left(\frac{W}{L}\right) = 1\text{mA}/\text{V}^2$ . (04 Marks)

 


Fig.Q.1(c)

- 2 a. Briefly explain any two types of biasing methods in MOS amplifier circuits. (06 Marks)
- b. For a common source amplifier with  $g_m = 2\text{ mA}/\text{V}$ ,  $r_o = 50\text{K}\Omega$  and  $R_D = 10\text{K}\Omega$ .  $R_G = 10\text{M}\Omega$ ,  $R_L = 20\text{K}\Omega$  and  $R_{sig} = 0.5\text{M}\Omega$ . Calculate  $R_{in}$ ,  $G_v$ ,  $A_v$ ,  $A_{vo}$ ,  $R_{out}$ . (10 Marks)
- c. Mention any 4 comparison of important characteristics of MOSFET and the BJT. (04 Marks)
- 3 a. Explain the CMOS implementation of IC common source amplifier and hence explain how to determine its small signal voltage gain. (10 Marks)
- b. For the common gate amplifier with  $W/L = 4\mu\text{m}/0.2\mu\text{m}$ ,  $\mu_n C_{OX} = 350\text{ }\mu\text{A}/\text{V}^2$ ,  $r_o = 18\text{ K}\Omega$ .  $I_D = 100\mu\text{A}$ ,  $g_m = 1.2\text{ mA}/\text{V}$ ,  $\chi = 0.2$ ,  $R_s = 10\text{K}\Omega$ ,  $R_L = 100\text{ K}\Omega$ ,  $C_{gs} = 20\text{fF}$ ,  $C_{gd} = 5\text{fF}$ ,  $C_L = 5\text{fF}$ . Find  $A_{vo}$ ,  $R_{in}$ ,  $R_{out}$ ,  $G_v$ ,  $G_{is}$ ,  $G_i$  and  $f_{H}$ . (10 Marks)
- 4 a. Explain the circuit of MOS cascade amplifier and hence obtain an expression for short circuit transconductance  $G_M$ . (10 Marks)
- b. Explain briefly with neat circuit diagrams:
- Wilson MOS mirror
  - Widlar current source.

(10 Marks)

## PART - B

- 5 a. Explain the basic operation of BJT differential pair. (08 Marks)
- b. For the nMOS differential pair with a common-mode voltage  $V_{cm}$  applied as shown in Fig.Q.5(b). let  $V_{DD} = V_{SS} = 2.5V$ ,  $K'_n W/L = 3mA/V^2$ ,  $V_{th} = 0.7V$ ,  $I = 0.2mA$ ,  $R_D = 5K\Omega$ . Neglect channel length modulation.
- Find  $V_{OV}$  and  $V_{GS}$  for each transistor.
  - For  $V_{CM} = 0$  find  $V_{s1}$ ,  $i_{D1}$ ,  $i_{D2}$ ,  $V_{D1}$  and  $V_{D2}$ .
  - Repeat (ii) for  $V_{cm} = 1V$ .
  - What is the highest value of  $V_{cm}$  for which  $Q_1$  and  $Q_2$  remain in saturation, if current source  $I$  requires a minimum voltage of  $0.3V$  to operate properly. What is the lowest value for  $V_s$  and hence for  $V_{cm}$ . (12 Marks)

 


Fig.Q.5(b).

- 6 a. Explain briefly with expressions the properties of negative feedback. (08 Marks)
- b. A series-shunt feedback amplifier employs a basic amplifier with input and output resistances each of  $1K\Omega$  and gain  $A = 2000 V/V$ . The feedback factor  $\beta = 0.1 V/V$ . Find the gain  $A_f$  the input resistance  $R_i$  and output resistance  $R_o$  of the closed loop amplifier. (06 Marks)
- c. Explain briefly an alternative approach for finding loop gain  $A\beta$ . (06 Marks)
- 7 a. Explain instrumentation amplifier with neat circuit diagrams. (08 Marks)
- b. With neat diagram, explain the sample and hold circuit using opamp. (07 Marks)
- c. Derive an expression for an input resistance of the inverting amplifier taking into account the finite open loop gain  $A$  of the opamp shown in Fig.Q.7(c). (05 Marks)

 


Fig.Q.7(c)

- 8 a. Briefly discuss the parameters used to characterize the operation and performance of logic circuit families. (08 Marks)
- b. Write the expressions for propagation delay of an inverter. (05 Marks)
- c. Sketch a CMOS logic circuit that realizes the function  $Y = AB + \overline{A}\overline{B}$  using equivalence or co-incidence function. (07 Marks)

\*\*\*\*\*