

Sixth Semester B.E. Degree Examination, June/July 2014
Microelectronics Circuits

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions, selecting
atleast TWO questions from each part.**

PART – A

- 1 a. With a neat diagram, derive the expression for i_D in saturation and triode region. What happened to i_D if the channel length modulation is considered? (10 Marks)
- b. Draw the large signal equivalent circuit model of NMOS and explain. (04 Marks)
- c. Determine the voltages at all nodes and the currents through all the branches of following circuit. Let $V_t = 1V$ and $kn'(W/L) = 1mA/V^2$. Neglect the channel – length modulation effect. (06 Marks)

 


Fig.Q.1(c)

- 2 a. Show the development of the T equivalent – circuit model for the MOSFET from hybrid π model without channel length modulation. (06 Marks)
- b. Draw the circuit of common-source amplifier with a source resistance. Draw its small signal equivalent circuit with γ_0 neglected. Obtain the expression for V_{gs} , i_d , v_o , A_v , A_{v0} and the overall voltage gain G_v . (10 Marks)
- c. What is scaling? Differentiate constant field scaling and constant-voltage scaling. (04 Marks)
- 3 a. Briefly explain about short channel effect due to scaling. (06 Marks)
- b. Compare NMOSFET and BJT in terms of
- Current voltage characteristic.
 - High frequency model.
 - Output resistance. (06 Marks)
- c. Following figure shows the high frequency equivalent circuit of a common-source MOSFET amplifier. The amplifier is fed with a signal generator V_{sig} having a resistance R_{sig} . Resistance R in is due to the biasing network. Resistance R'_L is the parallel equivalent of the load resistance R_L , the drain bias resistance R_D , and the FET output resistance r_o . Capacitors c_{gs} and c_{gd} are the MOSFET internal capacitance:

- i) Draw the equivalent circuit at midband frequencies.
- ii) Draw the circuit for determining the resistance seen by C_{gs} .
- iii) Draw the circuit for determining the resistance seen by C_{gd} . For $R_{sig} = 100K\Omega$, $R_{in} = 420K\Omega$, $C_{gs} = C_{gd} = 1pF$, $g_m = 4mA/V$, and $R'_L = 3.33K\Omega$
- iv) Find the mid band voltage gain $A_M = V_0/V_{sig}$.
- v) Find the upper 3-dB frequency f_H . (08 Marks)

 


Fig.Q.3(c)

- 4 a. In common-gate amplifier with active load, obtain 3-dB frequency f_H using open circuit time constants. Draw the circuit required for determining R_{gs} and R_{gd} . (08 Marks)
- b. Draw the $C_D - C_S$, $C_D - C_E$ and $C_D - C_a$ configurations. (06 Marks)
- c. Draw an IC source follower circuit. Obtain its small signal equivalent circuit and obtain its voltage gain $A_v = \frac{V_0}{V_i}$. (06 Marks)

PART - B

- 5 a. Obtain common-gate and common-mode rejection ratio (CMRR) of the MOS differential amplifier. Also find the effect of R_D mismatch on CMRR. (12 Marks)
- b. Draw the two-stage CMOS op-amp configuration and briefly explain. Obtain overall dc open-loop gain. (08 Marks)
- 6 a. Briefly explain about
 - i) Voltage amplifier
 - ii) Current amplifier
 - iii) Trans conductance amplifier
 - iv) Trans resistance amplifier. (08 Marks)
- b. Explain about series-shunt feedback amplifier with diagram and obtain the expression for input impedance and output impedance. (08 Marks)
- c. Briefly explain about stability and pole locations. (04 Marks)
- 7 a. Draw and explain about weighted summer capable of implementing summing coefficients of both signs. (06 Marks)
- b. Explain about DC imperfections. (04 Marks)
- c. Write short notes on:
 - i) Antilogarithmic amplifiers.
 - ii) Analog multipliers. (10 Marks)
- 8 a. Draw the CMOS realization of A01 gate and explain with truth table. (08 Marks)
- b. Draw and explain the exclusive OR function using PUN and PDN. (08 Marks)
- c. What all are the parameters used to characterize the operation and performance of a logic circuit family. (04 Marks)

* * * * *