

**Sixth Semester B.E. Degree Examination, June/July 2017**  
**Microelectronic Circuits**

Time: 3 hrs.

Max. Marks: 100

**Note: Answer Three questions from Part A and Two from Part B.**

**PART – A**

- 1 a. Draw the  $i_D$ - $V_{DS}$  characteristics of an enhancement MOSFET. Indicate the all regions of operation and explain it. (07 Marks)
- b. For the circuit shown in Fig. Q1 (b), derive the expression of voltage gain, overall voltage gain, input impedance and output impedance. (10 Marks)

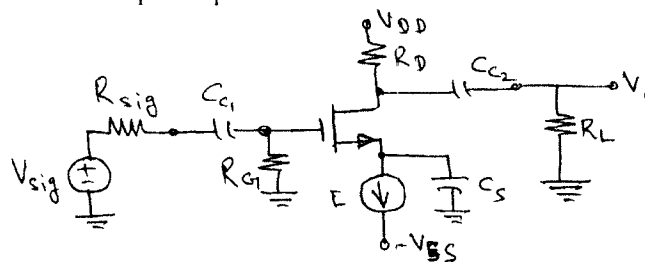


Fig. Q1 (b)

- c. An nMOS transistor has  $V_{t0} = 0.8$  V,  $2\phi_f = 0.7$  V and  $\gamma = 0.4$   $V^{1/2}$ . Find  $V_t$  when  $V_{SB} = 3$  V (03 Marks)
- 2 a. The high frequency response an amplifier is characterized by the transfer function,  

$$F_H(s) = \frac{1 - \frac{s}{10^5}}{\left(1 + \frac{s}{10^4}\right)\left(1 + \frac{s}{4 \times 10^5}\right)}$$
. Determine the 3-dB frequency. (04 Marks)
- b. Explain the operation of a current mirror using MOSFET. (08 Marks)
- c. Draw the circuit diagram to generate a number of constant currents of various magnitudes using BJT and explain it. (08 Marks)
- 3 a. Draw the circuit of a common gate amplifier with active load and explain it. (07 Marks)
- b. What is cascade amplifier? Mention the advantages of it. (04 Marks)
- c. Consider a common gate amplifier specified as follows:  $\frac{W}{L} = \frac{7.2 \mu\text{m}}{0.36 \mu\text{m}}$ ,  
 $\mu_n C_{ox} = 387 \mu\text{A}/\text{V}^2$ ,  $\gamma_0 = 18 \text{K}\Omega$ ,  $I_D = 100 \mu\text{A}$ ,  $g_m = 1.25 \text{mA}/\text{V}$ ,  $\psi = 0.2$ ,  $R_S = 10 \text{K}\Omega$ ,  
 $R_L = 100 \text{K}\Omega$ ,  $C_{gs} = 20 \text{fF}$ ,  $C_{gd} = 5 \text{fF}$  and  $C_L = 0$ . Find  $A_{VO}$ ,  $R_{in}$ ,  $R_{out}$ ,  $G_v$ ,  $G_{is}$  and  $G_i$ . (09 Marks)
- 4 a. Explain the operation of a MOS cascade amplifier. (06 Marks)
- b. What is the need for transistor pairings? Draw all transistor pairings and mention advantages of each. (08 Marks)
- c. Derive the expression of CMRR of a MOS differential amplifier for the two different cases. (06 Marks)

**PART – B**

- 5 a. Explain the operation of a active loaded MOS differential pair. (08 Marks)
- b. Why differential amplifiers are well suited for IC fabrication? (04 Marks)
- c. With neat circuit diagram, explain the operation of two-stage CMOS op-amp circuit. (08 Marks)
  
- 6 a. With a mathematical analysis, explain the effect of negative feedback on gain desensitivity and bandwidth extension. (08 Marks)
- b. Draw the structure of a series-shunt feedback amplifier and derive the expression of input and output impedance with feedback. (08 Marks)
- c. Draw the Root locus diagram for an amplifier with three poles and explain it. (04 Marks)
  
- 7 a. For the circuit shown in Fig. Q7 (a), determine the values of  $V_i$ ,  $i_1$ ,  $i_2$ ,  $V_o$  and  $i_L$ . Also determine the voltage gain  $\frac{V_o}{V_i}$ , current gain  $\frac{i_L}{i_1}$  and Power gain  $\frac{P_o}{P_i}$ . (07 Marks)

 


Fig. Q7 (a)

- b. Derive the output voltage expression of a logarithmic amplifier with temperature compensation. (09 Marks)
- c. With the help of waveform, explain the effect of slew rate limiting on output sinusoidal waveform. (04 Marks)
  
- 8 a. Define the following performance parameter of a logic circuit family and also draw the propagation delay and switching times waveform of the logic inverter.
  - (i) Noise margin
  - (ii) Propagation delay.
  - (iii) Robustness.
  - (iv) Delay-power product. (10 Marks)
- b. Implement the following expressions using AOI gates and also write logic equivalent circuit
  - (i)  $F = \overline{(A + B)(C + D)}$
  - (ii)  $F = XY + \overline{Z}$  (10 Marks)

\* \* \* \* \*