

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

NEW SCHEME

Sixth Semester B.E. Degree Examination, July 2006
E & EE

Power System Analysis and Stability

Time: 3 hrs.]

[Max. Marks: 100

Note: 1. Answer any FIVE full questions.

2. Assume the missing data, if any, suitably.

- 1 a. i) List any three advantages of per unit system of computations. (05 Marks)
ii) State the criteria for the selection of base quantities. (05 Marks)
- b. Show that the per-unit impedance of a transformer is the same when referred to either its primary side or the secondary side. (05 Marks)
- c. Draw the per unit impedance diagram for the system shown in fig.1(c), by taking a base of 100 MVA, 11 KV in the generator circuit. The various component ratings are: Transformer T1: 3 phase unit 90 MVA, 11/110 KV, $X=10\%$, Transformer T2: made up of 3 single-phase units each rated 33.33 MVA, 68/6.6 KV, $X=10\%$, Synchronous Generator: 80 MVA, 10 KV, $X=10\%$, Synchronous Motor: 95 MVA, 6.3 KV, $X=15\%$ and the line reactance is 20 ohms. (10 Marks)

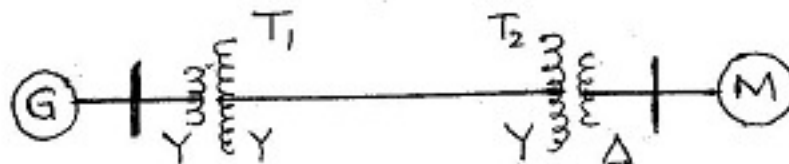


Fig.1(c)

- 2 a. A sudden 3-phase short circuit takes place at the terminals of an unloaded three-phase alternator. Discuss briefly on the different reactances that are met with assuming that the damper windings are provided at the pole faces of salient pole synchronous machine. (07 Marks)
- b. By stating the generalized algorithmic equations for determining the elements of the bus admittance matrix by the rule of inspection, obtain the matrix, Y_{BUS} for the resistive network shown in fig.2(b). All the values shown are in Ohms. (05 Marks)

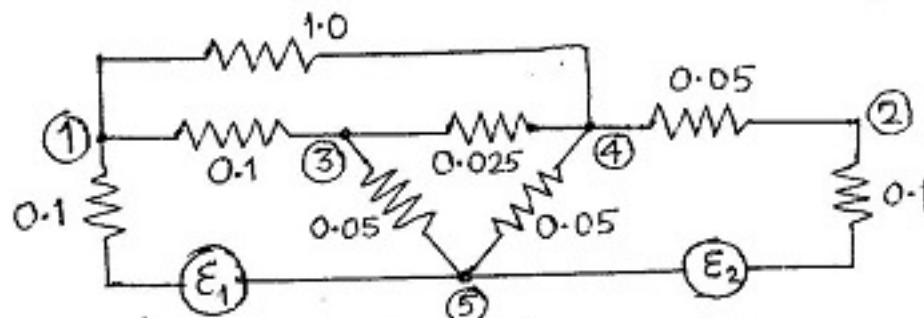


Fig.2(b)

Contd... 2

- c. A transmission line of inductance, $L = 0.1$ Henry and resistance, $R = 5$ Ohms, is suddenly short circuited at $t = 0$, at the far end of line as shown in fig.2(c). If the source voltage is: $v = 100 \sin(100\pi t + 15^\circ)$, obtain the following:
- Expression for the short circuit current, $i(t)$.
 - Exact value of the first current maximum and
 - Instant of short circuit at which the DC off-set current is zero. (08 Marks)

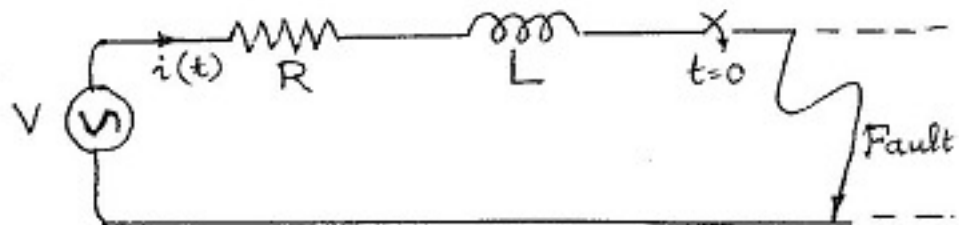


Fig.2(c)

- Derive an expression for the three phase complex power in terms of the sequence components and hence show that the symmetrical component transformation is power invariant. (06 Marks)
 - A balanced delta connected load is connected to a symmetrical three-phase system and supplied to it is a current of 15 amps. If the fuse in line-C melts, determine the symmetrical components of the line currents. (08 Marks)
 - A synchronous generator rated 500 KVA, 440 V, 0.1 pu sub-transient reactance is supplying a passive load of 400 KW at 0.8 pf (lag). Calculate the initial symmetrical (rms) current for a three-phase fault at the generator terminals. (06 Marks)
- With the help of the relevant phasor diagrams of voltages, show that there exists a phase shift of positive and negative sequence components in a three-phase Y- Δ transformer bank. Assume the HT side to be Y-connected and LT side, Δ -connected. (08 Marks)
 - Discuss on the sequence reactance - diagrams of transformers for their winding connections as follows: i) Y- Δ ii) Y-Y iii) Δ -Y iv) Δ - Δ (06 Marks)
 - Obtain the zero sequence diagrams for the system shown in fig.4(c). (06 Marks)

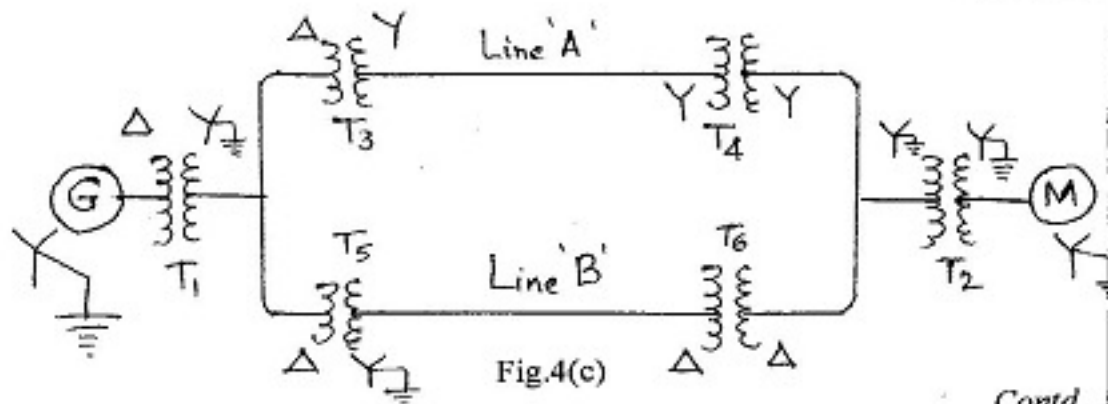


Fig.4(c)

Contd...

- 5 a. Show that the impedance Z_n between the Y-neutral and ground of a three-phase machine is represented equivalently as $3Z_n$ in its zero sequence diagram. (04 Marks)
- b. Derive the expression for the fault current in terms of the sequence impedances and hence obtain the connection diagram of the sequence networks for a line-to-line (LL) fault through the fault impedance, Z_f at the terminals of a Y-connected alternator. (10 Marks)
- c. A three-phase generator with constant internal voltages gave the fault currents under two different unsymmetrical faults as follows:
 L-L fault : 1400 Amperes and L-G fault : 2200 Amperes.
 If $E_{a1} = 2$ KV, and the positive sequence reactance is 2 Ohms, find the negative-sequence and zero-sequence impedance values. (06 Marks)
- 6 a. Discuss briefly about the open-conductor faults in electric power systems. (06 Marks)
- b. Three 6600 Volts, 10 MVA, 3-phase alternators are connected to a common set of bus-bars. Each has a positive-sequence reactance of 15%. The negative-sequence and zero-sequence reactances are respectively equal to 75% and 30% of the positive-sequence value. Find the fault current for L-G fault at the bus terminals if:
 i) Only one of the generator neutrals is solidly grounded.
 ii) Only one of the neutrals is earthed through a resistance of 0.3 Ohm. (14 Marks)
- 7 a. Distinguish between steady state stability and transient stability in power systems. Also elaborate on the corresponding power limits. (06 Marks)
- b. Develop the swing equation of a synchronous machine working on an infinite bus. (06 Marks)
- c. A 50 Hz, 4-pole turbo-alternator, rated 20 MVA, 11 KV has an inertia constant of $H = 9$ KWs/KVA. Find the acceleration if the input less the rotational losses is 26,800 HP and the electrical losses developed amount to 16 MW. (08 Marks)
- 8 a. Bring out the importance of the inertia constants M and H. (04 Marks)
- b. Explain the Equal Area Criterion of stability for a two-machine power system. State the assumptions made. (08 Marks)
- c. Obtain the power angle characteristic equations for a two-machine loss-less power system connected by a series impedance. (08 Marks)

ERROR: stackunderflow
OFFENDING COMMAND: ~

STACK: