

**Sixth Semester B.E. Degree Examination, June-July 2009**  
**Power System Analysis & Stability**

Time: 3 hrs.

Max. Marks:100

**Note: 1. Answer any FIVE full questions.**  
**2. Assume missing data suitably.**

- 1 a. What is per unit system? Mention the advantages of per unit system. (05 Marks)  
 b. What is one line diagram of a power system? What is its significance? (05 Marks)  
 c. A three winding transformer has rating as follows:
- |           |                    |         |          |
|-----------|--------------------|---------|----------|
| Primary   | Y connected        | 6.6 kV, | 15 MVA   |
| Secondary | Y connected        | 33 kV,  | 15 MVA   |
| Tertiary  | $\Delta$ connected | 2.2 kV, | 7.5 MVA. |

Leakage impedances measured from primary side as  $Z_{ps} = j 0.232 \Omega$ ,  $Z_{pt} = j 0.29 \Omega$  and on the secondary side  $Z_{st} = j 8.7 \Omega$ . Find the star connected equivalent on a base of 15 MVA, 6.6 kV in the primary circuit. Neglect resistances. (10 Marks)

- 2 a. Explain the concept of short circuit capacity. (05 Marks)  
 b. Determine the fault MVA, if a fault takes place at 'F' in the diagram, shown in Fig.2(b). The per unit values of reactances are given with 100 MVA as base. (15 Marks)

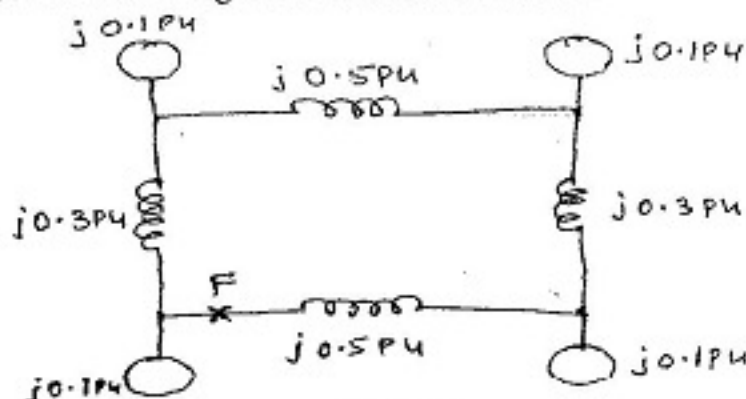


Fig.2(b)

- 3 a. Explain what are symmetrical components. How they are useful in solving the power system problems? (05 Marks)  
 b. Explain the effect of Neutral in the power system. (05 Marks)  
 c. A single phase resistive load of 100 kVA is connected across lines BC of a balanced supply of 3kV. Compute the symmetrical components of line currents. (10 Marks)
- 4 a. Explain sequence impedances and networks of synchronous generator. (05 Marks)  
 b. Draw the positive, negative and zero sequence networks for the power system. (15 Marks)

[Refer Fig.4(b) on Page 2]

Choose a base of 50 MVA, 220 kV in the 50  $\Omega$  transmission lines and mark all reactances in per unit. The ratings of the generators and transformers are

Gen 1 : 25 MVA, 11 kV,  $X'' = 20\%$ Gen 2 : 25 MVA, 11 kV,  $X'' = 20\%$ Three phase transformer (each) : 20 MVA, 11Y/220Y kV,  $X = 15\%$ 

The negative sequence reactances of each synchronous machine is equal to the sub transient reactances. The zero sequences reactances of lines are 250% of their positive sequences.

(15 Marks)

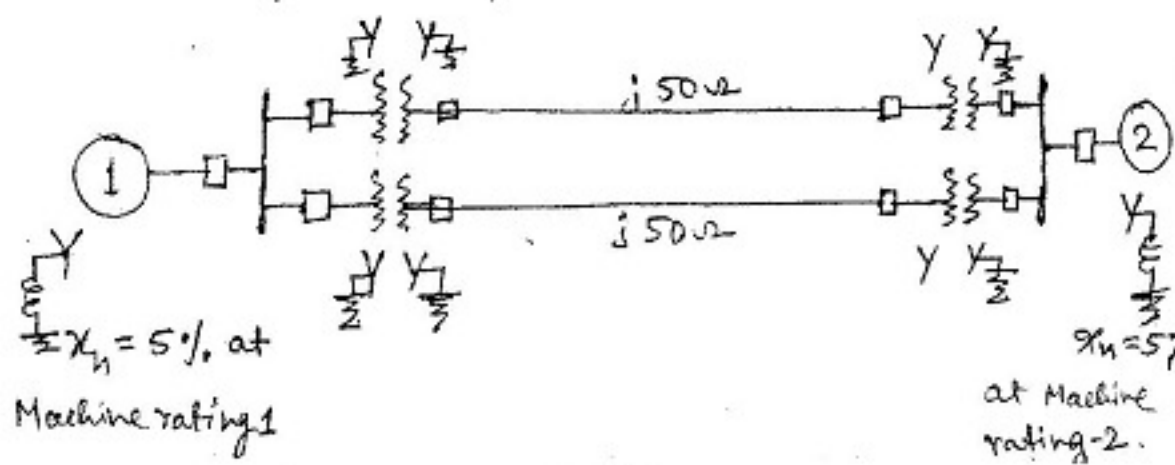


Fig.4(b)

- 5 a. For a double line to ground fault on unbalanced generator, derive the equation for the fault current and draw the connections and sequences networks. (10 Marks)
- b. A 3-phase alternator rated 40MVA, 11 kV, 50 Hz is running at rated speed and developing rated voltage. The generator neutral is isolated and a LLG fault takes place on phase b and c. Determine the fault current in p.u. Given  $X_1 = 0.3$  pu,  $X_2 = 0.2$  pu &  $X_0 = 0.1$  pu. Also find the fault current in amperes. (10 Marks)
- 6 a. Distinguish between steady state stability and transient stability in power system. (05 Marks)
- b. A two pole, 50 Hz, 11 kV turbo alternator has a rating of 100 MW, power factor 0.8 lagging. The rotor has a moment of inertia of  $10,000 \text{ kg.m}^2$ . Calculate H and M. (05 Marks)
- c. Explain the construction procedure of Clarke's diagram for a two machine system connected via impedances. (10 Marks)
- 7 a. Derive swing equation for a synchronous machine. (10 Marks)
- b. A 50 Hz generator is delivering 50% of the power that it is capable of delivering through a transmission line to an infinite bus. A fault occurs that increases the reactance between the generator and the infinite bus to 500% of the value before the fault. When the fault is isolated the maximum power that can be delivered is 75% of the original maximum value. Determine the critical clearing angle for the condition described. (10 Marks)
- 8 Write short notes on the following:
- Factors affecting the transient stability of a power system.
  - Equal area criterion (EAC)
  - Steady state stability analysis
  - Selection of C.B's