

--	--	--	--	--	--	--	--	--	--	--	--

Sixth Semester B.E. Degree Examination, June/July 2015
Power System Analysis and Stability

Time: 3 hrs.

Max. Marks:100

Note: 1. Answer any FIVE full questions, selecting at least TWO questions from each part.
2. Missing data, if any, may be suitably assumed.

PART – A

- 1 a. Define per unit quantity. Mention the advantages of per unit system. (05 Marks)
- b. Show that the per unit reactance is same for both HV and LV side of a two winding transformer. (05 Marks)
- c. The one line diagram of an unloaded generator is shown in Fig. Q1(c). Draw the PV reactance diagram. Choose a base of 50 MVA, 13.8 KV in the circuit of generator G₁.

The ratings are as follows :

G ₁ : 20 MVA, 13.8 KV, x'' = 20%	T ₁ : 25 MVA, 13.8/220 KV, x = 10%
G ₂ : 30 MVA, 18 KV, x'' = 20%	T ₂ : 30 MVA, 220/18 KV, x = 10%
G ₃ : 30 MVA, 20 KV, x'' = 20%	T ₃ : 35 MVA, 220/22 KV, x = 10%.

(10 Marks)

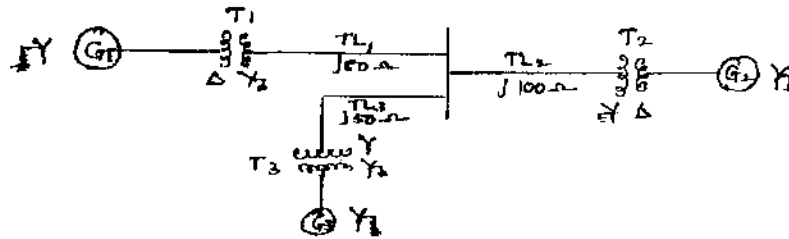


Fig.Q1(c)

- 2 a. With the oscillogram of the short circuit current of a synchronous machine, define sub transient reactance, transient and steady state reactances. (10 Marks)
- b. For the system shown in the Fig. Q2(b). The ratings of the various components are :

G : 25 MVA, 12.4 KV, x _d '' = 10%
M : 20 MVA, 3.8 KV, x _d '' = 15%
T ₁ : 25 MVA, 11/33 KV, x = 8%
T ₂ : 25 MVA, 33/3.3 KV, x = 10%
T line : 20 Ω reactance

The system is loaded such that, the motor is drawing 15 MW at 0.9 pf. leading, the motor terminal voltage being 3.1 KV. Find the sub-transient fault current at motor side. Choose 25 MVA as base power, 11 KV in the generator circuit. (10 Marks)


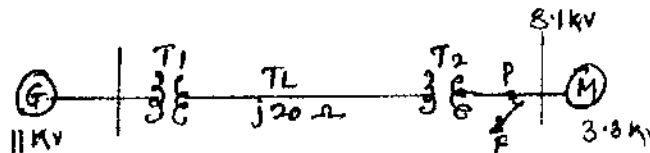


Fig.2Q(b)

- 3 a. Express symmetrical components in terms of unbalanced phasors. (06 Marks)
- b. Obtain an expression for the three – phase complex power in terms of sequence components. (08 Marks)
- c. In a 3 phase, 3 wire system the line currents are I_a = 100 ∠0°A and I_b = 100 ∠-100°A. Determine the sequence components of a line currents. (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

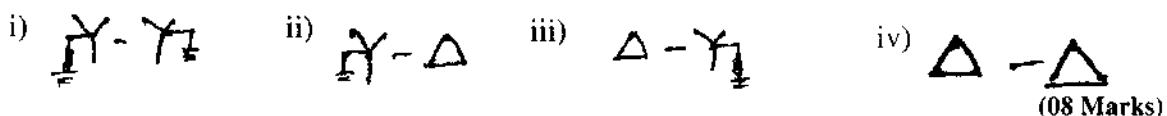- 4 a. What are sequence impedances and sequence networks? (04 Marks)
 b. Draw the zero sequence impedance network of a transformer for the following connection :



- c. Draw the positive, negative and zero sequence network for the power system shown in Fig. Q4(c).

Choose a base of 50 MVA, 220 KV in the 50 Ω Transmission lines and marks all reactance's in PV. The ratings of the generator and transformers are :

G_1 : 25 MVA, 11 KV, $x'' = 20\%$

G_2 : 25 MVA, 11 KV, $x'' = 20\%$

3φ transformers (each) : 20 MVA, 11/220 KV, $x = 15\%$

The negative sequence reactance of each synchronous machine is equal to the sub-transient reactance. The zero sequence reactance of a each machine is 8%. Assume that the zero sequence reactances of lines are 250% of their positive sequence reactances. (08 Marks)

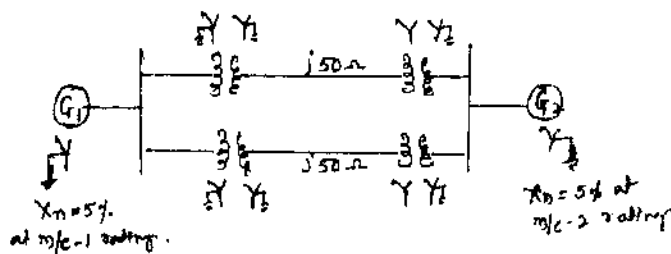


Fig. Q4(c)

PART - B

- 5 a. Define 'FAULTS' in power system. Give the classification of faults. (04 Marks)
 b. Derive an expression for fault current, when single line to ground (SLG) fault occurs on an unloaded generator. (08 Marks)
 c. A three phase generator with an open circuit voltage of 400 V is subjected to an SLG fault through a fault impedance of $j2 \Omega$. Determine the fault current, if $Z_1 = j4\Omega$, $Z_2 = j2\Omega$ and $Z_0 = j1\Omega$. Repeat the problem for LL fault. (08 Marks)
- 6 a. Derive expression for fault current if line-line-ground (LLG) fault occurs through fault impedance Z_f in power system. Show the connection of sequence networks to represent the fault. (10 Marks)
 b. Derive expression for fault currents for i) one conductor open fault ii) tow conductor open fault and draw the sequence network diagrams. (10 Marks)
- 7 a. Define stability pertaining to a power system and classify the different types of stability. (04 Marks)
 b. Derive the power angle equation of a non salient pole synchronous machine connected to an infinite bus. Draw the power angle curve. (10 Marks)
 c. A 2 pole, 50 Hz, 11 KV turbo alternator has a rating of 100 MW, 0.85 p.f. lagging. The rotor has a moment of inertia of 10000 kg-m^2 . Calculate H and M. (06 Marks)
- 8 Write short notes on :
 a. Swing equation
 b. Steady state and transient stability
 c. Equal area criterion for transient stability
 d. Analysis of 3 φ IM with one line open. (20 Marks)
