

Sixth Semester B.E. Degree Examination, Dec.09/Jan.10
Switch Gear and Protection

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting
at least TWO questions from each part.**

Part – A

- 1 a. With neat sketch explain the time current and cut-off characteristics of H.R.C fuse. What are the advantages and disadvantages of H.R.C fuse? (12 Marks)
- b. Explain the principle of D.C. circuit breaking. (08 Marks)
- 2 a. Explain the problems involved in interruption of low inductive and capacitive currents. (12 Marks)
- b. In a 220 kV system, the reactance and capacitance up to the location of circuit breaker is 8Ω and $0.025 \mu\text{F}$ respectively. A resistance of 600Ω is connected across the contacts of the circuit breaker. Determine the following:
 - i) Natural frequency of oscillation.
 - ii) Damped frequency of oscillation.
 - iii) Critical value of resistance which will give no transient oscillation.
 - iv) The value of resistance which will give damped frequency of oscillation, $\frac{1}{4}$ th of the natural frequency of oscillation. (08 Marks)
- 3 a. Explain the working of air blast circuit breaker with reference to i) Axial blast ii) Cross blast. (10 Marks)
- b. With neat sketch explain the construction and working of non-buffer type SF₆ breaker. (10 Marks)
- 4 a. With neat sketch explain construction and working of vacuum C.B. What are the advantages and disadvantages of the above? (10 Marks)
- b. With neat circuits, explain briefly the two types of synthetic test on circuit breaker. (10 Marks)

Part – B

- 5 a. What are the basic requirements of protective relaying? Explain briefly. (10 Marks)
- b. With the aid of neat sketch explain the operation of directional over current relay. (10 Marks)
- 6 a. Explain the principle of operation of, i) Percentage differential relay, ii) Voltage balance differential relay. (10 Marks)
- b. With the aid of neat diagram, explain Buchholz relay for protection of transformer. (10 Marks)
- 7 a. Draw and explain the Merz-Price protection of alternator stator windings. State its advantages. (10 Marks)
- b. The neutral point of a 11 kV alternator is earthed through a resistance of 12Ω , the relay is set to operate when there is out of balance current of 0.8 A. The C.T.S have a ratio of 200/5. What percentage of winding is protected against earth faults? What must be the minimum value of earthing resistance required to give 90% of protection to each phase? (10 Marks)
- 8 a. With the aid of neat circuit diagram, explain how protection for induction motor is given by, i) Single phase preventer ii) Ground fault protection. (12 Marks)
- b. A 11 kV/132 kV power transformer is connected in delta-star. The C.T.S on the low voltage side have turns ratio of 600/5. Find the suitable turns ratio for the C.T.S on high voltage side. (08 Marks)

Important Note: 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8=50, will be treated as malpractice.