

--	--	--	--	--	--	--	--	--	--

Sixth Semester B.E. Degree Examination, Dec.2015/Jan.2016

Switchgear and Protection

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART – A

- 1 a. Explain the construction and working of a HRC fuse with a neat sketch. List the advantages and disadvantages. (10 Marks)
- b. Write a short note on energy management of power. (05 Marks)
- c. Explain difference between isolating switch and load breaking switch. (05 Marks)
- 2 a. What is Resistance switching? Derive an expression for critical value of resistance to be added to circuit breaker. (08 Marks)
- b. Explain in detail, two theories of arc interruption in circuit Breakers. (06 Marks)
- c. In a 132KV system, the reactance and capacitance up to the location of the circuit breaker is 3Ω and 0.015 respectively. Calculate the following :
 - i) The frequency of transient oscillation
 - ii) Maximum value of restriking voltage across the contacts of the circuit Breaker and
 - iii) Maximum value of rate of rise restriking voltage. (06 Marks)
- 3 a. Explain the working of an air blast circuit breaker with reference to
 - i) Axial blast ii) Cross blast (12 Marks)
- b. Explain the properties of SF_6 gas. (08 Marks)
- 4 a. With a neat diagram explain the short circuit test on circuit breaker. (08 Marks)
- b. With a neat diagram, explain any one type of synthetic testing of circuit Breaker. (06 Marks)
- c. Explain the phenomenon of lightning discharge. (06 Marks)

PART – B

- 5 a. Explain the concept of primary and back up protection. (06 Marks)
- b. What are the essential qualities of a protective relay? Explain them briefly. (10 Marks)
- c. What is Relay? Define : i) Pickup level ii) burden iii) dropout with respect to relays. (04 Marks)
- 6 a. With a neat sketch, explain the working of induction type directional over current relay. (10 Marks)
- b. Explain with a neat circuit, the working of voltage balance differential relay. (05 Marks)
- c. Explain the working principle of an impedance Relay. (05 Marks)
- 7 a. Draw and explain the Merz – Price protection of alternator stator windings, state its advantage (Y and Δ connected alternators). (10 Marks)
- b. A 6.6KV, star connected alternator has a transient reactance of 2Ω per phase and negligible winding resistance. It is protected by circulating current Merz – Price protection. The alternator neutral is earthed through the resistance of 7.5Ω . The relays are set to operate when there is out of balance current of 1 ampere in secondary of 500/5 amper current transformers. How much % of winding is protected against earth fault? (10 Marks)
- 8 a. With the basic circuit diagram, explain the harmonic restraint relay protection for a transformer. (08 Marks)
- b. Explain single phasing in induction motors. How motor is protected from single phasing. (08 Marks)
- c. List the various abnormal conditions against which large induction motor has to be protected. (04 Marks)

* * * * *