

<b>NEW SCHEME</b>
-------------------

**Sixth Semester B.E. Degree Examination, July 2006**  
**Electrical and Electronics Engineering**  
**Switchgear and Protection**

Time: 3 hrs.]

[Max. Marks:100

Note: I. Answer any FIVE questions.

1.
  - a. Derive expressions for restriking voltage and RRRV in terms of system voltage, inductance voltage and capacitance. (08 Marks)
  - b. For a 132 kV system, the reactance and capacitance up to the location of the circuit breaker are  $3 \Omega$  and  $0.015 \mu\text{F}$  respectively. Calculate the following :
    - i) The frequency of transient oscillation,
    - ii) The maximum value of the restriking voltage across the contacts of the circuit breaker,
    - iii) The maximum value of RRRV. (06 Marks)
  - c. Explain the phenomenon of current chopping in a circuit breaker. (06 Marks)
2.
  - a. With a neat sketch describe the working principle of an axial air blast type circuit breaker. (10 Marks)
  - b. Describe the working principle of  $\text{SF}_6$  circuit breaker. What are its advantages over other types of circuit breakers? For what voltage range is it recommended?(10 Marks)
3.
  - a. Explain the following with reference to circuit breakers :
    - i) Breaking capacity ii) Making capacity iii) Short-time capacity.(07 Marks)
  - b. With a neat sketch describe the working principle of a liquid fuse. (07 Marks)
  - c. What do you mean by discrimination? Discuss discrimination between
    - i) two fuses and ii) a fuse and a over current relay. (06 Marks)
4.
  - a. The current ratings of an over current relay is 5A. It has a PSM = 2, TSM = 0.3, C.T. ratio = 400/5, Fault current = 4000 A. Determine the time of operation of the relay assuming normal IDMT characteristics. (04 Marks)
  - b. Explain time graded and current graded system for a feeder. (08 Marks)
  - c. With a neat sketch explain the principle of operation of a non-directional over current relay. (08 Marks)
5.
  - a. Explain the principle of working and operating characteristics of a percentage biased differential relay. (10 Marks)
  - b. Explain differential scheme of bus bar protection. What can be drawbacks of this scheme and how this can be overcome? (10 Marks)
6.
  - a. Explain the working principle and characteristics of an impedance relay. (06 Marks)
  - b. Describe the three-zone distance protection of transmission lines. (08 Marks)
  - c. Explain the principle of DC arc extinction in circuit breaker. (06 Marks)
7.
  - a. List the various abnormal operating conditions against which a modern large turbo-alternator has to be protected. (06 Marks)
  - b. Draw the connection diagram showing differential protection, negative sequence protection, over-current protection and earth fault protection of a Y-connected generator. (08 Marks)
  - c. List the various abnormal operating conditions against which a large induction motor has to be protected. (06 Marks)
8.
  - a. Explain the working of Buchholz relay. (08 Marks)
  - b. Describe the harmonic restraint relay used to protect transformers. (08 Marks)
  - c. A 3-phase transformer rated for 33 KV/6.6 KV is connected star/delta and the protecting current transformer on the low voltage side have a ratio of 400/5. Determine the ratio of the CT on the HV side. (04 Marks)