## **NEW SCHEME**

TICAL			ПП	
USN				1 1

Sixth Semester B.E. Degree Examination, July/August 2005

Electrical & Electronics Engineering

## Transformers and Induction Mechanics

Time: 3 hrs.]

[Max.Marks: 100

Note: Answer any FIVE full questions.

- 1. (a) Develop the phasor diagram of a single phase transformer under lagging p.f. load.

  (5 Marks)
  - (b) Draw the equivalent circuit of a transformer and describe briefly the various parameters involved in it.

    (5 Marks)
  - (c) A single-phase, 1100/220V transformer gave the following test results.
    - i) 1100V., 0.5A, 55W. on hv side, lv side being open circuited.
    - ii) 10V., 80A, 400W. on lv side, hv side being short circuited.

Draw the equivalent of the transformer and find the regulation and efficiency when supplying 100A at 220V 0.8p.f. lag.

(10 Marks)

- 2. (a) Derive an expression for load division between two dissimilar transformers connected in parallel with unequal voltage ratios.

  (10 Marks)
  - (b) A 5kVA, single phase transformer has a core loss of 40W and full load ohmic loss of 100W. The daily variation of load is as follows

7AM to 1PM - 3kW at 0.6p.f.

1PM to 6PM - 2kW at 0.8p.f.

6PM to 1AM - 6kW at 0.9p.f.

1AM to 7AM - No load.

Determine the all day efficiency of the transformer.

(10 Marks)

- 3. (a) What is an auto-transformer? Derive an expression for the saving of copper in an auto-transformer as compared to an equivalent two winding transformer. What are the advantages and limitations? (10 Marks)
  - (b) Two electric furnaces are supplied with single-phase current at 80V. from a 3 ph. 11kV. system through Scott connected transformers. The load on teaser secondary is 500 kW and on the main transformer secondary is 800 kW. Determine the line currents on the primary.
    - i) at u.p.f
- ii) 0.5 p.f.

(10 Marks)

- 4. (a) Starting from the fundamentals develop the equivalent circuit of a poly phase induction motor and also draw the phasor diagram when the motor is driving a load.

  (10 Marks)
  - (b) The power input to a 500V. 50 Hz, 6 pole 3 ph. IM. running at 975 rpm is 40 kW. The stator losses are 1kW and friction and windage losses total are 2kW. Calculate:
    - i) The slip
- ii) The rotor copper loss
- iii) The efficiency
- iv) The shaft torque.

Six

Time

1.

2.

3.

- 5. (a) With a neat sketch explain the working of a double cage IM. Draw its equivalent circuit.
  - (b) A 3ph. 400V., 20hp, 50Hz star connected IM, gave the following test readings (line-values)

No load

400V., 1250 W,

Blocked rotor : 150 V., 4000 W., 38 A.

Stator copper loss equal to rotor copper loss at stand still. Draw the circle diagram and estimate:

- Full load current
- Full load p.f ii)
- iii) Full load stiop
- iv) ratio of maximum torque to full load torque.

(12 Marks)

- 6. (a) Describe the different speed control methods of a 3-ph induction motor.
  - (b) With the help of a neat diagram explain the working of a star-delta starter (6 Marks) to start a 3-ph induction motor.
  - (c) A 3-ph induction motor in a short circuit current equal to 4 times the full load current. Determine the starting torque as a percentage of full load torque if (4 Marks) full load slip is 2.5%.
- 7. (a) Explain double field revolving theory as applied to a single phase induction motor and prove that it cannot produce any starting torque.
  - (b) With neat sketches explain the construction, working and applications of
    - Split phase and
    - ii) Capacitor start single phase induction motors.

(10 Marks)

- Write notes on any FOUR of the following: 8.
  - (a) Cooling of transformers
  - (b) Polarity test
  - (c) Sumpner's test
  - (d) Losses in induction motor
  - (e) Cogging and crawling
  - (f) Induction generator.

(4×5=20 Marks)