

--	--	--	--	--	--	--	--	--	--

Seventh Semester B.E. Degree Examination, December 2011
Power Electronics

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting at least TWO questions from each part.

PART – A

- 1 a. What are the important applications of power electronics? (06 Marks)
 b. Explain peripheral effects of power converter system. (06 Marks)
 c. Explain different types of power electronic converter circuits. (08 Marks)

- 2 a. Draw the equivalent model of BJT and explain the switching characteristics of power transistor. (08 Marks)
 b. Compare the BJT and MOSFET. (05 Marks)
 c. Discuss the different methods of providing isolation of gate drive circuits from power circuit. (07 Marks)

- 3 a. Explain the two transistor analogy of an SCR. Derive an expression for anode current. Also explain the process of regeneration cycle. (10 Marks)
 b. Write a short note on $\frac{dv}{dt}$ and $\frac{di}{dt}$ protection. (05 Marks)
 c. A UJT is connected across a 20 V DC supply. A valley and peak point voltages are 1 V and 15 V. The period of relaxation oscillation is 20 ms. Find the value of charging capacitor, if a charging resistor of 100 k Ω is used. (05 Marks)

- 4 a. Explain with the help of wave forms, 1- ϕ semi-converter (half bridge converter) with R-load. Derive an expression for $V_o(\text{avg})$ and $V_o(\text{rms})$. (10 Marks)
 b. A single phase dual converter is operated from 120 V, 50 Hz supply and the load resistance $R = 10 \Omega$ the circulating inductance $L_r = 40 \text{ mH}$ delay angle are $\alpha_1 = 60^\circ$ and $\alpha_2 = 120^\circ$. Calculate the peak circulating current and peak current of converter. (06 Marks)
 c. What is the use of free wheeling diode in a converter circuit? (04 Marks)

PART – B

- 5 a. Explain the self commutation with the help of neat sketch and obtain the expression for the capacitor voltage and current. (10 Marks)
 b. Distinguish between the natural and forced commutation. (05 Marks)
 c. In the parallel capacitor turn-off circuit shown in Fig. Q5 (c), the main SCRT, is to be reverse biased for at least 40 μs for proper commutation and holding current of auxiliary SCRT₂ is 2 mA. Determine the value of R and C. (05 Marks)

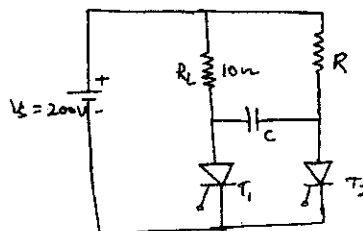


Fig. Q5 (c)

- 6 a. With the help of circuit diagram, explain the operation of single phase AC regulator using ON-OFF control. Derive the expression for rms value of load voltage. (10 Marks)
- b. Explain the single phase bidirectional AC voltage controller with resistive load with waveform. (10 Marks)
- 7 a. With neat circuit diagram and explain the four quadrant chopper. (08 Marks)
- b. With neat circuit diagram, explain the principle of operation of step up chopper. (08 Marks)
- c. A chopper circuit is operating on Time Ration Control (TRC) at a frequency of 2 kHz on a 460 V supply of the load voltage of 350 V. Calculate the conduction period of the thyristors in each cycle. (04 Marks)
- 8 a. Explain the performance of inverters. (06 Marks)
- b. With a neat circuit diagram, explain the principle of variable DC link. (08 Marks)
- Write a short note on CSI (Current Source Inverter). (06 Marks)

* * * * *