

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

Seventh Semester B.E. Degree Examination, December 2012
Power Electronics

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting
at least TWO questions from each part.**

PART – A

1. a. What is power electronics? Give two applications of P.E. (06 Marks)
 b. What is the difference between thyristor and a TRIAC? (04 Marks)
 c. What are the peripheral effects of power electronics equipments? (10 Marks)
2. a. What is a bipolar transistor and explain how many types are there and what are their three region operations? (10 Marks)
 b. What are pinch of voltage, threshold voltage and transconductance of MOSFET? (06 Marks)
 c. Compare BJT, MOSFET and IGBTs. (04 Marks)
3. a. What is the difference between SCR and a TRIAC? Explain its characteristics? (08 Marks)
 b. The input voltage of Fig.Q3(b) is $V_s = 200V$ with load resistance of $R = 5\Omega$. The load and stray inductance are negligible and the thyristor is operated at a frequency of $f_s = 2\text{ kHz}$. If the required dV/dt is $100\text{ V}/\mu\text{s}$ and the discharge current is to be limited to 100 A . Determine i) the value of R_s and C_s , ii) the scrubber loss and iii) the power rating of scrubber resistor. (08 Marks)

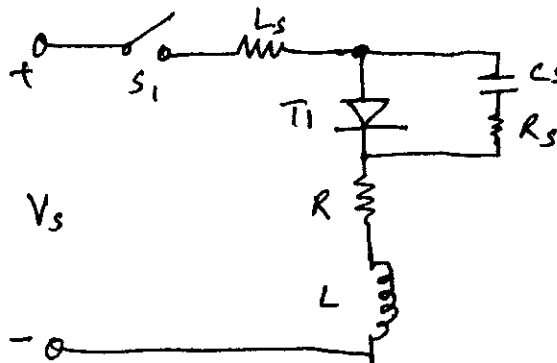


Fig.Q3(b)

- c. What is the common technique for voltage sharing and serial connected thyristor? (04 Marks)
4. a. With a neat diagram and waveforms, explain the principle of single phase full connectors purely resistive load. Derive the expression for voltage o/p voltage and rms o/p voltage. (10 Marks)
 b. What are the advantages and disadvantages of series converters? (06 Marks)
 c. How do you classify phase control converters? Explain. (04 Marks)

PART - B

- 5 a. Draw a circuit diagram and associated waveforms, explain the operation of a single phase bi-directional AC voltage controller with resistive load, obtain the rms output voltage. (10 Marks)
- b. An ac voltage controller in Fig.Q5(b) has a resistive load of $R = 10\Omega$ and the root-mean-square (rms) input voltage is $V_s = 120V$, 60 Hz. The thyristor switch is on for $n = 25$ cycles and is off for $m = 75$ cycles. Determine i) the rms output voltage V_o , ii) the input power factor (PF) and iii) the average and rms current of thyristors. (07 Marks)

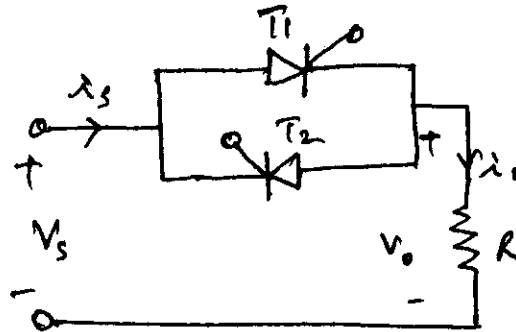


Fig.Q5(b)

- c. What are the advantages and disadvantages of ON-OFF control? (03 Marks)
- 6 a. What is an inverter? Explain its principle of operation (any one) with a neat diagram and waveforms. (08 Marks)
- b. What are the performance parameters of inverters? (06 Marks)
- c. How to differentiate 1 ϕ and 3 ϕ inverters? (06 Marks)
- 7 a. What is the principle of stepdown operation of chopper? (04 Marks)
- b. The stepdown chopper circuit shown in Fig.Q7b(i) & (ii), having resistive load. Derive an expression for the following:
 i) Average output voltage $V_o(av)$ ii) rms output voltage V_o (rms). (08 Marks)

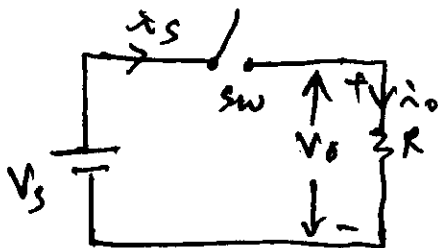


Fig.Q7b(i)

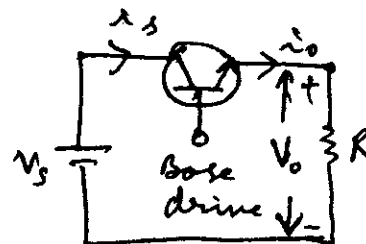


Fig.Q7b(ii)

- c. A chopper circuit is operating on TRC at a frequency of 2 kHz on a 460 V supply of the load voltage of 350V. Calculate the conduction period of the thyristor in each cycle. (08 Marks)
- 8 Write short notes on : (20 Marks)
- Communication techniques
 - Difference between ON-OFF control and phase control
 - Static induction transistor (SIT's)
 - Performance parameters of rectifier.
