

USN

--	--	--	--	--	--	--	--	--	--

10EC73

Seventh Semester B.E. Degree Examination, Feb./Mar. 2022
Power Electronics

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting at least TWO full questions from each part.

PART - A

1. a. Draw the control characteristics, circuit diagram and waveform of the following devices and explain it: i) SCR ii) GTO iii) MCT. (08 Marks)
- b. What are the different types of power electronic converter circuits and explain it. Also indicate the applications in each case. (08 Marks)
- c. Write a short note on peripheral effects associated with power converter. (04 Marks)
2. a. For the transistor circuit shown in Fig.Q.2(a). Find:
 - i) The value of R_B that results in saturation with an ODF of 5
 - ii) The β_{forced}
 - iii) Power loss in the transistor. Given $R_C = 11\Omega$, $V_{CC} = 200V$, $V_B = 10V$, $V_{BE(sat)} = 1.5V$, $V_{CE(sat)} = 1V$ and $\beta_{(mn)} = 8$. (08 Marks)

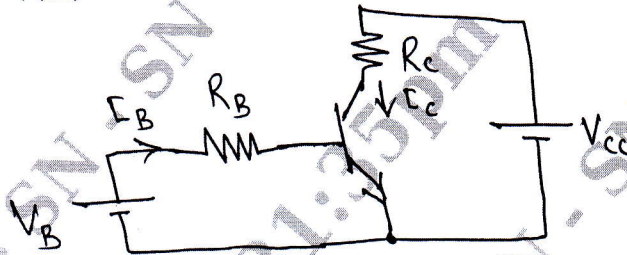


Fig.Q.2(a)

- b. With necessary waveforms, explain the switching characteristics of MOSFET. (06 Marks)
- c. What is base drive control? Discuss the different techniques for optimizing the base drive of a transistor. (06 Marks)
3. a. For the circuit shown in Fig.Q.3(a) with $V_S = 200V$, damping ratio is 0.7 and discharging current of the capacitor is 5A, determine:
 - i) The value of R_S and C_S
 - ii) The maximum $\frac{dv}{dt}$. (06 Marks)

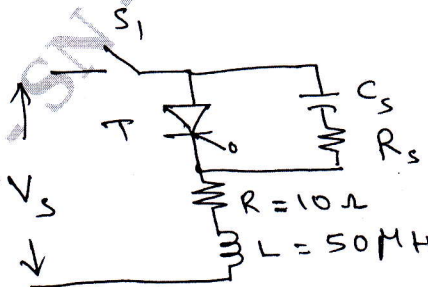


Fig.Q.3(a)

- b. Discuss the various methods of turn on the thyristors. (06 Marks)
- c. With necessary waveforms, explain the working of a UJT triggering circuit. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- 4 a. With a circuit diagram and waveforms explain the working of a single-phase semi converter with inductive load. (08 Marks)
- b. A single phase half wave controlled rectifier is used to supply power to 10Ω load from $230V, 50Hz$ supply at a firing angle of 30° find: i) Average output voltage ii) RMS value of output voltage iii) Average load current. (06 Marks)
- c. What are the functions of a free wheeling diode in a converter circuit? (03 Marks)
- d. What are the advantages of circulating current mode of a dual converters? (03 Marks)

PART - B

- 5 a. Derive the expression of

$$t_{\text{off}} = \sqrt{L_1 C} \tan^{-1} \frac{V_s}{I_o} \sqrt{\frac{C}{L_1}}$$

of a impulse commutation with accelerated recharging.

(08 Marks)

- b. With a circuit diagram and waveforms explain the operation of a complementary commutation. (08 Marks)
- c. For the circuit shown in Fig.Q.5(c), find the peak value of resonant current and conduction time of a Thyristor. Assume $V_0 = 200V$ (04 Marks)

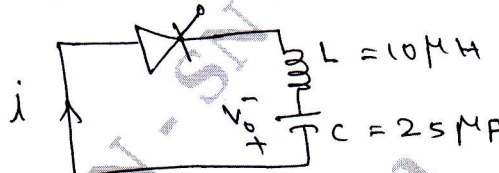


Fig.Q.5(c)

- 6 a. Explain the operation of a 1- ϕ controllers with inductive loads. (08 Marks)
- b. A 1- ϕ ac voltage controller shown in Fig.Q.6(b) has a resistive load of 10Ω and the input voltage $V_s = 120V, 60Hz$. The delay angle of thyristor is $\pi/2$. Determine:
- rms value of output voltage
 - Output power factor
 - Average output voltage
 - Average input current.

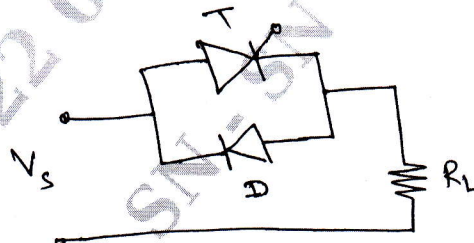


Fig.Q.6(b)

(08 Marks)

- c. In an ON-OFF control circuit using 1- $\phi, 230V, 50Hz$ supply, the ON time is 10 cycles, and OFF time is 4 cycles. Calculate the RMS value of the output voltage. (04 Marks)
- 7 a. A step down chopper is feeding an RL load with $V_s = 220V, R = 5\Omega, L = 7.5mH, f = 1kHz, K = 0.5$ and $E = 0V$. Calculate: i) Minimum instantaneous load current ii) Peak Instantaneous load current iii) Maximum P-P load current iv) Average value of load current. (08 Marks)
- b. With circuit diagram and waveforms explain the working of step up chopper. (08 Marks)
- c. Mention the applications of DC choppers. (04 Marks)

- 8 a. What are the applications of current source inverters? (04 Marks)
- b. With circuit diagram and waveforms, explain the operation of a 1- ϕ full bridge inverter. (08 Marks)
- c. A 1- ϕ transistorized bridge inverter has a resistive load of $R = 3\Omega$ and the dc input voltage of $E_{dc} = 48\text{volts}$. Determine:
- i) Transistor rating
 - ii) Total harmonic distortion
 - iii) Distortion factor
 - iv) Harmonic factor and distortion factor at the lowest order harmonic. (08 Marks)
