

USN

--	--	--	--	--	--	--	--	--	--

10EC73

Seventh Semester B.E. Degree Examination, Jan./Feb. 2023
Power Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, selecting at least TWO questions from each part.

PART - A

- 1
 - a. Give the definition of power electronics. Explain the relationship of power electronics to power, electronics and control. Mention any four applications of PE. (06 Marks)
 - b. With the circuit diagram, input and output waveforms, explain the control characteristics of:
 - (i) SCR
 - (ii) GTO
 - (iii) BJT
 - (iv) MOSFET
 (08 Marks)
 - c. What are the advantages of static power converters? Mention the peripheral effects of such static converters. (06 Marks)
- 2
 - a. Draw the transient model of BJT and explain the switching characteristics of power transistor. (10 Marks)
 - b. The bipolar transistor in Fig.Q2(b) is specified to have β in the range 8 to 40. The load resistance is $R_C = 11 \Omega$. The dc supply voltage is $V_{CC} = 200 \text{ V}$ and the input voltage to base circuit is $V_B = 10 \text{ V}$ if $V_{CE(\text{sat})} = 1.0 \text{ V}$ and $V_{BE(\text{sat})} = 1.5 \text{ V}$. Find:
 - (i) The value of R_B that results in saturation with an over drive factor of 5.
 - (ii) The forced β_f
 - (iii) The power loss P_T in the transistor

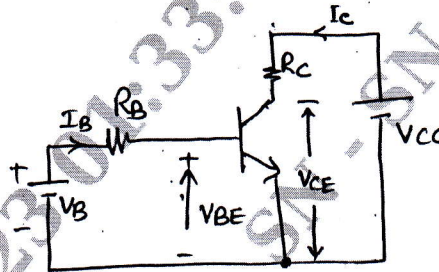


Fig.Q2(b)

- c. Compare the BJT and MOSFET. (06 Marks)
 - (04 Marks)
- 3
 - a. Sketch the V-I characteristics of an SCR and explain two transistor model of a thyristor and derive anode current expression. (10 Marks)
 - b. With the help of neat circuit diagram and waveforms, explain RC firing circuit used with half controlled rectifier. (06 Marks)
 - c. The latching current shown in Fig.Q3(c) is 50 mA. The duration of gate pulse is 50 μsec . Will the thyristor get fired?

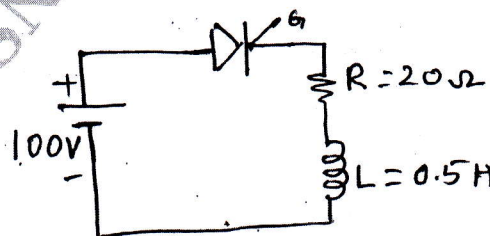


Fig.Q3(c)

(04 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- 4 a. With a neat circuit diagram and waveforms, explain the working of a single phase full converter feeding highly inductive load. Derive the expression for the average output voltage and rms output voltage. (10 Marks)
- b. If the converter of Fig.Q4(b) is as shown, has purely resistive load of R and the delay angle is $\alpha = \frac{\pi}{2}$, determine:
- The rectification efficiency
 - The form factor
 - The ripple factor

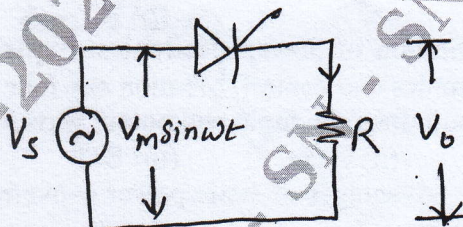


Fig.Q4(b)

(10 Marks)

PART - B

- 5 a. What is forced commutation? With the help of neat diagram and relevant equations, explain the operations of self commutation circuit. (10 Marks)
- b. Explain the complementary commutation with the help of neat circuit and waveforms. Also determine the circuit turn-off time, t_{off} , if the load resistance of $R_1 = R_2 = R = 5\Omega$, capacitance $C = 10 \mu f$ and supply voltage $V_s = 100 V$. (10 Marks)
- 6 a. With the help of circuit diagram, explain the operation of single phase full wave controller using ON-OFF control. Derive the expression for rms value of load voltage. (10 Marks)
- b. Explain the single phase bidirectional AC voltage controller with resistive load with waveform. Also discuss single phase full wave controller with one thyristor. (10 Marks)
- 7 a. With neat circuit diagram, explain the principal of operation of step up chopper. (08 Marks)
- b. Give the classification of Choppers. Explain briefly with relevant circuit diagrams. (12 Marks)
- 8 a. What do you mean by inverters? Explain the principle of operation of single phase half inverter. (08 Marks)
- b. Explain the performance parameters of an inverter. (06 Marks)
- c. With neat circuit, explain the variable DC link inverter. (06 Marks)
