

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EC73

## Seventh Semester B.E. Degree Examination, Jan./Feb. 2023 Power Electronics

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

### Module-1

- 1 a. Explain different types of power electronic circuits. (10 Marks)  
b. Explain peripheral effects of power electronic components and equipment and mention how to reduce them with a neat block diagram. (10 Marks)

OR

- 2 a. List different types of power MOSFET and explain p-channel depletion type in detail. (10 Marks)  
b. Explain the features and structure of IGBT. (10 Marks)

### Module-2

- 3 a. Explain two transistor model of SCR and derive an expression for anode current in terms of transistor parameters for a thyristor. (10 Marks)  
b. Explain static anode-cathode characteristics of SCR. (10 Marks)

OR

- 4 a. Explain gate characteristics of SCR with a neat diagram. (10 Marks)  
b. Explain different turn-on methods of SCR. (05 Marks)  
c. Differentiate between natural and forced commutation. (05 Marks)

### Module-3

- 5 a. Explain single phase full converter with the help of circuit diagram and waveforms. (10 Marks)  
b. The single phase dual converter is operated from a 120V, 60hz supply and the load resistance is  $R = 10\Omega$ . The circulating inductance is  $L_r = 40\text{mH}$  delay angles are  $\alpha_1 = 60^\circ$  and  $\alpha_2 = 120^\circ$ . Calculate the peak circulating current and the peak current of converter 1. (10 Marks)

OR

- 6 a. An on-off type ac regulator is operating with a resistive load of  $R = 10\Omega$  and the rms supply  $v/g$  is 230V. The controller remains on for 40 cycles and is off for 60 cycles. Determine:  
i) rms load  $v/g$  ii) Input power factor. (10 Marks)  
b. Explain the principle of phase controlled converter operation. (10 Marks)

**Module-4**

- 7 a. Explain buckboost regulator with neat circuit diagram and waveforms. (10 Marks)  
 b. The buck regulator has an input v/g of  $V_s = 12V$ . The required average o/p v/g is  $V_a = 5V$  at  $R = 500\Omega$  and the peak to peak o/p ripple v/g is  $20mV$ . The switching frequency is  $25kHz$ . If the peak to peak ripple current of inductor is limited to  $0.8A$ . Determine: i) Duty cycle  $K$   
 ii) The filter inductance iii) The filter capacitor  $C$  and iv) Critical values of  $L$  and  $C$ . (10 Marks)

OR

- 8 a. Explain different dc converter classification. (10 Marks)  
 b. The step down dc converter has a resistive load  $R = 10\Omega$  and the input voltage is  $V_s = 220V$ , when the converter switch remains on its v/g drop is  $u_{ch} = 2V$  and the chopping frequency  $f = 1kHz$ . If the duty cycle is  $50\%$ , determine: i) average output v/g  $v_a$  ii) rms o/p v/g  $v_o$   
 iii) Converter efficiency. (10 Marks)

**Module-5**

- 9 a. Explain single phase half bridge inverter with neat circuit diagram and waveforms. (10 Marks)  
 b. The single-phase half-bridge inverter has a resistive load of  $R = 2.4\Omega$  and the dc i/p v/g  $V_s = 48v$ . Determine i) the rms o/p v/g at the fundamental frequency  $V_{01}$ , ii) the output power  $P_0$  iii) average and peak currents of each transistor iv) the peak reverse blocking voltage  $V_{BR}$  of each transistor. (10 Marks)

OR

- 10 a. Explain dc switches with neat circuit diagram. (06 Marks)  
 b. Outline various performance parameters used for inverters. (08 Marks)  
 c. Explain single phase AC switches. (06 Marks)

\*\*\*\*\*