

USN

--	--	--	--	--	--	--	--	--	--

06EC73

**Seventh Semester B.E. Degree Examination, June/July 2011**  
**Power Electronics**

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting at least TWO questions from each part.**

**PART - A**

1. a. Give the definition of power electronics. Explain the relationship of power electronics to power, electronics and control. Mention any two applications of PE. (06 Marks)
- b. With the circuit diagram, input and output waveforms, explain the control characteristics of SCR and IGBT. (06 Marks)
- c. Explain any four different types of power converter circuits with the circuit, input and output waveforms. Also, mention one application of each type. (08 Marks)
2. a. What is the necessity of base drive control in a power transistor? Explain proportional base control. (08 Marks)
- b. A transistor switch of Fig.Q2(b) has  $\beta$  in the range of 8 to 40. Calculate i) the value of  $R_B$  that results in saturation, with an overdrive factor of 5. ii) The forced  $\beta_f$  and iii) The power loss in the transistor. (06 Marks)

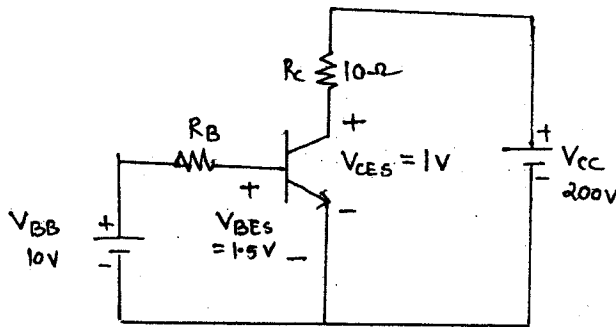


Fig.Q2(b)

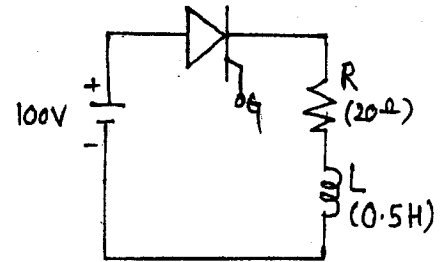


Fig.Q3(c)

- c. With necessary sketches, explain briefly the switching characteristics of an IGBT. (06 Marks)
3. a. Sketch the gate characteristics of an SCR and explain the different regions of gate characteristics. Also indicate different regions, different voltages and different currents on the gate characteristics. (10 Marks)
- b. With a neat circuit diagram and waveforms, explain the resistor triggering circuit. (06 Marks)
- c. The latching current of a thyristor shown in Fig.Q3(c) is 50 mA. The duration of gate pulse is 50 μsec. Will the thyristor get fired? (04 Marks)
4. a. With a neat circuit diagram and waveforms, explain the working of a single phase full converter feeding highly inductive load. Derive the expression for the average output voltage and rms output voltage. (10 Marks)
- b. Give the equations to show that the power factor of semiconverter is better than that of full converter. (04 Marks)
- c. Design UJT relaxation oscillator for triggering of thyristor. The UJT has the following parameters  $\eta = 0.7$ ,  $I_P = 50 \mu A$ ,  $V_V = 2V$ ,  $I_V = 6 mA$ ,  $V_{BB} = 20V$ ,  $R_{BB} = 7 k\Omega$ ,  $I_{EO} = 2 mA$ . Also determine the limits for the output frequency of the oscillator. Assume  $V_{g(min)} = 0.2V$ . (06 Marks)

Important Note : 1. On completing your answers, carefully draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appearance to evaluator and/or equations written eg. 42+8 = 50, will be treated as malpractice.

**PART - A**

- 5 a. With a neat circuit diagram and waveforms, explain the auxiliary commutation. (10 Marks)  
 b. For the complementary commutation circuit show in Fig.Q5(b), calculate the values of C to provide circuit turn off time of 20  $\mu$ sec. (06 Marks)

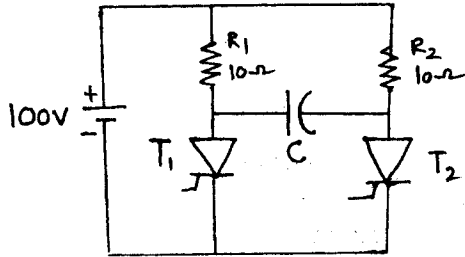


Fig.Q5(b)

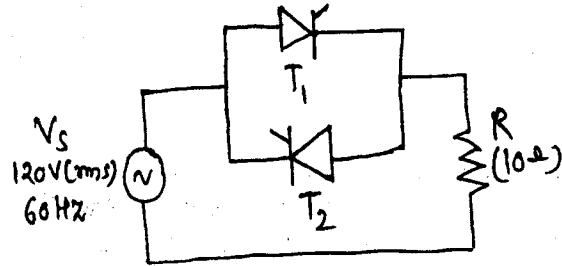


Fig.Q6(c)

- c. State the conditions under which load carrying thyristor can be successfully commutated. (04 Marks)
- 6 a. With a necessary waveforms, explain the operation of a single phase full wave controller with inductive load. Derive the expression for rms output voltage. (08 Marks)  
 b. What is an ac voltage controller? With the help of circuit diagram and waveform, explain the principle of phase control. (06 Marks)  
 c. A 1 $\phi$  full wave ACVC has a resistive load of  $R = 10 \Omega$  as shown in Fig.Q6(c). The input is  $V_s = 120 \text{ V(rms)}$ , 60 Hz. The delay angle of thyristors  $T_1$  and  $T_2$  are equal to  $\alpha_1 = \alpha_2 = \pi/2$ . Calculate i) rms output voltage ii) the average current through thyristors  $I_A$  iii) rms current of thyristors  $I_R$  iv) the input P.F. (06 Marks)
- 7 a. Explain the different control strategies used in choppers. (06 Marks)  
 b. With a neat circuit diagram and waveforms, explain the operation of Jones chopper. (10 Marks)  
 c. In the chopper circuit shown in Fig.Q7(c), the average output voltage is 109 V. The voltage drop across chopper switch when it is ON is  $V_s = 2 \text{ V}$ . The load resistor  $R = 10\Omega$ ,  $f = 1.5 \text{ kHz}$  and duty cycle ratio  $\delta = 50\%$ . Calculate the i) dc input voltage to the chopper ii) rms output voltage. (04 Marks)

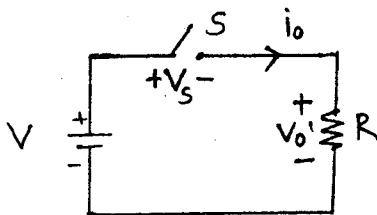


Fig.Q7(c)

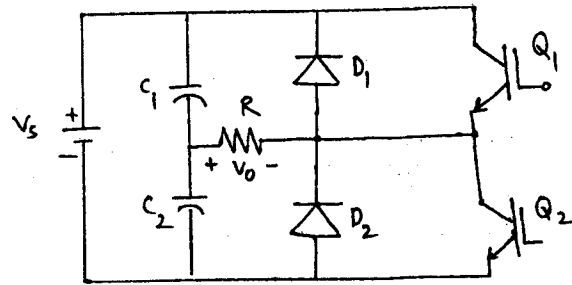


Fig.Q8(c)

- 8 a. With necessary sketches, explain the single phase transistorized current source inverter. (08 Marks)  
 b. With necessary waveforms, explain the single pulse width modulation technique of varying the magnitude of output voltage in a single-phase inverter. (06 Marks)  
 c. The single phase bridge inverter in Fig.Q8(c) has a resistive load of  $R = 2.4\Omega$  and the dc input voltage is  $V_s = 48\text{V}$ . Calculate i) the rms output voltage at the fundamental frequency  $V_{o1}$  ii) the output power iii) the average and peak currents of each transistor iv) the peak reverse blocking voltage  $V_{BR}$  of each transistor v) the THD vi) D.F. (06 Marks)

\*\*\*\*\*