

- c. A single phase half wave controlled rectifier is used to supply power to 10Ω load from 230V, 50 Hz supply at a firing angle of 30° . Calculate (i) average output voltage (ii) effective output voltage (iii) average load current. (06 Marks)

PART - B

- 5 a. What is the necessary condition for successful commutation of SCR? Compare between forced and natural commutation. (06 Marks)
- b. With necessary circuit and waveforms explain the working of complementary commutation. Also perform circuit analysis. (08 Marks)
- c. For the impulse commutated thyristor of circuit Fig.Q5(c), determine the turn-off time of the circuit, if $V_s = 200 \text{ V}$, $R = 10 \Omega$, $C = 5 \mu\text{F}$ and $V_c(t = 0) = V_s$. Also derive the equations used. (06 Marks)

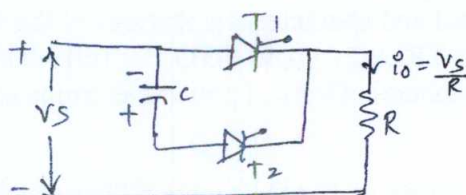


Fig.Q5(c)

- 6 a. With the help of neat circuit and relevant waveforms explain the working of ON-OFF control, for single phase AC voltage controller with resistive load. Also derive an expression for RMS output voltage. (08 Marks)
- b. A 1ϕ half wave ac voltage controller has an input voltage of 120 V, 60 Hz and a load resistance of 10Ω . The firing angle of thyristor is 60° . Find (i) RMS output voltage (ii) Input power factor (iii) Average input current. (08 Marks)
- c. What is the problem caused by sharp single pulse triggering in a 1ϕ AC voltage controller when the load is inductive? How can this be solved? (04 Marks)
- 7 a. Briefly explain the classification of choppers with circuit, waveforms and quadrant diagrams. (08 Marks)
- b. For the chopper shown in below Fig.Q7(b), DC source voltage is 200 V, load resistance is 20Ω . Consider the voltage drop of 4 V across chopper when it is ON. For a duty cycle of 0.6, calculate (i) Average and rms value of output voltage. (04 Marks)

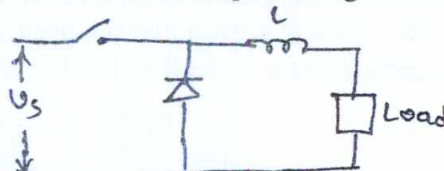


Fig.Q7(b)

- c. Explain the operation of step down chopper with RL load. Also derive an expression of peak-peak output ripple current. (08 Marks)
- 8 a. Explain the principle of single phase half bridge inverter with suitable circuit and waveforms. (10 Marks)
- b. Explain the performance parameters of inverter. (04 Marks)
- c. Explain principle of working of variable DC link inverter. Also mention advantages and disadvantages. (06 Marks)

* * * * *