

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18EC72

Seventh Semester B.E. Degree Examination, Dec.2023/Jan.2024 VLSI Design

Time: 3 hrs.

Max. Marks: 100

*Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.
2. Missing data may be suitably assumed.*

Module-1

- 1 a. Derive an expression for drain current in linear and saturation region. (08 Marks)
- b. Draw the CMOS inverter circuit and explain its D.C. characteristic. (08 Marks)
- c. Implement a 2:1 MUX using transmission gate. (04 Marks)

OR

- 2 a. Explain the non ideal IV effect of MOSFET with respect to CMOS channel length modulation and mobility degradation. (08 Marks)
- b. Explain the operation of nMOS transistor with IV characteristics. (08 Marks)
- c. Sketch a static CMOS gate computing $y = \overline{(A + B + C)D}$. (04 Marks)

Module-2

- 3 a. Explain CMOS nWell process with necessary diagrams. (12 Marks)
- b. Mention different types of MOSFET capacitances with necessary diagrams and equations also MOSFET. Capacitances in cut off, linear and saturation region. (08 Marks)

OR

- 4 a. Define scaling. Explain constant field scaling and constant voltage scaling and why constant voltage scaling is usually preferred over full scaling. (07 Marks)
- b. With neat diagram, explain the Lambda based design rules for two metal layers. (06 Marks)
- c. Draw the layout for $f = \overline{ABC}$ and estimate the cell area. (07 Marks)

Module-3

- 5 a. Develop the RC delay model to compute the delay of the logic circuit and calculate the delay of unit sized inverter driving another unit in vertex. (06 Marks)
- b. Estimate t_{pdf} and t_{pdr} for the 3 input NAND gate shown in Fig.Q.5(b) if the output is loaded with h identical NAND gates. (08 Marks)

 


Fig.Q.5(b)


- c. Explain eVSL with an example.

(06 Marks)

OR

- 6 a. Explain: i) Pseudo-nMOS ii) Ganged CMOS with necessary circuit examples. (06 Marks)
- b. If a unit transistor has $R = 10K\Omega$ and $e = 0.1fF$ in a 65nm process, compute the delay, in picoseconds, of the inverter Fig.Q.6(b) with a fan out of $h = 4$. (06 Marks)

Fig.Q.6(b)

 


- c. Explain linear delay model compare the logical effort of the following gates with the help of schematic diagrams: i) 3-input NAND gate ii) 3 input NOR gate. (08 Marks)

Module-4

- 7 a. Explain Resettable latches and flipflops using CMOS transmission gate. (06 Marks)
- b. Explain Dynamic logic. (06 Marks)
- c. Consider the two nFET chain in Fig.Q.7(c). The power supply is set to a value of $V_{DD} = 3.3V$ and the nFET threshold voltage is $V_{Tn} = 0.55V$. Find the output voltage V_{out} at the right side of the chain for the following values: i) $V_{in} = 2.9V$ ii) $V_{in} = 3.0V$ iii) $V_{in} = 1.4V$ iv) $V_{in} = 3.1V$. (08 Marks)


Fig.Q.7(c)

 

OR

- 8 a. Explain pulsed latches with schematic and waveforms. (06 Marks)
- b. The output of an nFET is used to drive the gate of another nFET as shown in Fig.Q.8(b). Assume that $V_{DD} = 3.3V$ and $V_{tn} = 0.6V$. Find the output voltage V_{out} when the input voltages are at following values:
 i) $V_a = 3.3V$ and $V_b = 3.3V$
 ii) $V_a = 2.0V$ and $V_b = 2.5V$.

Fig.Q.8(b)

 

- c. Explain Domino logic. (06 Marks)

Module-5

- 9 a. With neat schematic diagram explain the operation of Full CMOS static RAM cell. (10 Marks)
- b. Explain the different fault models. (10 Marks)

OR

- 10 a. With neat schematic diagram explain the operation of three transistor DRAM cell. (10 Marks)
- b. Write short notes on: i) Built in Self Test ii) Scan Design. (10 Marks)
